

# **DLD**

## **Syllabus:**

- 1. Number System**
- 2. Logic Functions**
- 3. Minimization**
- 4. Design & Synthesis of Combinational Circuits**
- 5. Sequential circuits**

# Number System - 59

## ① Introduction:-

Base-1  $\rightarrow$  0

Base-2  $\rightarrow$  0, 1

Base-8  $\rightarrow$  0, 1, 2, 3, 4, 5, 6, 7

~~Base-N  $\rightarrow$  0, 1, 2, ..., N-1.~~

Base-12  $\rightarrow$  0, 1, 2, ..., 9, A, B

Base-16  $\rightarrow$  0, 1, 2, ..., 9, A, B, C, D, E, F.

A  $\rightarrow$  10  
B  $\rightarrow$  11  
C  $\rightarrow$  12  
D  $\rightarrow$  13  
E  $\rightarrow$  14  
F  $\rightarrow$  15

Ex:-  $(0126)_6 \rightarrow$  Wrong  $(012\overset{2}{6})$

## ② Conversion to Base 10:-

$b_1 \rightarrow b_2$

~~i~~  $b_1 \rightarrow b_{10}$

~~ii~~  $b_{10} \rightarrow b_2$

①  $(abc)_x \rightarrow (?)_{10}$

$$= ax^2 + bx + cx^0$$

$$= (ax^2 + bx + c)_{10}$$

②  $(123)_7 = (?)_{10}$

$$1 \times 7^2 + 2 \times 7^1 + 3 \times 7^0$$

$$= 49 + 14 + 3$$

③  $(12AB)_6 = (?)_{10}$

$$\begin{aligned} & \times 16^3 + 2 \times 16^2 + A \times 16^1 + B \times 16^0 \\ & (16^3 + 2 \times 16^2 + 10 \times 16 + 11)_{10} \end{aligned}$$

④  $(1010)_2 = (?)_{10}$

$$(1010)_2$$

$$= 1 \times 2^3 + 1 \times 2^1 = 8 + 2 = (10)_{10}$$

⑤  $101010$   
 $3 \times 2^{e-2}$

$$32 + 8 + 2 = (42)_{10}$$

③ Conversion from base 10:-

$$\textcircled{1} \quad (11)_{10} \rightarrow (?)_2 \Rightarrow (1011)_2$$

$$11 = \begin{array}{r} 8 \ 4 \ 2 \ 1 \\ | \ 0 \ 1 \ 1 \end{array}$$

$$\textcircled{2} \quad (32)_{10} = (?)_2 \quad (100000)_2$$

$$32 = \begin{array}{r} 32 \ 16 \ 8 \ 4 \ 2 \ 1 \\ | \ 0 \ 0 \ 0 \ 0 \ 0 \end{array}$$

$$\textcircled{3} \quad (1056)_{16} = (?)_2$$

$$\begin{array}{r} 1056 = \cancel{00001000001010110} \\ \cancel{(0000001010110)}_2 \end{array}$$

$$1056 = \underbrace{(00010000001010110)}_2$$

$$\therefore \cancel{(0000001010110)}_2 = (?)_{16}$$

$$= \textcircled{4} \quad (1056)_{16}$$

$$\textcircled{4} \quad (273)_8 = (?)_2$$

$$273 = 010111011 = (10111011)_2$$

$$\textcircled{5} \quad (32)_{10} \rightarrow (?)_2$$

$$(32)_{10} \rightarrow \textcircled{6} \rightarrow (?)_2$$

$$(32)_{10} \rightarrow \begin{pmatrix} 00100000 \\ 100000 \end{pmatrix}$$

$$\textcircled{1} \quad (65)_{10} \rightarrow (?)_2$$

$$(65)_{10} \rightarrow (?)_{16} \rightarrow (?)_2$$

$$(41)_{16} \rightarrow 0100\ 0001 \quad , \quad (85F)_{16} \rightarrow (?)_2$$
$$\Rightarrow \underline{(1000001)}$$

$$⑥ \text{ If } (11)_2 + (22)_3 + (33)_4 + (44)_5 = (abc)_6$$

Find  $a, b, c$

$a, b, c$  values are  $0, 1, -1$

Convert to base 10

$$(11)_2 + (22)_3 + (33)_4 + (44)_5$$

$$3 + 8 + 15 + 20 = 46_{10}$$

$$(50)_{10} = (abc)_6$$

~~(82)~~  $(\begin{smallmatrix} 1 & b & c \\ 2 & 2 \end{smallmatrix})_6$

$$\begin{array}{r} 6 | 150 \\ 6 | 8 \\ 12 \end{array}$$

Find the following solution, determine the possible values of 'x'

① condition

$$(123)_5 = f(8)y$$

② ~~(123)~~ convert to base 10

$$(123)_5 \rightarrow 25 + 10 + 3 = 38$$

$$x < y; y > 8$$

$$38 = xy + 8$$

$$\Rightarrow xy = 30$$

$$(8)_y = 38$$

$$(130) \quad (2, 15)$$

$$x < y \& y > 8$$

$$1 \times 30 \cancel{x}$$

$$2 \times 15$$

$$3 \times 10$$

$$5 \times 6 \cancel{x}$$

$$6 \times 5 \cancel{1}$$

$$10 \times 3 \cancel{x}$$

$$15 \times 2 \cancel{x}$$

$$30 \times 1 \cancel{x}$$

$$\therefore (1, 30), (2, 15), (3, 10)$$

$$\therefore x = 1, 2, 3$$

$$\cancel{4, 5, 6, 7, 8, 9, 10}$$

(8) How many values of  $x$  and  $y$  are possible to

$$(12)_9 = (x_3)_y$$

$$x < y$$

$$y > 3$$

$$\Rightarrow (12)_9 = (38)_{10}$$

$$\therefore 38 = xy + 3$$

$$\therefore xy = 35$$

$$\begin{array}{c} x \\ \cancel{1, 2, 3, 4, 5, 6, 7, 8, 9, 10} \\ y \\ \cancel{5, 7, 11, 13, 17} \end{array}$$

$$1 \times 35$$

$$5 \times 7$$

$$7 \times 5 \cancel{x}$$

$$35 \times 1 \cancel{x}$$

$$x = 1, 5 \quad (1, 5) (5, 7)$$

$$y = 7, 35$$

(9)  $(123)_x = (12\cancel{x})_3$  ;  $x = \underline{\hspace{2cm}}$

- a) 3   b) -3, u   c) 3, -u   d) None

$$x > 3 \quad | \quad x < 3$$

$$\cancel{1, 2, 3, 4, 5, 6, 7, 8, 9, 10}$$

⑩ Determine the base of the system from following solution

$$a) 38 + 43 = 80$$

$$b) \text{Roots of } \alpha\sqrt{11x+22} = 0 \text{ are } 3, 6$$

$$c) \frac{66}{b} = 11$$

$$\textcircled{a) } 38_b + 43_b = 80_b$$

$$3b + 4b + 8 + 3 = 8b + 0$$

$$7b + 11 = 8b$$

$$\boxed{b = 11}$$

$$\textcircled{b) } ax^2 + bx + c = 0$$

~~(abc)~~

$$\text{Product of roots} = c/a$$

$$3b + 6b = \frac{22}{1_b} \rightarrow \textcircled{1}$$

~~$$(3 \cdot 6) + b = 22$$~~

$$\Rightarrow 3 \cdot 6 = \frac{2b + 2}{1}$$

$$2b = 18 - 2 = 16$$

$$\Rightarrow \boxed{b = 8}$$

base  $\textcircled{1}$  true

$$\textcircled{c) } \frac{66_b}{b_b} = 11_b \quad \text{all values of } b > 6$$

$$\Rightarrow \frac{6b + 6}{b} = b + 1 \Rightarrow 6b + 6 = b^2 + b$$

$$\Leftrightarrow \boxed{b + 1 = b + 1} \text{ for all values of } b$$

## (12) Complementary Number System:-

→ The main aim of complements is subtraction can be done using addition only (adder not subtractor).

Base-b: -  $\begin{cases} (b-1)'s \text{ complement} \\ b's \text{ complement} \end{cases}$

→  $b's$  complement is called as radix complement.

→  $(b-1)'s$  complement is called as diminished radix complement.

For number 8

$$(b-1)'s \text{ complement} = (b^n - 1) - x$$

$$b's \text{ complement} = b^n - x$$

Base-2: -  $\begin{cases} 1's \text{ complement}, \bar{x} = 2^n - 1 - x \\ 2's \text{ complement}, \bar{x} = 2^n - x \end{cases}$

Base-3  $\begin{cases} 2's \text{ complement}, \bar{x} = 3^n - 1 - x \\ 3's \text{ complement}, \bar{x} = 3^n - x \end{cases}$

$1's$  complement at base 2 is different to  $2's$  complement at base 3.

Base-10: -  $\begin{cases} 9's \text{ comp.}, \bar{x} = 10^n - 1 - x \end{cases}$

$\hookrightarrow 10's \text{ comp.}, \bar{x} = 10^n - x$

Base-16: -  $\begin{cases} 15's \text{ comp.}, \bar{x} = 16^n - 1 - x \end{cases}$

$\hookrightarrow 16's \text{ comp.}, \bar{x} = 16^n - x$

Range

nobih	SM	1's	2's
3	<del>0 to 3</del> -3 to +3	-3 to +3	-4 to 3
4	-7 to +7	-7 to +7	-8 to +7
n	$\rightarrow \left(2^{n-1}\right) b$ $+ \left(2^{n-1}\right) l$	$-(2^{n-1}) b$ $+ (2^{n-1}) l$	$-(2^{n-1}) b$ $+ (2^{n-1}) l$

③ Find the max five number that can be represented by 10 bits in 2's complement.

$$-2^{n-1} \text{ to } +2^{n-1}$$

$$-2^{10-1} \text{ to } +2^{10-1}$$

$$-2^9 \text{ to } +2^9$$

$$\Rightarrow 512 - 1 = \underline{\underline{511}}$$

511 is the answer

~~∴ 512 > 511~~

30)

### Gray code:-

→ It is reflexive, unit distance code,  
Cyclic code, belongs to non-weighted code.

→ 1 bit 2 combinations

$$0 - 0$$

$$1 - 1$$

→ 2 bits 4 combinations

0	0	0
1	0	1
2	1	1
3	1	0

Mirror reflective

→ 3 bits 8 combinations

0	0	0	0
1	0	0	1
2	0	1	1
3	0	1	0
4	1	1	0
5	1	1	1
6	1	0	1
7	1	0	0

→ 4 bit 16 combinations

0 - 0 0 0 0	0 1 1 0 1 / 0 0
1 - 0 0 0 1	0 0 0 1 1 / 1 1 0
2 - 0 0 1 1	1 1 0 0 1 / 0 0 1
3 - 0 0 1 0	1 1 0 0 0 / 0 0 0
4 - 0 1 1 0	1 1 0 0 0 0 / 0
5 - 0 1 1 1	0 0 0 0 0 / 1
6 - 0 1 0 1	0 0 0 0 1 / 0 1
7 - 0 1 0 0	0 0 0 0 0 / 0 0
8 - 1 1 0 0	
9 - 1 1 0 1	
10 - 1 1 1 1	
11 - 1 1 1 0	
12 - 1 0 1 0	
13 - 1 0 1 1	
14 - 1 0 0 1	
15 - 1 0 0 0	

→ (12) in BCD  $\rightarrow$  0001 0010

3221      0001 0010

gray      1010

Binary      1100

→ unit distance means for getting the next code only one bit is change (counting)


0010  
1110      → distance = 2

but in gray code distance b/w successive nos = 1

→ DM distance b/w last & first code = 1,  
so it is cyclic.

(31) Binary to array & vice-versa:-

$$① (12)_{10} \rightarrow (1100)$$

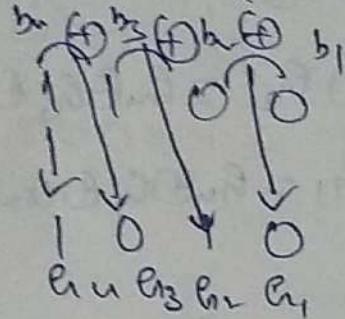

Binary  $\rightarrow$  array


array code of 12 = 1010

$$\cancel{b_4 \ b_3 \ b_2 \ b_1} \Rightarrow e_4 = b_4$$

$$e_3 = b_4 \oplus b_3$$

$$e_2 = b_3 \oplus b_2$$


$$e_1 = b_2 \oplus b_1$$

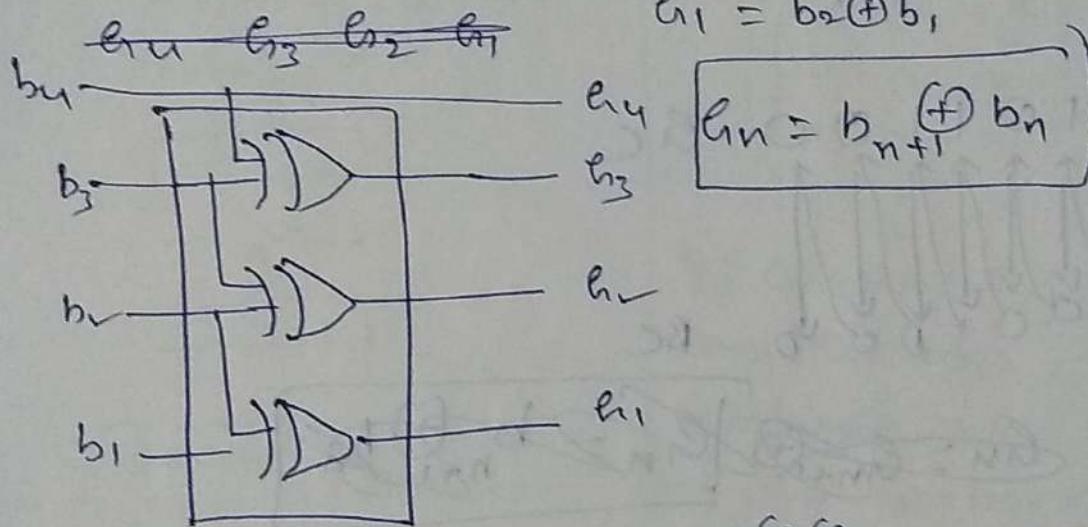


$$e_n = b_{n+1} \oplus b_n$$

$$② B \rightarrow G$$

$$③ 200 =$$

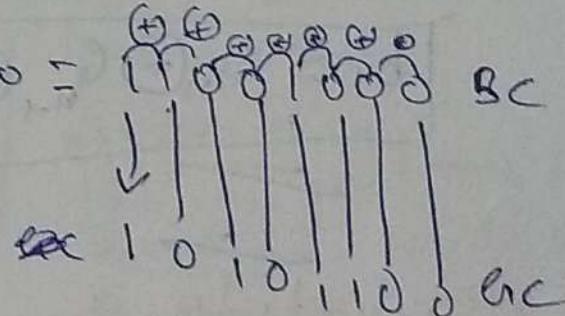

array code  $\rightarrow$  Binary

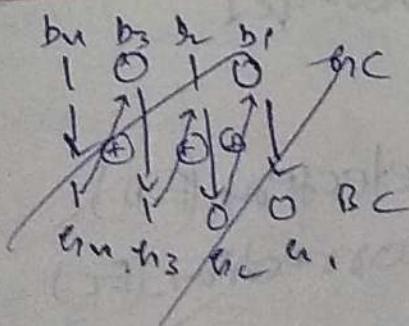

$$b_4 = e_4$$

$$b_3 = e_4 \oplus e_3$$

$$b_2 = e_3 \oplus e_2$$

$$b_1 = e_2 \oplus e_1$$


# Logic Gates

Logic gate:- Fundamental building block of a digital system.


Basic gates:- AND(N), OR(V), NOT( $\sim$ )

Universal gates:- NAND( $\uparrow$ ), NOR( $\downarrow$ ).


AND (N)

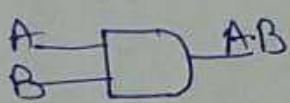

OR (V)


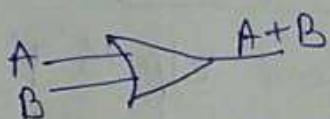


NOT ( $\sim 1-1'$ )


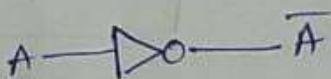


A	B	$A \cdot B$	$A + B$	$\bar{A}$
0	0	0	0	1
0	1	0	1	1
1	0	0	1	0
1	1	1	1	0

NAND( $\overline{AB}$ )

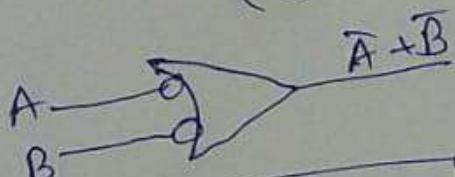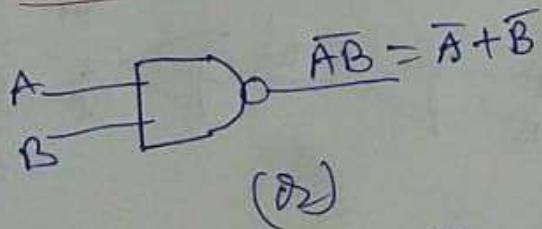


NOR( $\overline{A+B}$ )

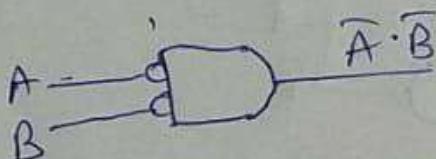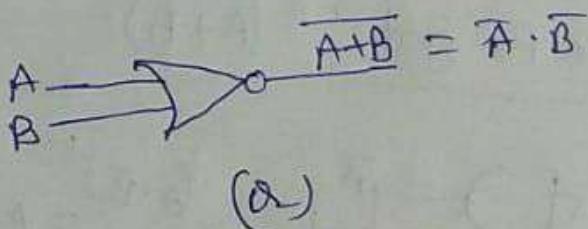


A	B	$\overline{AB}$	$\overline{A+B}$
0	0	1	0
0	1	1	0
1	0	0	0
1	1	0	0

Ex-OR gate ( $\oplus$ ) :-  $A \oplus B$

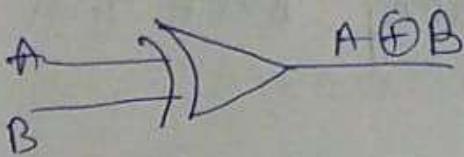

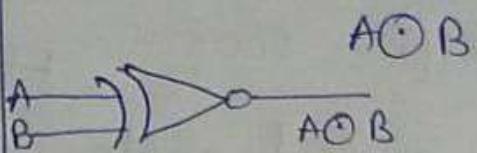
Ex-NOR gate ( $\ominus$ ) :-  $A \ominus B$



A	B	$A \oplus B$	$A \ominus B$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

$\oplus$  :- diff i/p then o/p is '1'.  
 $\ominus$  :- same i/p then o/p is '0'.


① AND gate :-  $(A \cdot B)$

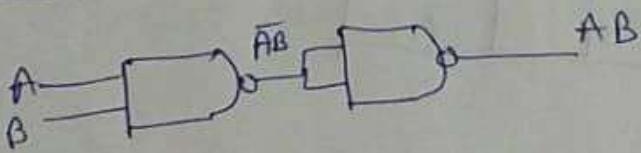

$$x \rightarrow \text{AND} \rightarrow \bar{x} \quad (\bar{x} + \bar{y})^1 = xy$$

$$y \rightarrow \text{AND} \rightarrow \bar{y}$$



② OR gate :-  $(A + B)$

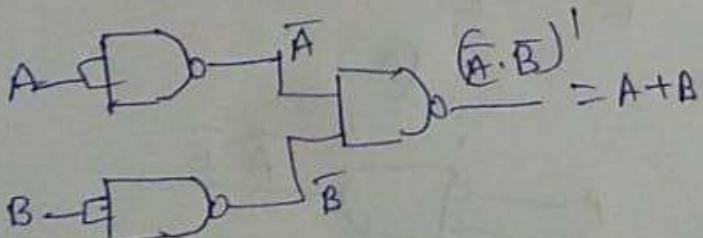




$$A \rightarrow \text{NOT} \rightarrow \bar{A} \quad (A + B) \rightarrow \text{OR} \rightarrow (A + B)^1$$

$$B \rightarrow \text{NOT} \rightarrow \bar{B} \quad (A + B)^1 = A + B$$

③ NOT gate ( $\bar{A}$ ) :-

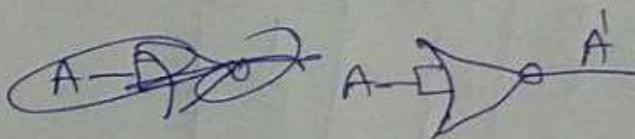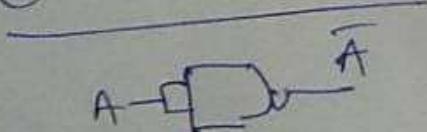

④ XOR ( $A \oplus B$ ):-

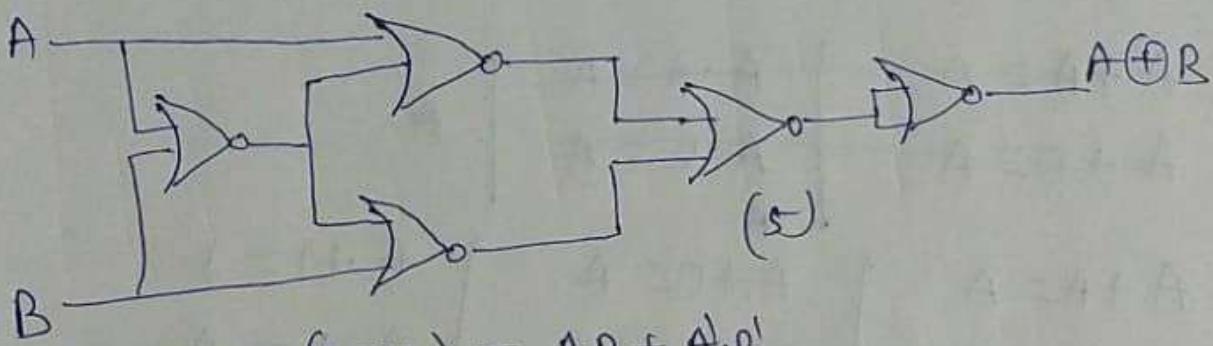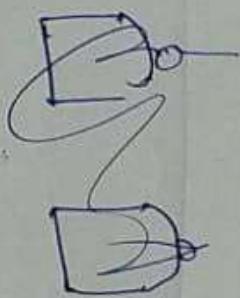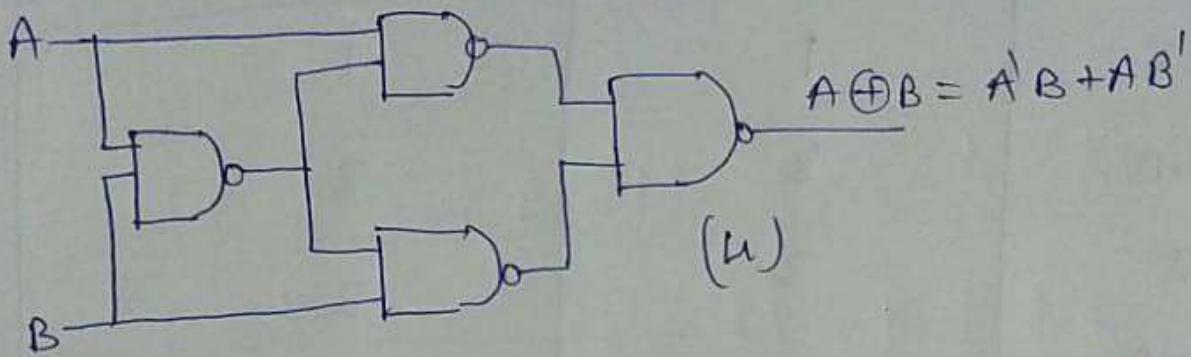

⑤ XNOR ( $A \odot B$ ) =  $AB + A \cdot B'$

Replace NAND with NOR gates.

(5)

(n)

Function to be realized	Min. NAND required	Min. NOR required
NOT	1	1
AND	2	3
OR	3	2
NAND	1	4
NOR	4	1
EX-OR	4	5
EX-NOR	5	4

$$\begin{array}{c|c|c}
 \cancel{A+A=A} & \cancel{A \cdot A = A} & \\
 \cancel{A+0=A} & \cancel{A \cdot 0 = A} & \\
 \hline
 \textcircled{1} \quad \begin{array}{c|c|c}
 A+A=A & A+0=A & A+1=1 \\
 A \cdot A = A & A \cdot 0 = 0 & A \cdot 1 = A
 \end{array} & 
 \end{array}$$

$$\textcircled{2} \quad A + \overline{A} = 1 \\
 A \cdot \overline{A} = 0$$

$$\textcircled{3} \quad (A+B)' = \overline{A} \cdot \overline{B} = A' \cdot B' \\
 (AB)' = A' + B'$$

## Syllabus

Logic functions, Minimization, Design and Synthesis of combinational and sequential circuitry, Number representation and Computer Arithmetic (fixed and floating point).

- ① Logic functions (32)
- ② Minimization (40)
- ③ Design and synthesis of combinational circ (64)
- ④ Sequential (44) (51)
- ⑤ Number System (59)
- ⑥ Practice questions (8)

### ① Logic functions

#### ① Basic Properties of Switching Algebra:-

A basic element of switching algebra is boolean variable. Boolean variable value is either 0 or 1.

{0, 1}.

Switching algebra operators. + OR

• AND  
~ (NOT)

		f	.	~
		0	0	1
		0	1	0
1	0	1	0	1
1	1	1	1	0

## Basic Properties:-

① Idempotency :-  $x \cdot x = x$

$$x+x = x \quad \text{go to truth table}$$

$$\left. \begin{array}{l} x+1=1 \\ x \cdot 0=0 \end{array} \right\} \quad \left. \begin{array}{l} x+0=x \\ x \cdot 1=x \end{array} \right\} \rightarrow \begin{array}{l} 1 \leftrightarrow 1 \\ 0 \leftrightarrow 1 \end{array}$$

(go to truth table)

ii) Commutativity :-

$$x+y=y+x$$

$$xy=yx$$

iii) Associativity :-

$$x+(y+z) = (x+y)+z$$

$$x(yz) = (xy)z$$

iv) Complementation :-

$$x + \bar{x} = 1$$

$$x \cdot \bar{x} = 0$$

v) Distributivity :-

$$x(y+z) = xy + xz$$

$$* x+yz = (x+y)(x+z)$$

→ Associativity

$\left[ \begin{array}{l} \text{left Asso.} \\ \text{right Asso.} \end{array} \right]$

$$\begin{aligned} & a+b+c \\ & ((a+b)+c) - LA \\ & (a+(b+c)) - RA \end{aligned}$$

$$x(\cancel{x+y}) = x(y+z) = xy + xz$$

\* last checking  $x=0 \Rightarrow 0(y+z) = 0y+0z$   
 $0=0$

$x=1$   $\Rightarrow 1(y+z) = 1 \cdot y + 1 \cdot z$   
 $y+z = y+z$

$$\therefore x(y+z) = xy + xz$$

→ In all the above it is happened  
 $\Leftrightarrow 0 \leftrightarrow 1$  It is called  
 principle of "Duality".

### ② Switching Expression and Simplification

Switching expression is a finite no. of combinations of switching variables and constants {0,1} by means of switching operations

(+, ·, NOT)

Ex:-  $x + \bar{y}yz + \bar{y}\bar{z}$ ,  $a+b\bar{c}+\bar{b}d$

Properties for Simplifying SE:-

① Absorption :-

$$\boxed{\begin{aligned} x+x\bar{y} &= x \\ x+x'y &= x+y \end{aligned}}$$

$$\begin{aligned} x+xy & \\ x(1+y) &= x \end{aligned}$$

② Dual :-  $x \cdot \cancel{(x+y)}$

$$(x+x)(x+y) = x$$

$$x(x+y) = x$$

$$\begin{aligned} x+x'y & \\ (x+x')(x+y) & \\ 1(x+y) & \\ x+y & \end{aligned}$$

Dual

$$x \cdot (1+y) = x \cdot y$$

$$x \cdot 1 + x \cdot y = xy$$

$$0 + xy = xy \Rightarrow xy = xy$$

Conservancy Theorem:-

$$\boxed{xy + \bar{x}y + yz = xy + \bar{x}y}$$

$$\begin{aligned} xy + \bar{x}y + yz(1) &= xy + \bar{x}y + yz(x + \bar{x}) \\ &= xy + \underbrace{\bar{x}y}_{\text{Redundant}} + \underbrace{xyz + \bar{x}yz}_{\text{Redundant}} \\ &= xy(1 + z) + \bar{x}y(1 + z) \\ &= xy + \bar{x}y \end{aligned}$$

$$\begin{aligned} &\boxed{xy + \bar{x}y + yz = xy + \bar{x}y} \\ &\cancel{\boxed{xy + \bar{x}y + yz}} \quad (\text{Redundant}) \\ &\Rightarrow xy + \bar{x}y \end{aligned}$$

\* In place of  $x$ , there will be a big expression.

①

$$xy'z + yz + xz = ?$$

$$\Rightarrow z(x'y + y + x) \quad (\text{In TDC, not commutative})$$

$$z((y+x)(y+x') + x)$$


$$z(x' + y + x) = z(x' + x + y) = z(y) = z$$

③ De Morgan's Law and Simplification:-

$$\begin{aligned} (\bar{x} \cdot y) &= \bar{x} + y & + \leftrightarrow \cdot \\ (\bar{x} + y)' &= \bar{x} \cdot \bar{y} & \times \leftrightarrow \bar{x} \\ & & 0 \leftrightarrow 1 \end{aligned}$$


$$f(a, b, c, \dots, \bar{z}, 0, 1, \cdot, +, \cdot)$$
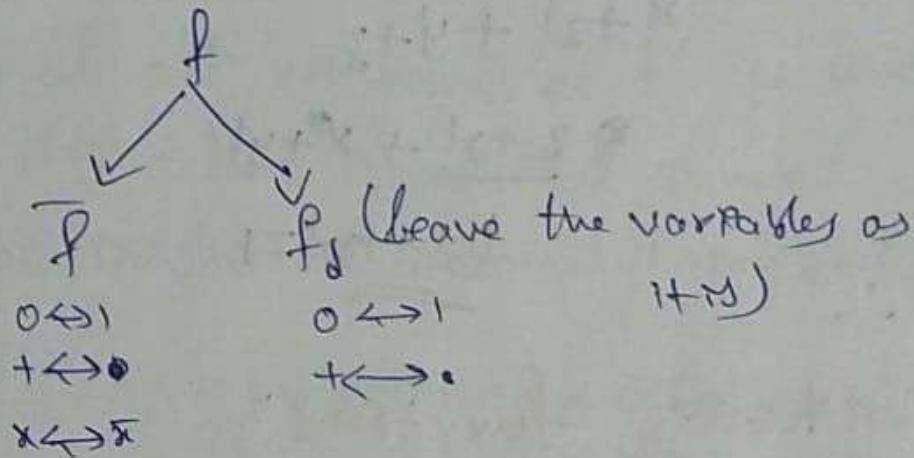
$$f_d = f(a', b', c', \dots, \bar{z}', 1, 0, +, \cdot)$$



$$\text{Ex:- } f = \bar{x} + \bar{y}$$
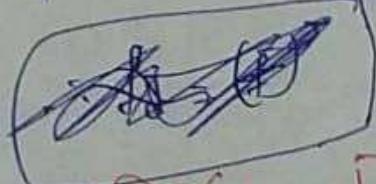
$$f = x \cdot y ; f_d = \bar{x} \cdot \bar{y}$$



$$\textcircled{9} \quad (x+y)[x(y+z)]' + xy + xz = ?$$

$$(x+y)(x+yz) + xy + xz$$

$$(x+y)(x+y)(x+z) + xy + xz$$

$$(x+y)(1+z) + xy + xz$$

$$1 + xz + xz + yz + xy + xz$$

$$x(1-y+z) + yz + xy' + x'y$$

$$x + yz + xy' + x'y$$

$$x + xy' + yz + x'y$$

$$(x+y)(x+y') + yz + x'y$$

$$x + y' + yz + x'y$$

$$\underline{x + x'y} + \underline{y' + yz}$$

$$x + y + yz$$

$$\underline{z + y} + \underline{x + y'}$$

$$1 + x + y' = 1$$

$\therefore$  L.H.S.  $\equiv$

#### ④ Switching functions:-

$$f(a, b, c) = a + bc$$

a	b	c	f	f'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

→ Boolean expression defining a function.

## (5) Canonical Forms:- (SOP, POS)

- A product term which contains each of 'n' variables as factors either in complemented or un-complemented form is called a "Minterm".
- A minterm given the value '1' for exactly one combination of the variables.
- The sum of all minterms of 'f' for which 'f' assumes '1' is called canonical sum of products (or) Disjunctive Normal Form (DNF).

Minterms are:-

$$\begin{array}{cccccc} abc & + & \bar{a}bc & + & \bar{a}\bar{b}c & + \\ \text{111} & & \text{011} & & \text{001} & - \\ & & & & & \end{array}$$

$$x \rightarrow 1$$

$$\bar{x} \rightarrow 0$$

a	b	c	f
0	0	0	0
1	0	1	1
0	1	0	1
1	1	0	0
0	0	1	1
1	0	0	0
1	1	1	1
0	1	1	0

Min terms are  $\bar{a}\bar{b}c$ ,  $\bar{a}bc$ ,  $a\bar{b}\bar{c}$ ,  $abc$ .

!

SOP :-  $a + bc + \bar{a}c$

→ Canonical SOP  $\equiv abc + \bar{a}bc$

→ CSOP means min term containing all the variables.

$$\therefore f(a, b, c) = \bar{a}\bar{b}c + \bar{a}b\bar{c} + a\bar{b}\bar{c} + ab\bar{c}$$

$\Sigma(1, 2, 4, 6)$

⑥ Canonical Product of Sums (CPOS) :-

→ A sum term which contains each of 'n' variables as factor either in complemented or un-complemented form is called a "max. term".

$$\bar{a} + b + c, a + \bar{b} + c, \bar{a} + \bar{b} + \bar{c}$$

→ A max. term gives the value '0' to exactly one combination of the variables.

→ The product of all max. terms of 'f' for which 'f' assumes 0 is called CPOS(f).

Conjunctive Normal Form (CNF).

a	b	c	f
0	0	0	0✓
1	0	1	1
2	0	1	0
3	0	1	0✓
4	1	0	0✓
5	1	0	1
6	1	1	0✓
7	1	1	1

$$f(a, b, c) = (a + b + c)(a + \bar{b} + \bar{c})$$

$$(\bar{a} + b + c)(\bar{a} + \bar{b} + c)$$

$$\overline{(a + b + c)} \quad \overline{(a + \bar{b} + \bar{c})} \quad \Pi(0, 3, 4, 6)$$

7 Examples of Canonical Forms :-

$\Sigma$  - min terms  
 $\Pi$  - max terms

a	b	c	f <sub>1</sub>	f <sub>2</sub>	f <sub>3</sub>
0	0	0	0	1	1
1	0	0	1	0	1
2	0	1	0	1	0
3	0	1	1	0	0
4	1	0	0	0	1
5	1	0	1	0	0
6	1	1	0	1	1
7	1	1	1	0	1

$$f_1 = \Sigma(2, 3, 5, 6, 7) - CSOP$$

$$f_1 = \pi(0, 1, 4) - CPoS$$

$$f_2 = \Sigma(0, 2, 4, 6)$$

$$= \pi(1, 3, 5, 7)$$

$$f_3 = \Theta\Sigma(0, 1, 6, 7)$$

$$= \pi(2, 3, 4, 5)$$

$$f(x_1, x_2, x_3) = xy + z' + xyz, \text{ CSOP?}$$

~~$x'y'z$~~   $x'y'z^{(3)} + x'yz^{(6)} + xyz^{(7)}$

~~$x'yz$~~   $x'yz^{(100)}(4)$

$010 \quad \vdash yz^{(010)}(2)$

$(y) \quad \vdash y'z^{(000)}(0)$

$\therefore \Sigma(3, 2, 6, 4, 0, 7)$

$\Rightarrow \Sigma(0, 2, 3, 4, 6, 7) \text{ then } \Pi?$

$\Rightarrow \Pi(1, 5)$

8 Functional properties:-

→ The canonical SOP & POS form a switching function is unique.

→ Two switching functions  $f_1(x_1, x_2, \dots, x_n)$  &  $f_2(x_1, x_2, \dots, x_n)$  are said to be logically


equivalent iff both functions have same value for each and every combination of  $(x_1, x_2, \dots, x_n)$ .

→ Two switching functions are equivalent if their canonical POS (or SOP) are identical.

a	b	$f_1$	$f_2$
0	0	0	0
0	1	0	0
1	0	1	1
1	1	1	1

logically

equivalent

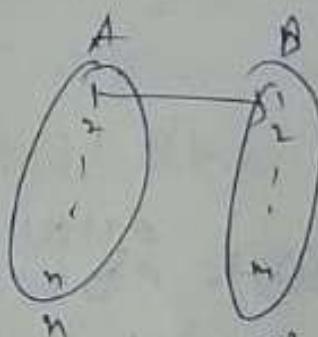

$1 \ 2 \ \dots \ n$

number for  $n^n$


⑨ No. of Functions:-

→ n - boolean variables are how many boolean functions are possible?  $2^{2^n}$

1	2	3	...	$n$	$f$
$2^2$	$\times 2$	$\times 2$	$\times \dots \times 2$		
$2^1$	$2^2$	$2^3$	$\dots$	$2^n$	$2^{2^n}$


$\rightarrow$  n-ternary var. Then how many boolean functions are possible?  $2^{3^n}$
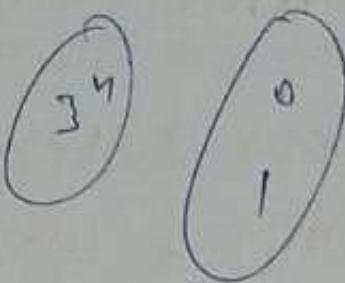
$$\begin{array}{c} 1 \ 2 \ 3 \ \dots \ n \\ \hline 3 \ 3 \ 3 \ \dots \ 3^n \end{array} \quad f$$



$\rightarrow$  n-k-ary variable Then how many many functions are possible?  $m^{k^n}$
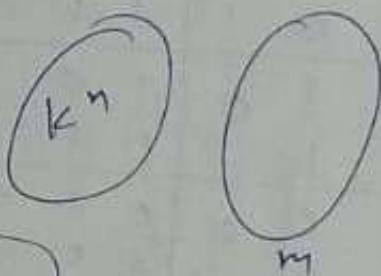
$$\begin{array}{c} 1 \ 2 \ \dots \ n \\ k \ k \ \dots \ k \end{array}$$



$f$   $\rightarrow$  no. of variables  
 $m^k$   $\rightarrow$  type of variables  
 $\rightarrow$  Type of function

$\rightarrow$  2 boolean var. Then how many boolean functions?

$$2^{2^2} = 2^4 = 16$$

$p$  — no. of vari.  
 $n$  — type of variables  
 $m$  — type of function

⑩ Counting the no. of function and  
neutral function:

→ How many boolean functions are possible  
with 3 variables such that there are  
exactly 3 minterms.

3 var → 8 combinations out of these 3 can be.

a	b	c		
(0) 0	0	0	1 0	- -
(1) 0	0	1	1 1	- -
(4) 0	1	0	1 0	- -
(1) 0	1	1	0 1	- -
(4) 1	0	0	0 1	- -
(5) 1	0	1	0 0	- -
(6) 1	1	0	0 0	- -
(7) 1	1	1	0 0	- -

at most 3' min terms

$$8C_3 + 8C_2 + 8C_1 + 8C_0$$

at least 3' min terms

$$8C_3 + 8C_4 + 8C_5 + 8C_6 + 8C_7 + 8C_8$$

=  
K-var then  $2^k$  combinations possible, minimum  
terms need then  $\boxed{2^K C_m}$

if ternary,  $\boxed{3^k C_n}$

→ Minteral function means, The no. of min terms is equal to no. of max terms.

A	B	$\Delta$	B	$\bar{A}$	$\Theta$	$\oplus$	$\bar{B}$
0	0	0	0	1	1	0	1
0	1	0	1	1	0	1	0
1	0	1	0	0	0	1	1
1	1	1	1	0	1	0	0

for 2 vars there 4 combinations

for two minterms twin  $4C_2$


n' variables then no. of m's  $2^n C$   
 $(2^n)_2$

$$\Rightarrow 2^n C$$


$$2^{n-1}$$
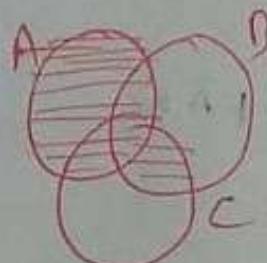
## II Venn Diagram Representation:

Find the boolean function that the following Venn diagram represents




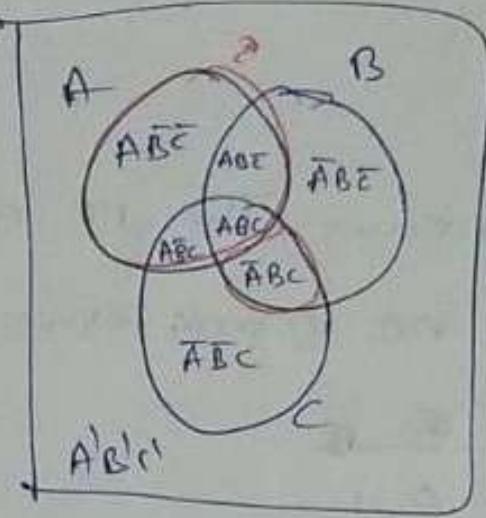- a)  $A + A'B'C$  :
- b)  $A + BC$  ✓  $A + A'B'C$   $\cancel{(A+A')(A+BC)}$   
 $= 1(A+BC)$   
 $= A+BC$
- c)  $A + ABC$
- d)  $A \oplus BC$





$$A + \overline{ABC}$$
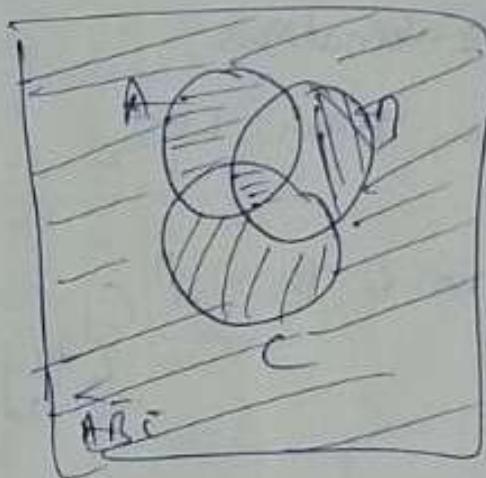
$$\cancel{(A+A)} (A+\overline{BC}) = A+\overline{BC}$$


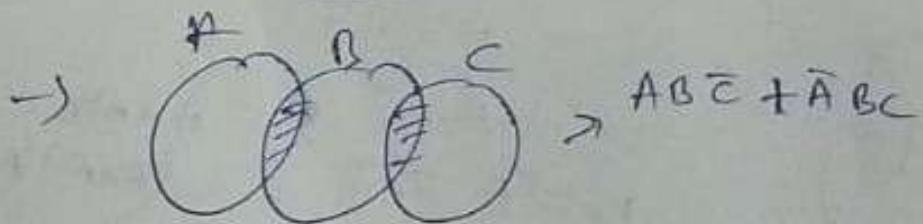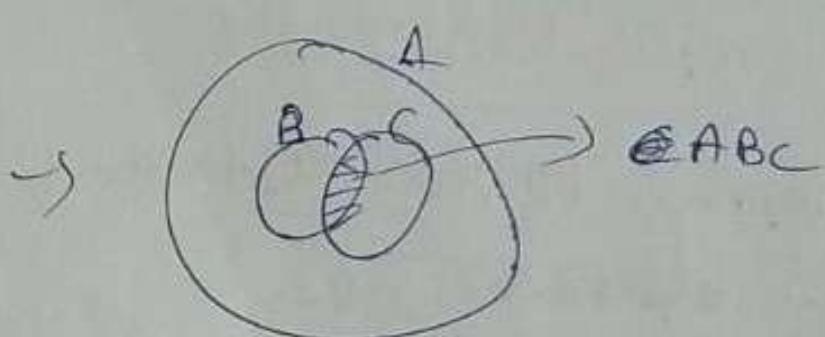
$$\overline{A}\overline{B}\overline{C} + A\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}\overline{B}C + A\overline{B}C$$



Forward path:- Any path starting from  $\oplus p$  and ending at  $\oplus p$  without performing a cycle.

Validity:- It means no path should contain a variable in both true and complemented form.

$$AAB'C' + \underline{AABC} + AABA + \underline{ABC} + ABA + \boxed{AC'D} + ACD$$

With validity rule

$$AAB'C' + ABC(A+1) + AABA + ABA + ACD$$

$$AAB'C' + ABC + ABA + ABA + AC'D$$

→ Simplify this.

(13) Nested function

In the following simultaneous boolean expression, what are the values of  $w, x, y, z$ ?

i)  $x+y+z=1$  a)  $\begin{smallmatrix} w & y \\ 0 & 0 \\ 0 & 0 \end{smallmatrix}$

ii)  $xz + w\bar{z} = 0$  b)  $1101$

iii)  $xw\bar{z} + y\bar{z} = 1$  c)  $0101$

d)  $1000$

Substitute option c, it satisfies i, ii & iii.

$$f(A, B) = A+B \text{ then find } f(f(x+y, z), z)$$


$$f(x+y, z) = (x+y) + z = xy + z = x + y$$

$$f(f(x+y, z), z) = f(x+y, z) = (x+y) + z = \underline{x+y} + z$$

(10) Minimum no. of gates required for EX-OR


EX-NOR :-

EX-OR  
using NAND

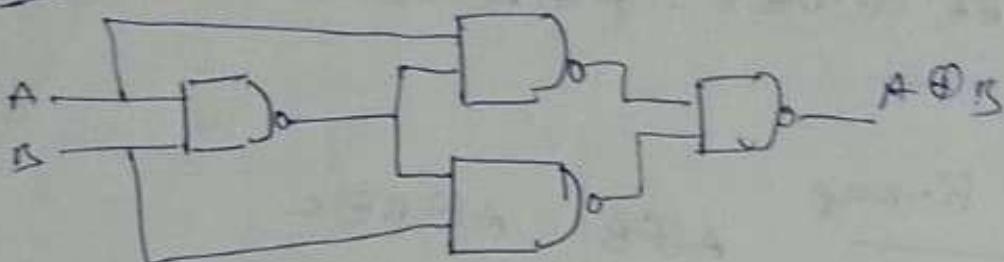

Min. no. of NAND gates are  $\pm 4$


using NOR

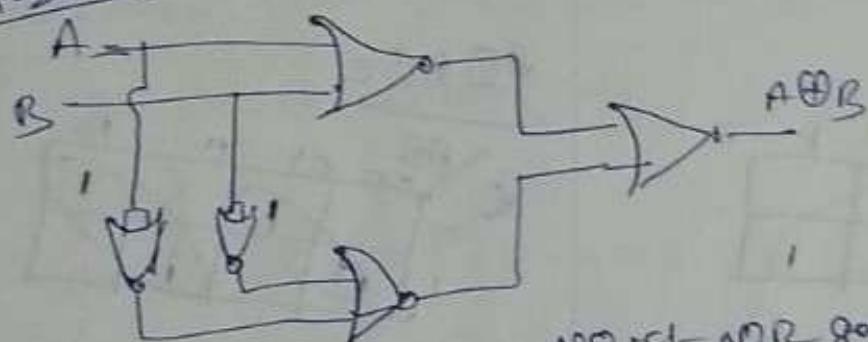

No. of NOR gates = 5


EX-NOR

using NOR

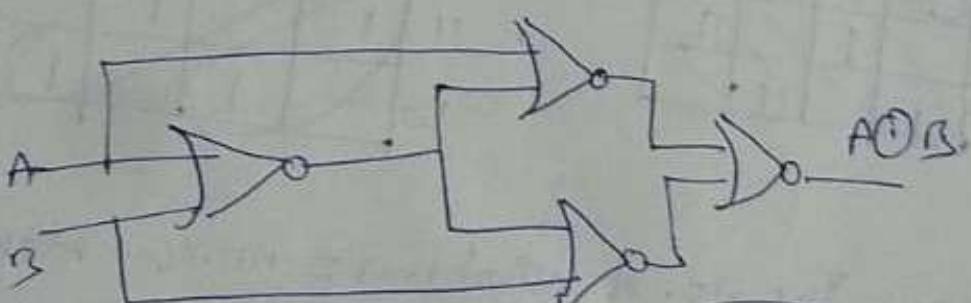

4 gates

## Using NAND

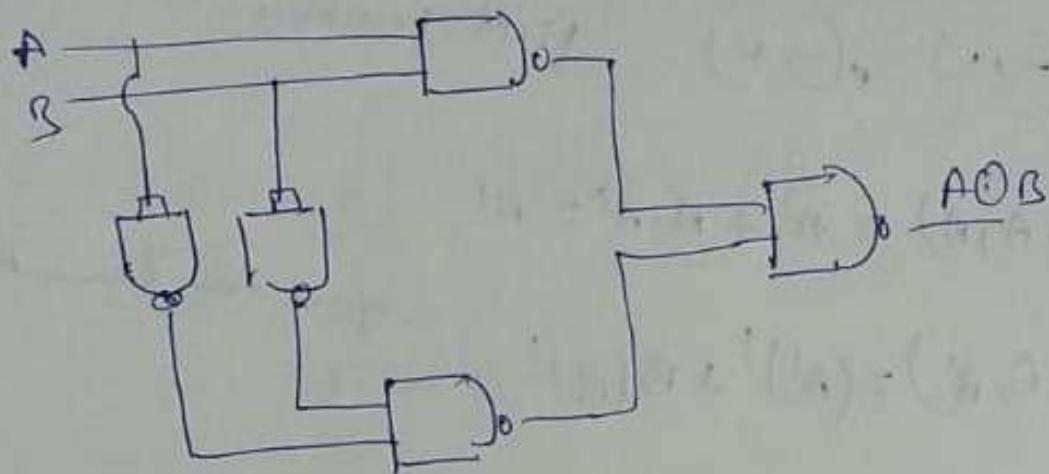

Min. no. of NAND gates = 5

	NAND	NOR
Ex-or	4	5
Ex-Nor	5	4

### (20) Functionally Complete operations:

A set of operations is said to be functionally complete (or) universal iff every switching function can be expressed by means of operations in it.

$$\rightarrow \{+, \cdot, \bar{\cdot}\}$$

$$\{+, -\}$$

$\{ \cdot, - \}$  are functionally complete.

→ Functionally complete means, it is able to derive at least two operations.

$$(-, \circ) \text{ or } (-, +)$$

$$(2) f(A, B, C) = A^I + BC^I$$

$$(-, \cdot) \rightarrow (+)$$

first you have to derive one

$$\text{Ex: } f(A, A, A) = A^I + A \cdot A^I = A^I$$

$$f(A, B, B) = (A^I)^I + B(B^I)^I$$

you can derive one

$$(2) f(A, B) = \bar{A} + B = A + B = \rightarrow FC$$

$$f(A, A) = \bar{A} + A = 1$$

$$f(B, B) = \bar{B} + B = 1$$

(+1) ✓

$$f(A, 0) = \bar{A} + 0 = \bar{A}$$


So, it takes the help from 'd'

$$f(f(A, 0), B)$$

$$= f(\bar{A}, B)$$

$$= A + B \rightarrow +$$

So, partially FC.

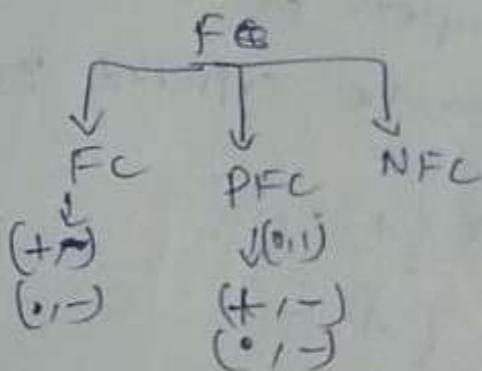

$$f(A, B) = \bar{A}B$$

$$f(A, A) = \bar{A} \cdot A = 0 \quad (-, \cdot)$$

$$f(B, B) = \bar{B} \cdot B = 0$$

$$\Rightarrow f(A, 0) = \bar{A} \cdot 0 = 0$$

$$f(A, 1) = \bar{A} \cdot 1 = \bar{A}$$

∴ with the help of '1' it is complement.

$$f(f(\underbrace{A, 1}_{A'}), B) = (A')' B = AB$$

∴ Partially FC.

(24)

$$f(A, B, C) = AB + BC + CA$$

$$f(A, A, A) = A$$

Prime complement is absent in expression,  
can't derive  
∴ NOT FC.

(25)

$$f(x, y) = \bar{x}y + x\bar{y}$$

$$f(x, x) = \bar{x} \cdot x + x \cdot \bar{x} = 0; f(y, y) = 0$$

$$f(x, y) = \bar{x} \cdot 1 + x\bar{1} = \bar{x} + 0 = \bar{x} \quad \text{complement by derived.}$$

$$f(f(\underbrace{x, 1}_{x}), y) = (\bar{x})' y + \bar{x}\bar{y}$$
$$= xy + \bar{x}\bar{y}$$

$$f(x, \bar{y}) = x\bar{y} + \bar{x}y$$

$$f(\bar{x}, y) = \bar{x}\bar{y} + x\bar{y}$$

$$f(f(x, \bar{x})) =$$

$$f(f(y, \bar{y})) =$$

| Here we can't derive  
xy or x $\bar{y}$

so NFC

Q8 Any Boolean function can be defined with  
combinations of the following operations?

a)  $\oplus$ , NOT

$$\cancel{\oplus} \quad \oplus, \text{ NOT}$$

c)  $\oplus, 1, \text{ NOT}$

d)  $\oplus, 1, \text{ NOT}$

( $\oplus, 1$ ) gives  $\rightarrow$  one  
 $\oplus(x,y) = \bar{x}y + xy$

$$f(x,y) = xy + \bar{x}y \quad f(x,y) = \cancel{x} \cdot 1 + \cancel{x} \cdot 0$$

$$f(x,x) = xx + \bar{x}\bar{x} = x + \bar{x} = 1$$

$$f(0,y) = 1 \quad \} \text{No complement}$$

$$f(x,1) = x \cdot 1 + \bar{x} \cdot 1 = x + 0 = x$$

$$f(y,1) = y \quad \} \text{no}$$

$$\cancel{\oplus} \quad f(x,0) = x0 + \bar{x}1 = \bar{x}$$

By using  $(\oplus, 0)$  we can find complement.

$$f(x,y) = xy + (\bar{x})^1 y^1 = xy + \bar{x}y$$

$$f(x^1 y^1) = \cancel{\bar{x} + \bar{y}} = x^1 y^1 + x^1 y^1$$

$$f(x^1 y^1) = x^1 y^1 + xy$$

NFC.

By observing  $\oplus$  then  $\oplus$  last problem,

$$x \oplus y = x^1 \oplus y = x \oplus y^1 = x^1 \oplus y^1$$

$$x \oplus y = x^1 \oplus y = x \oplus y^1 = x^1 \oplus y^1$$

## Q27 Self-Dual Functions:-

$\leftrightarrow$   
 $\leftrightarrow$

$$\rightarrow f(A, B, C) = AB + BC + CA$$

$$f_2(A, B, C) = (A+B)(B+C)(C+A)$$

$$\Rightarrow f(A, B, C) = AB(C+C') + (A+A')BC + C(B+B')A$$

$$= ABC + ABC' + A'BC + A'B'C$$

|      |      |      |  
 A'BC    A'BC'    ABC'    A'B'C'

Mutual  
Exclusive  
terms

→ A boolean function is self-dual if

i) It is neutral (no. of minterms = no. of max terms) ( $2^{n-1} = 2^{n-1}$ )

ii) The function does not contain two mutually exclusive terms

$$ABC \rightarrow A'BC'$$

$$A'BC' - \underline{ABC}$$

## Q28 No. of Self-Dual functions:-

A	B	C
0	0	0
1	0	1
2	1	0
3	1	1
4	0	0
5	0	1
6	1	0
7	1	1

(1,7) (1,6), (2,5) (3,4) all  
mutually exclusive  
terms

0-7

1-6

2-5

3-4

(minterm, Mutual Exclusive term)

$$(0,1,2) \quad (1,6) \quad (2,5) \quad (3,4)$$

$$f = 2 \times 2 \times 2 \times 2$$

$$\Sigma(0,1,2,3)$$

No. of self-dual functions  $= 2^4 = 16$

$n$  variables,  $2^n$  combinations

$$\text{no. of pairs} = 2^{n-1}$$

$$2 \times 2 \times 2 \times \dots \times 2^{n-1}$$


$$\therefore = 2^{2^{n-1}}$$

No. of self-dual functions ~~are~~ with  $n$  var

$$= 2^{2^{n-1}}$$

No. of neutral functions  $= 2^n C_{(N)}$

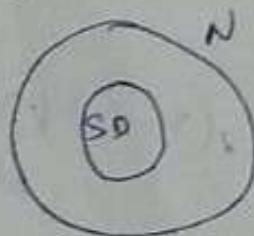No. of self-dual functions  $= 2^{2^{n-1}}$



$\equiv$

$$\Sigma(0,1,2,3) \rightarrow N$$

— SD — X

(2a) Self-Dual functions are closed under

Complementation:-

which of the following functions are self-dual.

$$f(A, B, C) = \Sigma(0, 2, 3) \times 1 \text{ is closed}$$

$$f(A, B, C) = \Sigma(1, 1, 6A) \times (\underline{1}, \underline{6})$$

$$f(A, B, C) = \Sigma(0, 1, 2, 4) \checkmark$$

$$f(A, B, C) = \Sigma(3, 5, 6, 7) \checkmark$$

$$\begin{matrix} 0 & 7 \\ 1 & 6 \\ 2 & 5 \\ 3 & 4 \end{matrix} \quad \begin{matrix} (0, 2)(1, 6)(2, 5)(3, 4) \\ (0, 1, 2, 3) \end{matrix}$$

	A	B	C	f	g
0				1	0
1				1	0
2				1	0
3				1	0
4				0	1
5				0	1
6				0	1
7				0	1

complement also s.d.

-ve LS

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

A  $\leftrightarrow$  L

1  $\leftrightarrow$  0

0 — H — 1  
(ne)

0 or 1  
AND

∴ Everything is dual.

→ PLS & NLS are dual to each other

gate logic H as O/P  
and O/P L, L as I/P  
or O/P HI

		A	F
true	(not)	H	L
A		L	H
1	0		
0	1		

+ve LS

A	F
0	1
1	0

→ By default we follow the Positive Logic System (PLS) everywhere.

Q) Let  $x_1 \oplus x_2 \oplus x_3 \oplus x_4 = 0$ ,  $x_1, x_2, x_3, x_4$  are Boolean variables.  $\oplus$  is XOR operation, which one of the following must always be True?

Sum of given no's = 0

A)  $x_1 x_2 x_3 x_4 = 0$

0 - 1's

B)  $x_1 x_2 + x_3 = 0$

2 - 1's

C)  $\bar{x}_1 \oplus \bar{x}_3 = \bar{x}_2 \oplus \bar{x}_4$

4 - 1's

D)  $x_1 + x_2 + x_3 + x_4 = 0$

( $\oplus$ ) is mod 2 sum

$$x_1 \oplus x_2 \oplus x_3 \oplus x_4 = 0 \rightarrow \text{D}$$

all are 1's then @ B is 00

X A) 1.1.1.1. = 0d

B) 1.1+1 = 0d

D) 1+1+1+1 = 0d

C)

$$\bar{x}_1 \oplus \bar{x}_3 = x_1 \oplus x_3 = 1 \oplus 1 = 0$$

$$x_1 \oplus x_3 = x_2 \oplus x_4$$

$$\bar{x}_2 \oplus \bar{x}_4 = x_2 \oplus x_4 = 1 \oplus 1 = 0$$

0 0 ✓  
0 1 ✓  
1 0 ✓  
1 1 ✓

all are satisfied by C

$$\begin{array}{r} 0 \oplus 0 = 0 \\ 0 \oplus 1 = 1 \\ 1 \oplus 1 = 0 \\ 1 \oplus 0 = 1 \\ 0 \oplus 0 = 0 \\ 0 \oplus 1 = 1 \\ 1 \oplus 1 = 0 \\ 1 \oplus 0 = 1 \end{array}$$

③ 06) Consider no. B represented in 4-bit

gray code ~~represented~~ let  $b_3 b_2 b_1 b_0$  be the

gray code representation of a number

'n' and let  $g_3 g_2 g_1 g_0$  be the gray code of

$(n+1) \bmod 16$  value of the no. which one of

the following functions is correct?

$$a) g_3(h_3 h_2 h_1 h_0) = \Sigma(12, 13, 6, 10, 13, 14, 15)$$

$$g_3(h_3 h_2 h_1 h_0) = \Sigma(4, 9, 10, 11, 12, 13, 14, 15)$$

$$g_2(h_3 h_2 h_1 h_0) = \Sigma(2, 4, 5, 6, 7, 12, 13, 15)$$

$$d) g_3(h_3 h_2 h_1 h_0) = \Sigma(0, 1, 6, 7, 10, 11, 12, 13)$$

$h_3 \ h_2 \ h_1 \ h_0$	$g_3 \ g_2 \ g_1 \ g_0$	$(n+1) \bmod 16$
0	1	
1	2	
2	3	
3		
4		
5		
6	0	
7		
8		
9		
10		
11		
12		
13		
14		
15	0	

$h_3 \ h_2 \ h_1 \ h_0$	$g_3 \ g_2 \ g_1 \ g_0$
0 - 0 0 0 0	0 0 0 1
1 - 0 0 0 1	0 0 1 1
2 - 0 0 1 1	0 0 0 0
3 - 0 0 1 0	0 1 1 0
4 - 0 1 1 0	0 1 1 1
5 - 0 1 1 1	0 1 0 1
6 - 0 1 0 1	0 1 0 0
7 - 0 1 0 0	1 1 0 0
8 - 1 1 0 0	1 1 0 1
9 - 1 1 0 1	1 1 1 1
10 - 1 1 1 1	1 1 1 0
11 - 1 1 1 0	1 0 1 0
12 - 1 0 1 0	1 0 1 1
13 - 1 0 1 1	1 0 0 1
14 - 1 0 0 1	1 0 0 0
15 - 1 0 0 0	0 0 0 0

$$g_2(h_3, h_2, \cancel{h_1}, h_0) = \Sigma(0100, 1100, 1101, 1111, 1110, 1010, 1011, 1001)$$

$$= \Sigma(4, 12, 13, 15, 14, 10, 11, 9)$$

$$g_2(h_3, h_2, h_1, h_0) = \cancel{\Sigma(0100)}, \Sigma(2, 6, 7, 5, 4, 12, 13, 15)$$

suffices 0100  
 $h_3, h_2, h_1, h_0$

	Identity	Commutative	Associativity
NAND	X	✓	X
NOT	X	✓	X
EXOR	X	✓	✓
EXNOR	X	✓	✓

$$\begin{array}{ccc} \textcircled{1} & \frac{0}{1} & \Rightarrow \textcircled{2} \begin{pmatrix} 0 \\ 0 \\ 1 \\ 0 \end{pmatrix} \\ \rightarrow & & \textcircled{3} \begin{pmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 1 \\ 1 \\ 0 \\ 1 \end{pmatrix} \end{array}$$

## ② Minimization

### ③ K-map Introduction:

- Minimization is very difficult using algebraic formulas, so K-map is produced.
- The algebraic procedure of combining narrow terms and applying to themselves becomes very tedious as the no. of variables increased.
- The Map method provides a systematic method for combining terms and deriving minimal expression.
- A K-map is a modified form of a truth table in which the arrangement of combinations is particularly convenient for minimization.
- Every 'n' variable map consists of "n" cells (squares), representing all possible combination of variables.

3-var map			
x <sub>1</sub>	0	01	11
x <sub>2</sub>	0	0 1	1 2
x <sub>3</sub>	0	3	7
1	1	5	9

4-var Map				
x <sub>1</sub>	x <sub>2</sub>	x <sub>3</sub>	x <sub>4</sub>	
00	00	00	00	0
00	00	01	01	1
00	01	10	10	2
01	00	11	11	3
01	01	10	10	4
10	00	01	11	5
10	01	10	01	6
11	00	11	00	7
11	01	00	11	8
10	10	00	01	9
10	11	01	10	10

- ① → The binary value associated with a particular combination is entered in the corresponding cell.
- ② → Cycle code is used in the combination as column and row heading.
- ③ → Because of these codes, two cells which have a common side correspond to combinations that differ by the value of just a single variable.
- ④ → These two cells play a major role in simplification process. Because they can be combined by means of rule  $A \oplus A' = 1$

$$\text{① } \Sigma(\bar{x}, \bar{y}) = \bar{x}y_3 + xy_2$$

3 variable

$\bar{x}\bar{y}$	$\bar{x}y$	$x\bar{y}$	$xy$
00	01	11	10
1			

- ② Cycle code means 00 → 01 → 11 → 10  
 00 → 01 → 11 → 10  
 no's 1 bit in change.  
 blw any two 6.3 junction

3 variable

$\bar{x}\bar{y}$	$\bar{x}y$	$x\bar{y}$	$xy$
00	01	11	10
1			

$\bar{x}y_3$        $xy_2$   
 change.

$$④ \underline{yz(x+x)} = yz$$

## ⑤ K-map Simplification:-





Simplification and Minimization of Functions using K-maps :-



- ① A collection of "2<sup>m</sup>" cells, each adjacent to 'm' cells of collection is called a Subcube, and the Subcube is said to cover these cells.
- ② Each Subcube can be expressed by a product containing "n-m" literals where ~~n~~ 'n' is no. of variables in which function depends.
- ③ Any cell may be included in as many Subcubes as ~~des~~ desired.

$$① 2^1 - 1$$

$$2^2 = 2$$

~~2^3 = 3~~

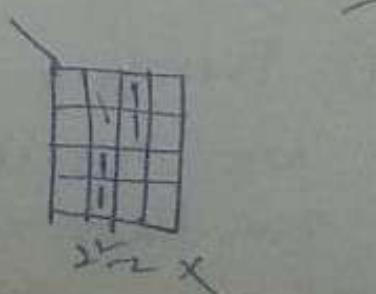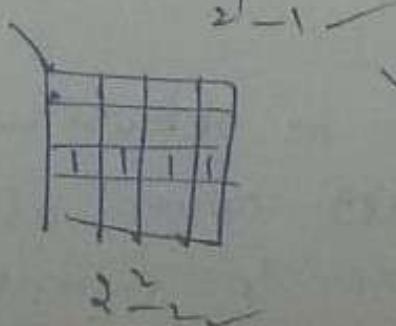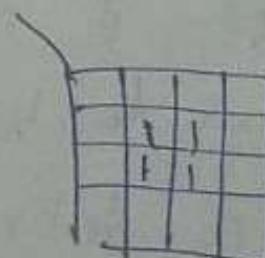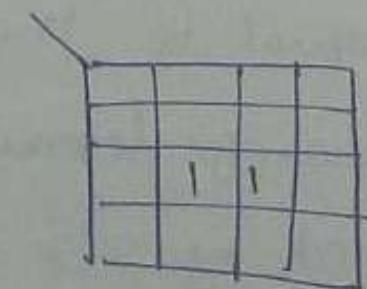

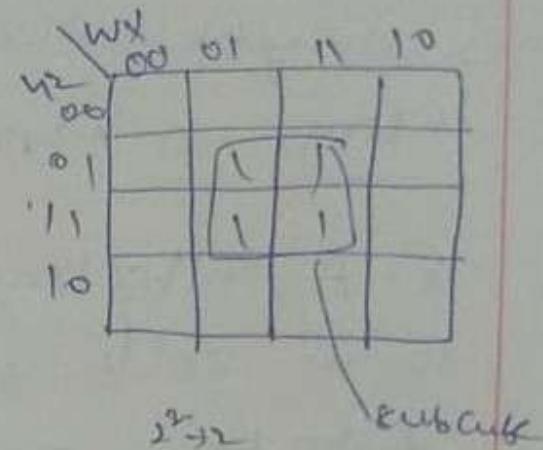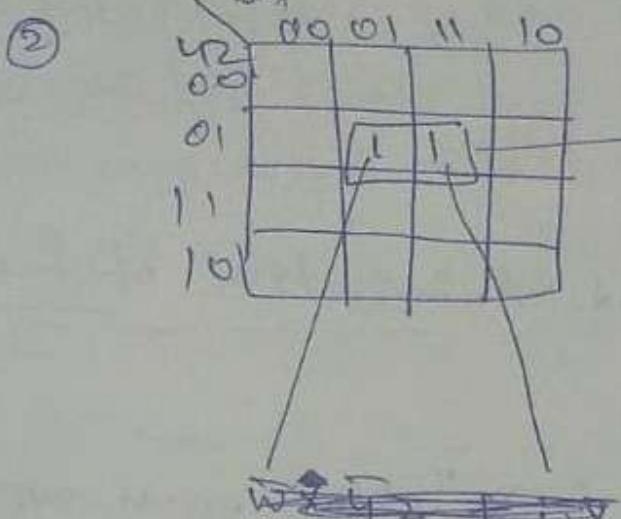

$$\bar{w} \times \bar{y}z + w \times \bar{y}z$$

$$(w + \bar{w}) \times \bar{y}z$$

$$x \bar{y}z$$


$$\left(\frac{w}{w}\right) \times \left(\frac{\bar{y}}{y}\right) z = xz$$

$$\textcircled{2} \quad n-m > m-2 = 2$$

Morphing:-

- ① A function 'f' can be expressed as sum of those product terms which corresponds to subcubes necessary to cover all its '1' cells.
- ② The no. of product terms in the expression for 'f' is equal to the no. of subcubes, while the no. of literals in each term is determined by size of corresponding subcubes.
- ③ Therefore to obtain minimal expression, we must cover all '1' cells with smallest no. of subcubes such that each


8 subcubes as long as possible.

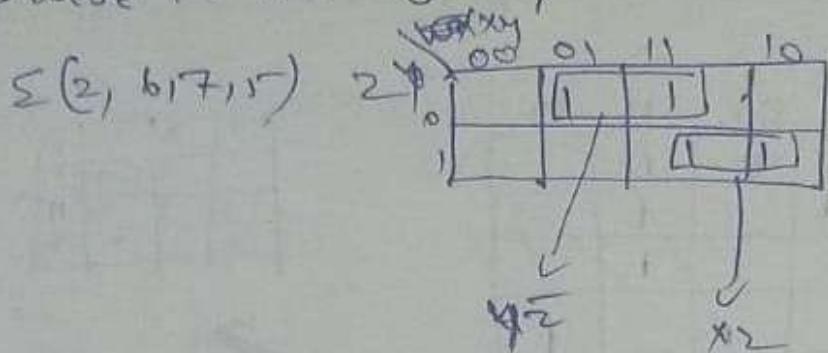

$$\therefore \Sigma(2, 6, 7, 15) = y\bar{z} + x\bar{z}$$


③ Examples on K-map:-

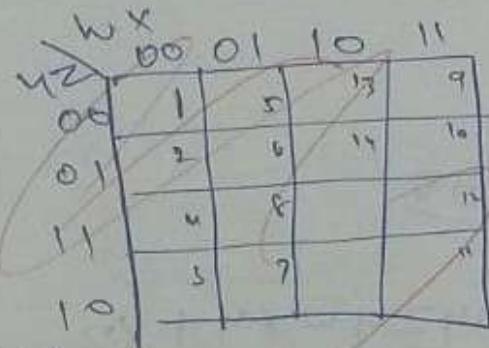① Minimize  $f(w, x, y, z) = \Sigma(0, 4, 6, 7, 8, 9, 15)$



$$w \times 4^2$$

00	01	10	11
00	01	10	11
00	01	10	11
00	01	10	11

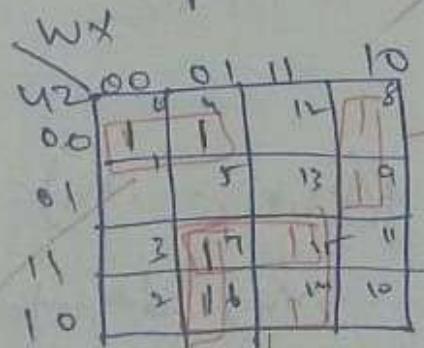



3 subcubes  
3 terms

$$wx\bar{y}$$

$$w\bar{y}\bar{z}$$


$$\therefore f(w, x, y, z) = w\bar{y}\bar{z} + w\bar{y}z + xy$$
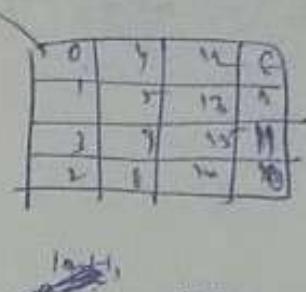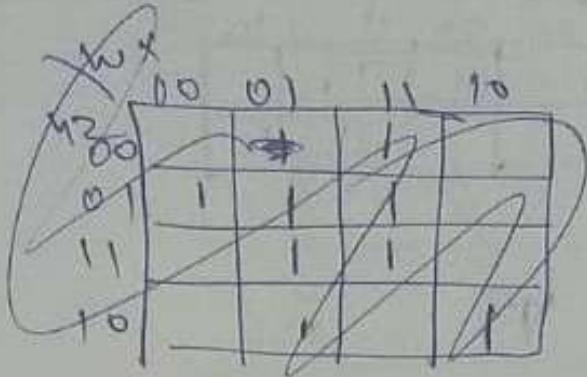
$$⑧ f(w, x, y, z) = \sum(1, 5, 6, 7, 11, 12, 13, 15)$$



$f = \sum(1, 5, 6, 7, 11, 12, 13, 15)$

$f = \sum(1, 5, 6, 7, 11, 12, 13, 15)$

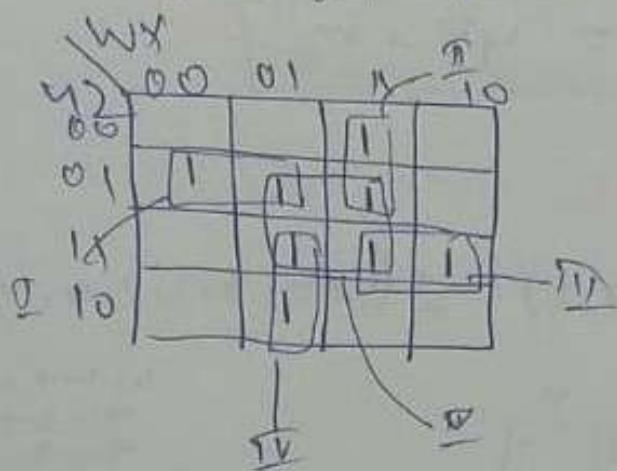

$\text{I} + \text{II} + \text{III} + \text{IV} + \text{V}$

$$\bar{w}\bar{y}z + w\bar{x}\bar{y} + w\bar{y}z + \bar{w}x\bar{y} + \bar{w}xz$$

6

Covering Functions:-

→ A switching function  $f(x_1, x_2, \dots, x_n)$  is said to cover  $g(x_1, x_2, \dots, x_n)$ , denoted by "f" is superset of "g" if 'f' attains true value whenever 'g' does.

Minterm	g	f
0	0	1
1	1	1
2	0	0
3	0	0

$f = \{0, 1, 3\}$   $g = \{1, 3\}$   
min terms

Note:- If "f" covers "g" and at the same time "g" covers "f", then "f" and "g" are equivalent.

	g	f	
0	0	0,1	2
1	1	1	x
2	0	0,1	2
3	0	0,1	x
			2

=g

→ If 'g' has 'x' min terms and 'g' is a function of 'n' variables, then no. of covering functions for 'g'  $\rightarrow \frac{(2^n - x)}{2}$ .

Ex:-

$$f(w, x, y, z) = wu + yz$$

~~wxyz~~  $f(w, x, y, z) \rightarrow 2^4 = 16$

$$wu \rightarrow \overbrace{11--}^{wxyz} = 1100 + 1101 + 1110 + 1111$$

$$yz \rightarrow \overbrace{--11}^{wxyz} = 0011 + 0111 + 1011 + \cancel{1111}$$

~~Repeated~~

$(wu + yz)$  has 9 minterms

$$\Rightarrow 2^4 - 9 = 2^4 - 9 = 16 - 9 = 7$$

$$\overbrace{=}^{=2^4}$$


## ⑦ Implicants and Prime Implicants:-

→ If 'f' covers 'g', then 'g' is said to imply 'f'. This is denoted by  $g \rightarrow f$   
 i.e. from 'f' we can derive 'g'.

$$\text{Ex: } f(a, b, c) = ab + c$$

$a$	$b$	$c$	$ab$	$c$	$ab + c$
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	0	0	0
0	1	1	0	1	1
1	0	0	0	0	0
1	0	1	0	1	1
1	1	0	1	0	1
1	1	1	1	1	1

$f$  covers  $f_1, f_2$

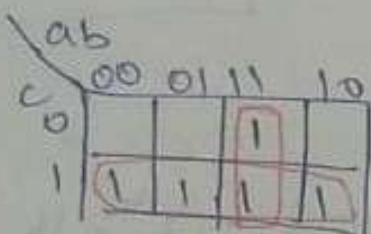

every subcube is an implicant

Prime Implicant:- An implicant 'p' of a function 'f' is said to be prime implicant if

- ① P is a Product term (i.e. subcube)
- ② deletion of any literal from 'p' results in a new product which is not covered by  $f'$  - (i.e., A subcube cannot be part of any other subcube).




## (8) Essential Prime Implicants:


→ A prime implicant 'P' of a function 'f' is said to be an essential prime implicant, if it covers atleast one minterm of 'f' which is not covered by any other prime implicants.

Simplicant → Sub cube.

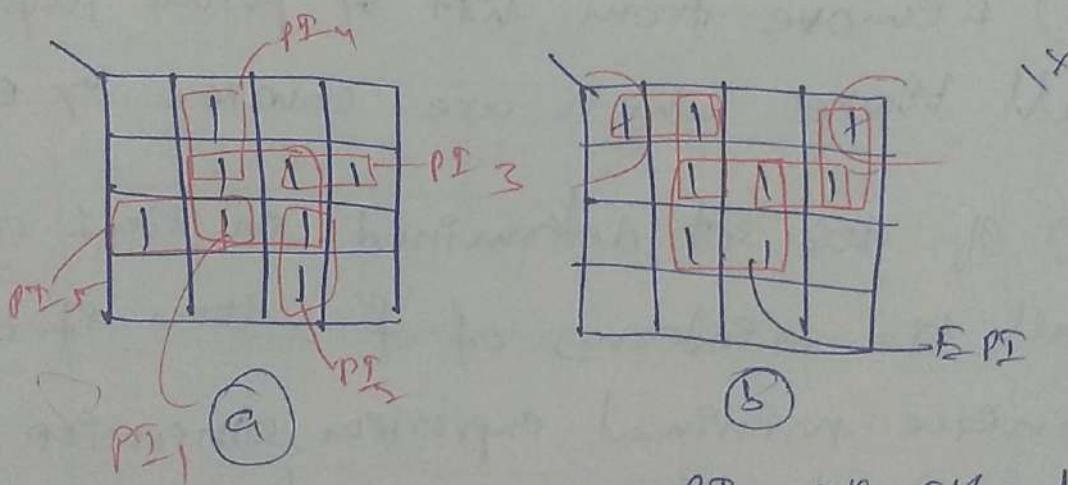Prime implicants - biggest subcube which is not a essential simplicants - part of other subcubes




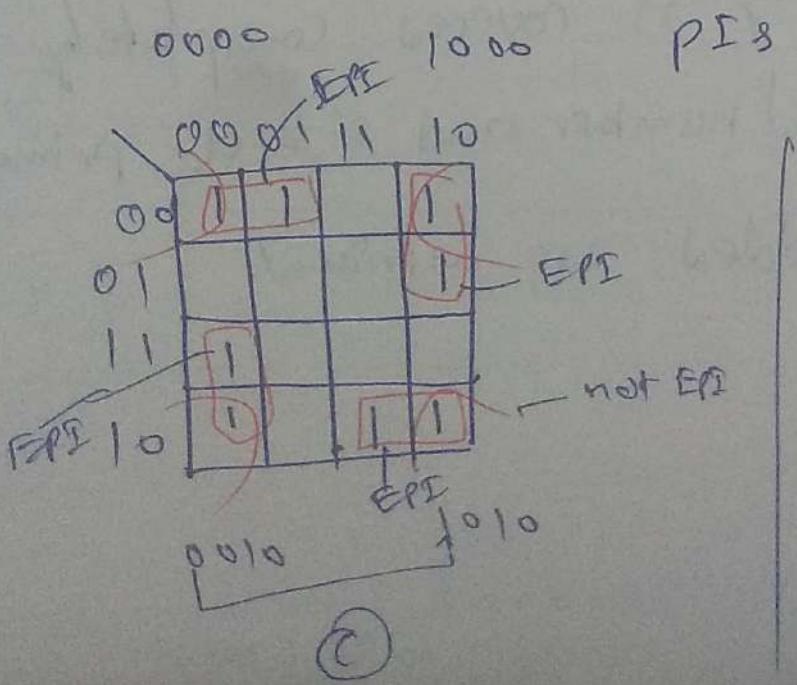PI<sub>1</sub>, PI<sub>2</sub>, PI<sub>3</sub>, PI<sub>4</sub>, EPI are essential



no EPIs here



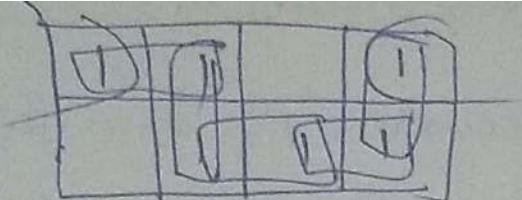


$\rightarrow \textcircled{1} \wedge \textcircled{2}$  are cyclic k-maps.
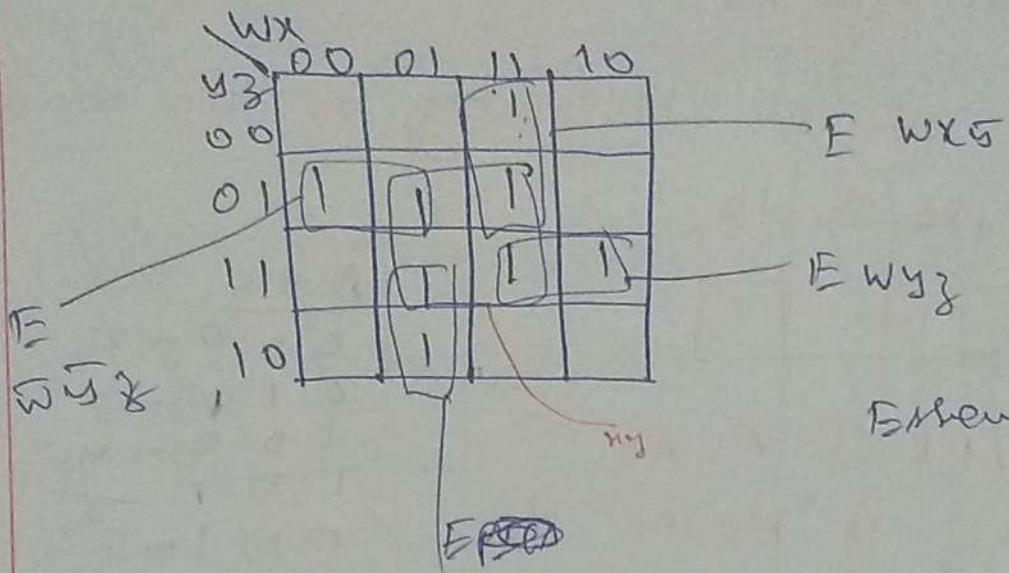
### (9) Procedure for obtaining Minimal SOP:-

- ① Determine all essential prime implicants and include them in the minimal SOP.
- ② Remove from list of prime implicants all those which are covered by EPIs.
- ③ If the set determined in Step I covers all the minterms of ' $f$ ', then it is unique minimal expression. otherwise select the additional prime implicants so that the function ' $f$ ' is covered completely and the total number and size of prime implicants added are minimal.

$$\text{Ex: } S(1, 5, 6, 7, 11, 12, 13, 15)$$



Essential prime implicant

$\bar{W}xy$

$$= \bar{W}y\bar{z} + \bar{W}xy + Wyz + Wx\bar{y}$$

Prime implicant chart:

	1	5	6	7	11	12	13	15
$\bar{W}y\bar{z}$	1	1						
$Wx\bar{y}$						1	1	
<del><math>Wyz</math></del>								1
$\bar{W}xy$			1	1				
$x\bar{z}$			1		1		1	1

$$(x_1, x_2, x_3, x_4)$$

$$\bar{W}y\bar{z} \Rightarrow 115$$

$$\bar{W}xy \Rightarrow 617$$

$$Wyz \Rightarrow 1115$$

$$Wx\bar{y} \Rightarrow 1113$$

⑩ Minimal SOP Exp:

which of the following PI are essential?

	AB 00	01	11	10
C 0	0	1	1	1
C 1	1	1	1	1

A 0	B 1	C 0	-2
0	1	1	-3
1	0	0	-4
1	0	1	-5
0	0	1	-1

- (a)  $B'C, A'B$  (b)  $A'C, A'B$   
~~(c)  $A'B, AB'$~~  (d)  $A'B, AB', B'C$

SL

	AB 00	01	11	10
C 0	0	1	1	1
C 1	1	0	0	0

$\bar{A}B$

$$A\bar{B} + \bar{A}B + \bar{A}C$$

$$A\bar{B} + \bar{A}B + \bar{B}C$$

2 minimal Expr.

	1	2	3	4	5
$A'B$			①	1	
$A\bar{B}$					① 1
$A'C$	1			1	
$B'C$	1	1			1

$$A'^0 = 2, 3$$

$$A^0 = 4, 5$$

$$(1, F, X, Y, Z)$$

(11) Min Pos :-

$$f(w, x, y, z) = \Sigma(5, 6, 9, 11, 10) \quad | \quad f(w, x, y, z) = \pi(5, 6, 9, 11, 10)$$

	wx	00	01	11	10	
yz	00	0	0	0	0	$y+z$
00	0	1	0	1	1	
01	1	0	1	0	1	
11	0	0	0	0	0	
10	0	1	0	1	0	

SOP - 1's

POS's = 0's

$(w+x)$

$$\Rightarrow \text{POS} \quad (y+z)(\bar{y}+\bar{z})(\bar{w}+\bar{x})(w+x)$$

	wx	00	01	11	10	
yz	00	1	1	1	1	$\bar{y}\bar{z}$
01	1	0	1	1	0	
11	1	1	1	1	1	
10	1	0	1	0	0	

$$\text{SOP} = \bar{w}\bar{x} + w\bar{x} + y\bar{z} + \bar{y}z$$

$$\begin{aligned} \text{POS} &= (\bar{w} + \bar{x} + y + z) \cdot (\bar{w} + x + y + z) \\ &\quad (w + x + \bar{y} + z) \cdot (\bar{w} + x + \bar{y} + z) \end{aligned}$$

SOP

$$\bar{w}x\bar{y}z + w\bar{x}\bar{y}z + \bar{w}x\bar{y}z + \bar{w}\bar{x}yz$$

(12) Examples on min pos:-

Find the no. of literals in Min. POS and SOP

$$\text{for } f(w, x, y, z) = \pi(1, 5, 6, 7, 11, 12, 13, 15).$$

	wx	00	01	11	10	
yz	00	1	1	0	1	
00	1	0	0	0	1	
01	0	1	0	0	0	
11	1	0	0	0	0	
10	0	1	0	1	0	


$$\begin{aligned} \text{POS} &= (\bar{w} + x + y) \cdot (\bar{w} + \bar{y} + \bar{z}) \cdot \\ &\quad (w + \bar{x} + \bar{y}) \cdot (w + y + z) \end{aligned} \quad (12)$$

$$\text{SOP} = w\bar{x}\bar{y} + w\bar{y}z + \bar{w}\bar{y}z + \bar{w}\bar{y}z \quad (12)$$

12 literal in both POS, SOP

now need a same count every time

B) Introduction to Don't care:

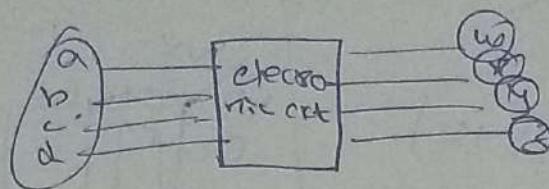

BCD  $\rightarrow$  Excess-3

$$\begin{array}{l} 0 \rightarrow 3 \\ 1 \rightarrow 4 \\ 2 \rightarrow 5 \\ 3 \rightarrow 6 \\ 4 \rightarrow 7 \\ 5 \rightarrow 8 \\ 6 \rightarrow 9 \\ 7 \rightarrow 10 \\ 8 \rightarrow 11 \\ 9 \rightarrow 12 \end{array}$$

$$\overline{\text{BCD}} = 0 \rightarrow q$$

	a b c d	w x y z
0	0 0 0 0	0 0 1 1
1	0 0 0 1	0 1 0 0
2	0 0 1 0	0 1 0 1
3	0 0 1 1	0 1 1 0
4	0 1 0 0	0 1 1 1
5	0 1 0 1	1 0 0 0
6	0 1 1 0	1 0 0 1
7	0 1 1 1	1 0 1 0
8	1 0 0 0	1 0 1 1
9	1 0 0 1	1 1 0 0
10	q q q q	
15		

## Dont care combinations :-

- A function is said to be completely specified if it is given 0 or 1 for every combination of variables. There exists some functions which are not completely specified.
- Combinations for which the value of a function is not specified are called 'don't care combinations'.
- The value of a function for such combination is denoted by ' $\phi$ ' or 'd'.
- Since each don't care combination represents two values ~~either~~ {0, 1}, an ~~in~~ n-variable completely specified function containing k-don't care combinations corresponds to a class of  $2^k$  distinct functions.
- Our task is to choose a function having minimal representation out of those  $2^k$  functions.
- We could assign a '0' or '1' to a don't care combination in such a way to increase (or) decrease size of a sub cube.


Ex:-

a	b	f	f <sub>1</sub>	f <sub>2</sub>	f <sub>3</sub>	f <sub>4</sub>
0	0	1		1	1	1
0	1	1	1		1	1
1	0	0	0	0	1	1

$n \text{ function} = 2^4$

Sub CUBE

Min. exp

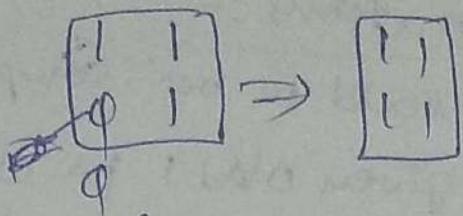

→ Subcube contains any of not possible

(14)

Don't care Ex:-

$$w = \Sigma(5, 6, 7, 8, 9) + \phi(10, 11, 12, 13, 14, 15)$$

W	12	11	10
12	00, 01	φ	1
00	1	φ	1
01	1	φ	1
11	1	φ	1
10	1	φ	1

XY

$\times_2$

$$\text{no. of functions} = 2^6 = 64$$

$$w = w + x_2 + x_4$$

(15)

Don't care Ex:-

AB	CD	CD
00	0 0 1 0	0 0 1 0
01	X X 1 X	X X 1 X
11	0 1 1 0	0 1 1 0
10	0 1 1 0	0 1 1 0

AD

not essential

AD+CD

(16) Dont care Ex 2.2:-

wx	yz	00	01	11	10	
00	0	1		1	0	$\bar{x}\bar{y}$
01	x	0	0		1	
11	x	0	0		1	
10	0	1		1	x	

$$x\bar{y} + \bar{x}\bar{y}$$


$$\underline{\underline{x\bar{y}}}$$

(17) Dont care Ex 2.3:-

xy	zw	00	01	11	10	
00	x	1		0	1	$\bar{w}\bar{y}$
01	0	1	x		0	
11		x	x		0	
10	x	0	0		x	

any one
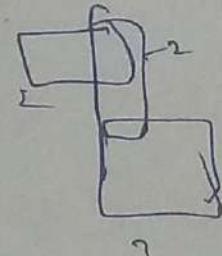
$$\underline{\underline{x\bar{y}\bar{w}}}$$



$$(z\bar{y}) - z$$

$$\underline{\underline{z}}$$

(18) Dont care Ex 2.4"

ab	cd	00	01	11	10	
00	1	1		1	1	$\bar{b}\bar{d}$
01	x					
11	x					
10	1	1		1	x	

$$\bar{a}\bar{d} + \bar{b}\bar{d}$$

$$\underline{\underline{\bar{a}\bar{d}}}$$

(19) Don't care Ex.:-

	ab	cd	00	01	11	10	
xy	00	01	X	X	1	1	bc
wz	00	01	X	X	1	1	bc
	00	01	X	X	1	1	
	10	10	X	X	1	1	

$F = \overline{b}\overline{d} + \overline{b}\overline{c}$

(20) Examples on don't care sets:-

xy\wz	00	01	11	10
00	0	X	0	0
01	0	X	1	1
11	1	1	1	1
10	0	X	0	0

(21) Which function does not implement the K-map given?

- a)  $(w+x)y$    b)  $xy+yzw$    c)  $(w+x)(\overline{w}+y)(\overline{x}+y)$

(22) None.

a) POS

b) POS

b) SOP

xy\wz	00	01	11	10	
00	0	X	0	0	y
01	0	X	1	1	$(w+x)$
11	1	1	1	1	
10	0	X	0	0	$w+yz$

(a)  $(w+x)y = wy+xy$

POS  
meets 0's

SOP  
check 1's

2 mix & 3 comb.  
y = 3 minterms  
- 3 comb.

b

$w_8$	00	01	11	10
$x_3$	0	x	0	0
00	0	x	1	1
01	0	x	1	1
11	1	1	1	1
10	0	x	0	0

$$\frac{x_4 + yw}{\text{mines}} \quad \text{mine}$$

$w_y$

$x_2$

$$x_4 + yw$$

$$x_4 \rightarrow \text{mines} \rightarrow \begin{matrix} \checkmark \text{ car} \\ \text{ no car} \end{matrix}$$

$$yw \rightarrow \text{no car}$$

( $w + n$ ) ( $\bar{w} + y$ ) ( $\bar{x} + y$ )

$\frac{w + n}{\text{no car}}$        $n$        $\frac{\bar{x} + y}{4}$


$w_8$	00	01	11	10
$x_3$	0	x	0	0
00	0	x	1	1
01	0	x	1	1
11	1	1	1	1
10	0	x	0	0

$$(w + n)$$


$$(\bar{x} + y)$$

$$(\bar{w} + y)$$


24) Finding Minimal Expressions:-

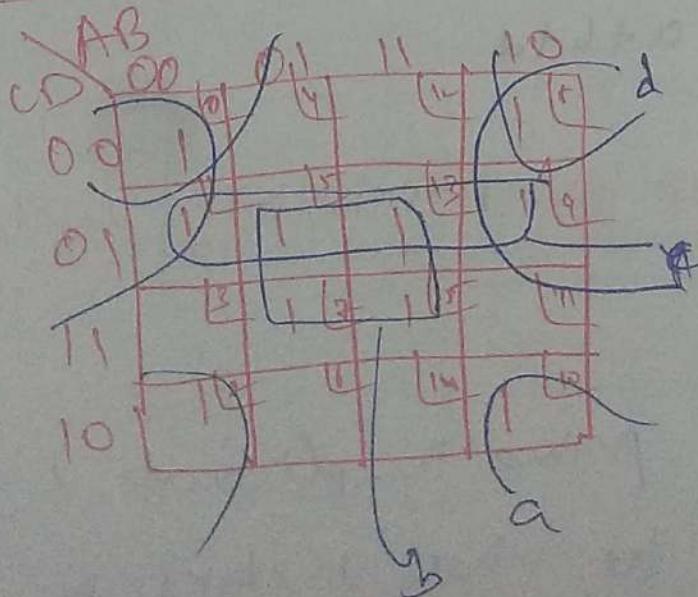


2-var K-map :-

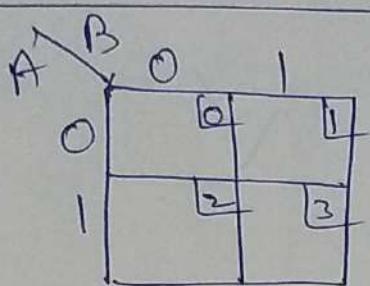

3-var K-map:-

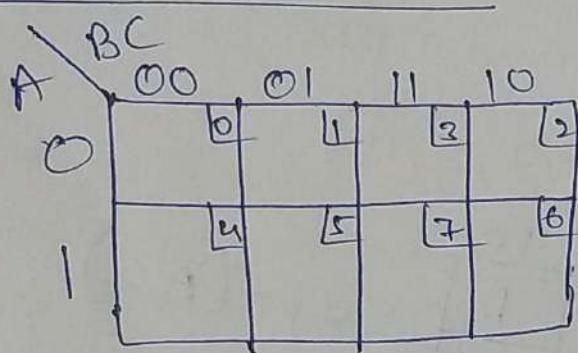

4-var K-map:-

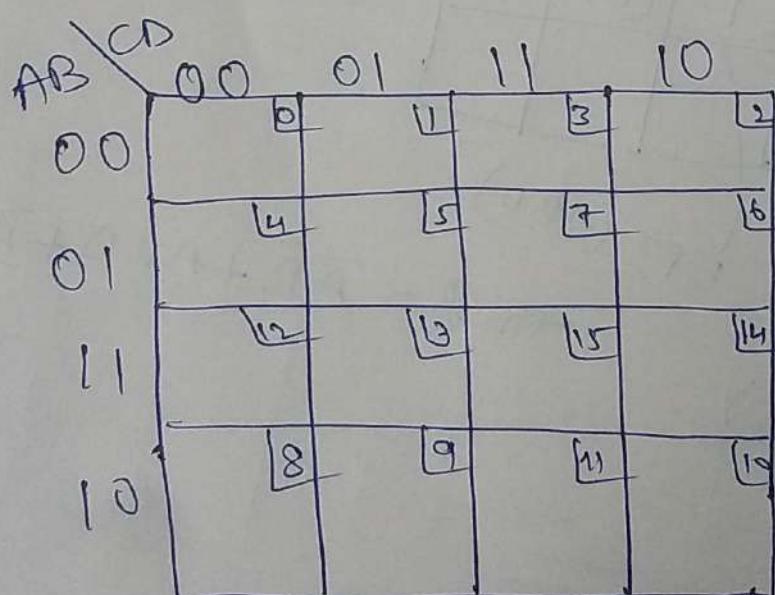

① The Boolean expression

$(x+y)(x+\bar{y}) + \bar{x}\bar{y} + \bar{x}$  simplifies to

- Ⓐ  $x$  Ⓑ  $y$  Ⓒ  $xy$  Ⓓ  $x+y$

Ans:-

$$x + x\bar{y} + xy + \bar{x}\bar{y} \cdot x$$

$$x(1 + \bar{y} + y + \bar{x}\bar{y}) = x$$

② In the Karnaugh map shown below,  $X$  denotes a don't care term. What is the minimal form of the function represented by the Karnaugh map?

		a\b	00	01	11	10
		c\d	00	01	11	10
00	00	1	1			
	01	X				
11	00	X				
	10	1	1		X	

- Ⓐ  $\bar{b}\bar{d} + \bar{a}\bar{d}$   
Ⓑ  $\bar{a}\cdot\bar{b} + \bar{b}\bar{d} + \bar{a}\bar{b}\bar{d}$   
Ⓒ  $\bar{b}\bar{d} + \bar{a}\bar{b}\bar{d}$   
Ⓓ  $\bar{a}\bar{b} + \bar{b}\bar{d} + \bar{a}\cdot\bar{d}$

		a\b	00	01	11	10
		c\d	00	01	11	10
00	00	1	1			
	01	X				
11	00	X				
	10	1	1	X		

$$\therefore \bar{a}\bar{d} + \bar{b}\bar{d}$$

option (a)

③ What is the equivalent boolean expression in product-of-sums form for the Karnaugh map given in fig.?


	AB	00	01	11	10
CD	00	1	1		
	01	1			1
	11	1	1	1	
	10		1	1	

a)  $B\bar{D} + \bar{B}D$

b)  $(B + \bar{C} + D)(\bar{B} + C + \bar{D})$

c)  $(B + D)(\bar{B} + \bar{D})$

d)  $(B + \bar{D})(\bar{B} + D)$

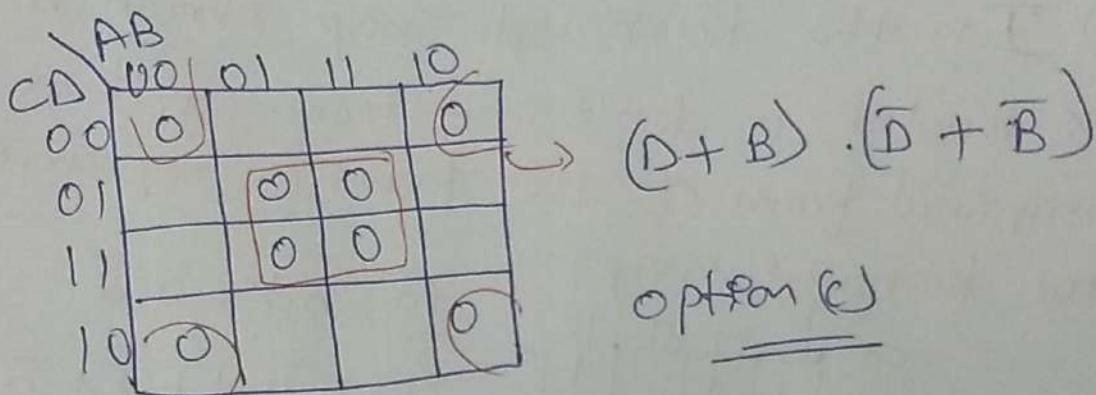

④ A Combinational circuit has inputs A, B and C and its Karnaugh map is given in below fig. The output of the circuit is?

	AB	00	01	11	10
C	0	1	1	1	1
	1	1	1	1	1

a)  $(AB + A\bar{B}) \cdot C$

b)  $(\bar{A}B + A\bar{B}) \cdot \bar{C}$

c)  $A \oplus B \oplus C$


d)  $\bar{A} \cdot \bar{B} \cdot \bar{C}$

$$\bar{A}\bar{B}\bar{C} + \bar{A} \cdot \bar{B}C + ABC + A\bar{B}\bar{C}$$

$$(\bar{A}B + A\bar{B})\bar{C} + (\bar{A}\bar{B} + AB)C$$


$$(A \oplus B)\bar{C} + A \oplus B \oplus C = A \oplus B \oplus C$$
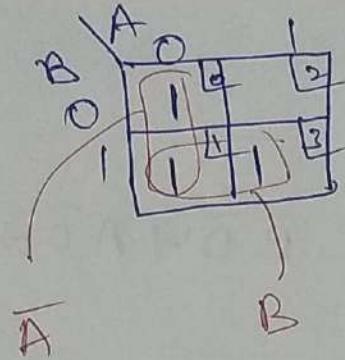
$$\textcircled{5} \quad f(A, B) = \sum m(0, 1, 3)$$




i.e.  $\bar{A} + B$
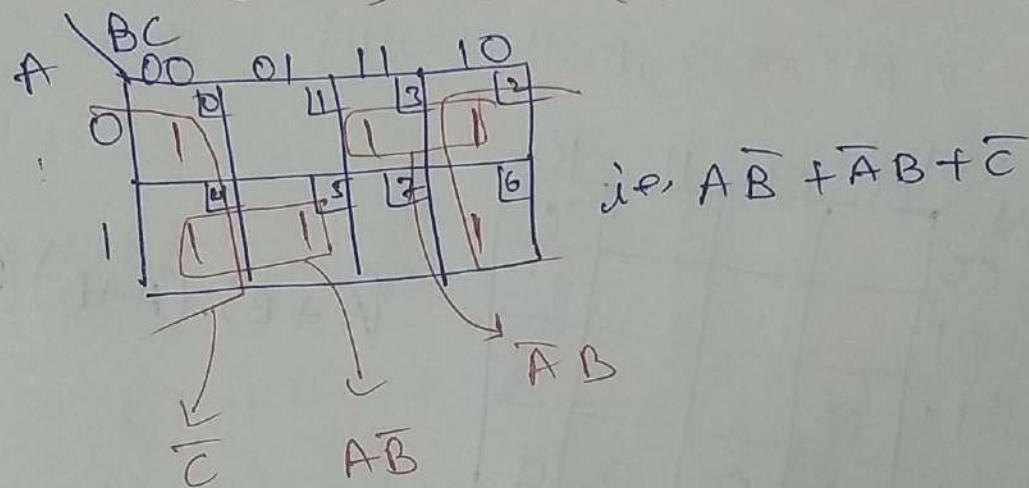
$$\textcircled{6} \quad \text{Reduce } f(A, B, C) = \sum m(0, 2, 3, 4, 5, 6)$$



i.e.  $A\bar{B} + \bar{A}B + \bar{C}$
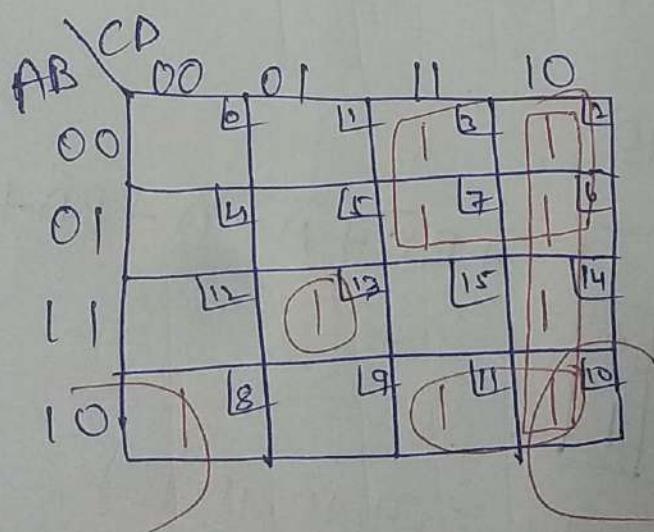
$$\textcircled{7} \quad f(A, B, C, D) = \sum m(2, 3, 6, 7, 8, 10, 11, 13, 14)$$



$\bar{CD} + \bar{A}C + \bar{B}C + A\bar{B}\bar{D} + AB\bar{D}$

$$⑧ f = \sum m(0, 1, 2, 3, 5, 7, 8, 9, 10, 12, 13)$$

AB \ CD	00	01	11	10
00	1	1	1	1
01		1	1	
11	1	1		
10	1	1		1

$$\bar{B}\bar{D} + A\bar{C} + \bar{A}D$$

$$⑨ f = \pi M(2, 8, 9, 10, 11, 12, 14)$$

AB \ CD	00	01	11	10
00				0
01				
11	0			0
10	0	0	0	0

$$(\bar{A} + B) \cdot (\bar{A} + D) \cdot (B + \bar{C} + D)$$

$$⑩ f(A, B, C, D) = \sum m(1, 4, 7, 10, 13) + \sum d(5, 14, 15)$$

AB \ CD	00	01	11	10
00		1		
01	1	0	1	
11		1	0	1
10				1

$$\bar{A}B\bar{C} + \bar{A}\bar{C}D + BD + AC\bar{D}$$

$$⑪ f(A, B, C, D) = \pi M(0, 1, 2, 3, 4, 10, 11, 15)$$

AB \ CD	00	01	11	10
00	0	0	0	0
01	0		0	
11			0	0
10			0	0

$$(B + \bar{C})(A + B)(A + C + D)(A + \bar{C} + \bar{D})$$

$$⑫ f(A, B, C, D) = \sum m(6, 7, 8, 9) + d(10, 11, 12, 13, 14, 15).$$

AB\CD	00	01	11	10
00				
01				
11	0	0	0	0
10	0	0	0	0

$$\bar{A}(\bar{B} + \bar{C}).$$

⑬ Make a K-map of the following expression and obtain minimal expression in SOP & POS form.

$$f = AB + A\bar{C} + C + AD + A\bar{B}C + ABC$$

SOP

$$f = \sum m(2, 3, 6, 7, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$= \sum m(0, 1, 4, 5)$$

AB\CD	00	01	11	10
00				
01				
11	1	1	1	1
10	1	1	1	1

AB\CD	00	01	11	10
00	0	0		
01	0	0		
11				
10				

$$A + C$$

$$⑭ f(A, B, C, D) = \sum m(0, 2, 7, 8, 12) + \sum d(10, 13) \quad (A + C)$$

AB\CD	00	01	11	10
00	1			1
01			1	
11	1	0		
10	1			0

$$\bar{B}\bar{D} + A\bar{C}\bar{D} + \bar{A}BCD$$

$$15) f(w, x, y, z) = \pi M(0, 5, 7, 10, 12, 13) \cdot \pi d(4, 15)$$

$w \times$	$y^z$	00	01	11	10	$(w+x+y+z)$
00	0					$(\bar{x} + \bar{z})$
01		0	0			$(\bar{w} + \bar{x})$
11	0	0	0	0		$(\bar{w} + \bar{y} + \bar{z})$
10				0	0	$(\bar{w} + y + z)$

$$\underline{(x + z)} \underline{(w + x)} \underline{(w + y + z)} \underline{(w + x + y + z)}$$


Prime Implicant :- (PI)

Each square (or) rectangle made up of the bunch of adjacent min terms is called a sub cube. Each of these sub cubes is called a prime implicant(PI).

Essential Prime Implicant (EPI):-

The prime implicant which contains at least one '1' which cannot be covered by any other prime implicant is called EPI.

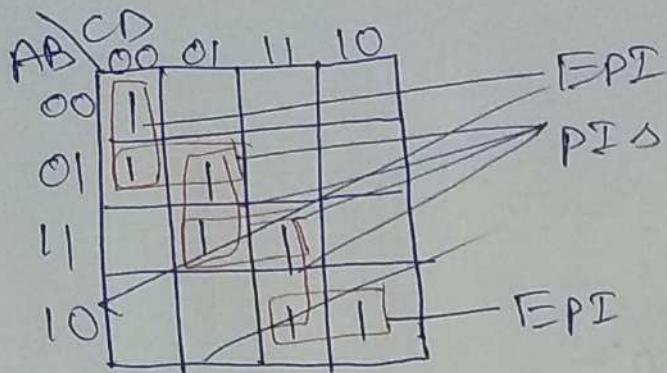
$$\textcircled{1} \quad f(A, B, C, D) = \sum m(0, 4, 5, 10, 11, 13, 15).$$



$\alpha$

\textcircled{2} Identify PIs and EPIs
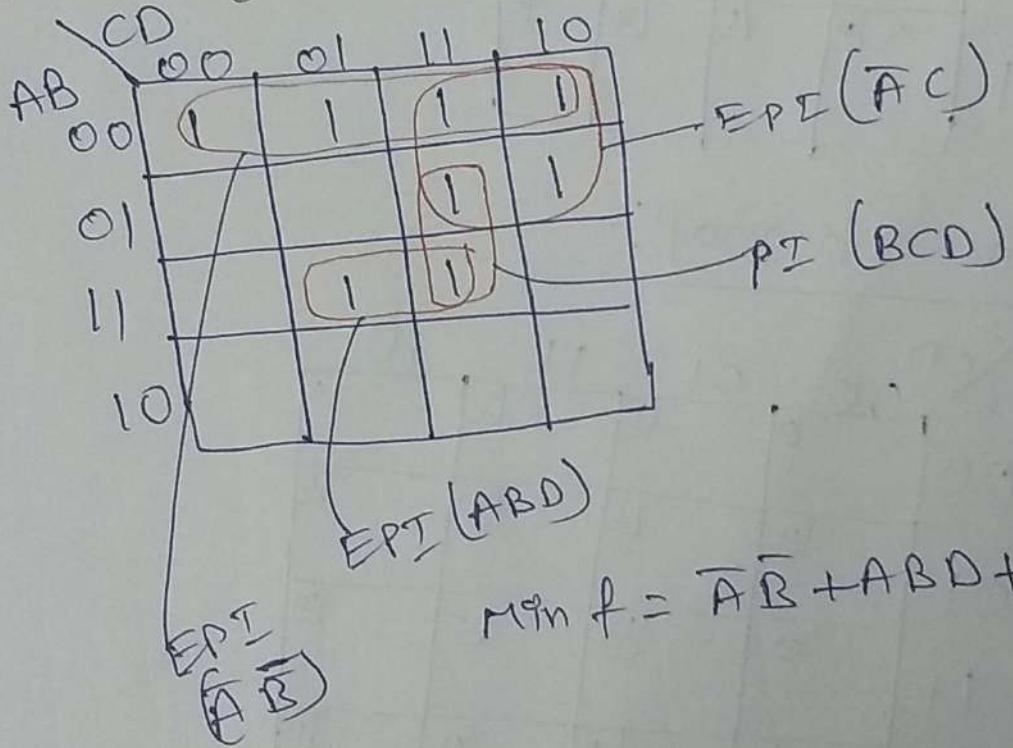
$$f = \sum m(0, 1, 2, 3, 6, 7, 13, 15).$$



$$\min f = \overline{A}\overline{B} + ABD + \overline{AC}$$


$\alpha$

### 3. Design and Synthesis of Combinational Circuits (6u)

①
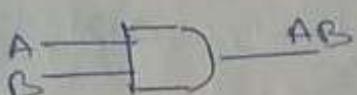
#### ① Introduction to Logic design:-


- The main application of Switching Theory in the design of digital circuits. It is called Logic design.
- These circuits are designed using basic elements called gates.




AND gate




OR gate

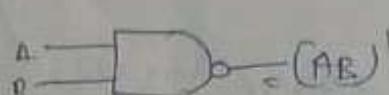
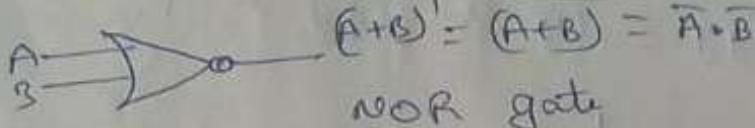
$$\text{NAND gate} = \overline{A \cdot B} = \overline{A} + \overline{B}$$




NOR gate

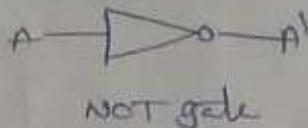

NOT gate




EX-OR gate

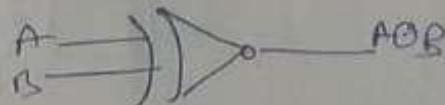

EX-NOR gate

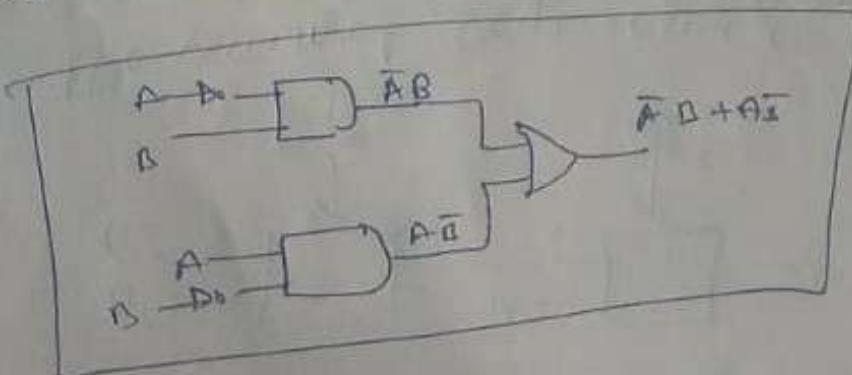②  $\overline{A} \cdot B + A \cdot \overline{B}$



- The ~~for~~ logic kit selected to propagation delay cost

→ Decrease no. of levels in the circuit decreases the propagation delay. (2)

→ Decrease the no. of gates decrease the cost of the circuit.

No. of gates in the circuit,

~~LST~~

< 10 - LST

10 - 100 - MST

100 - 1000 - CST

> 1000 - VLSI

→ Basic gates are, OR, AND, NOT gates.


→ Universal gates are NAND, NOR gates.

### a) AND-OR, OR-AND Realization:-

SOP

AND-OR realization

$$f(A, B, C, D) = AB + CD$$

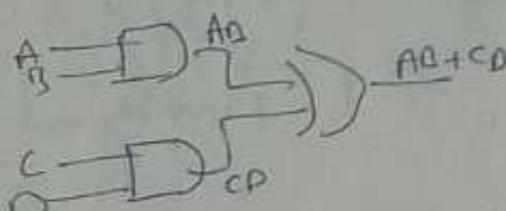


AND - OR realization


POS

OR-AND realization

$$f(A, B, C, D) = (A+B)(C+D)$$

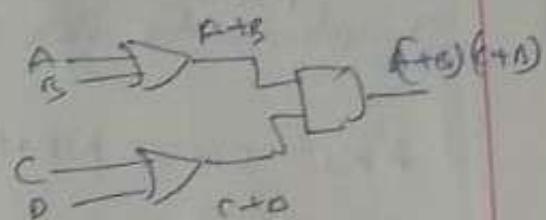

OR-AND realization

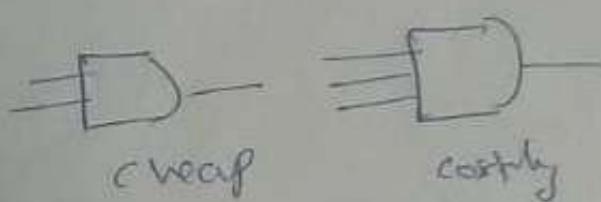

→ unless specified FOM in = 2

FOM out we can't consider

①  $\bar{A}B + \bar{C}D$





\* Realization means implement a function using gates.


(3)

② AND-OR ( $\Sigma\phi_1$ )

$AB + CD$

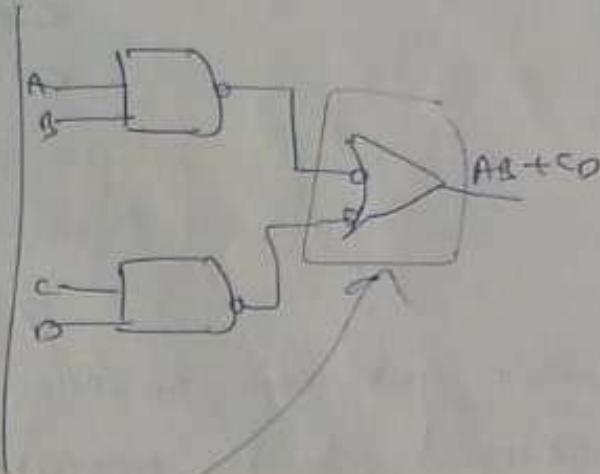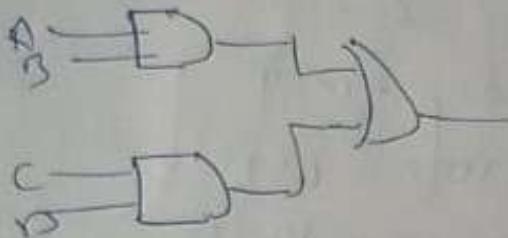

NOT also implements

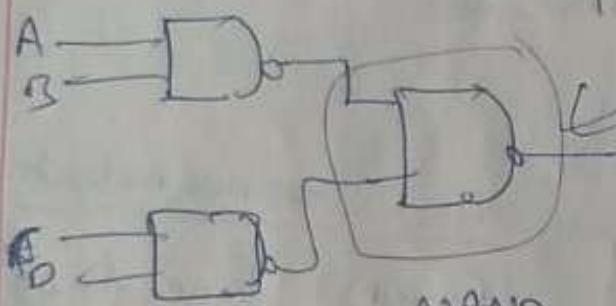

NAND  
Implemented with NAND only




( $\bar{x}_1, -$ ) - FC



AND-OR = NAND-NAND

Fundamentally complete

③ OR-AND is also same

$(A+B)(C+D)$

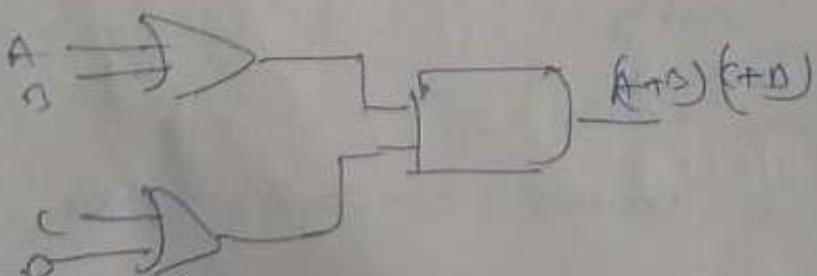


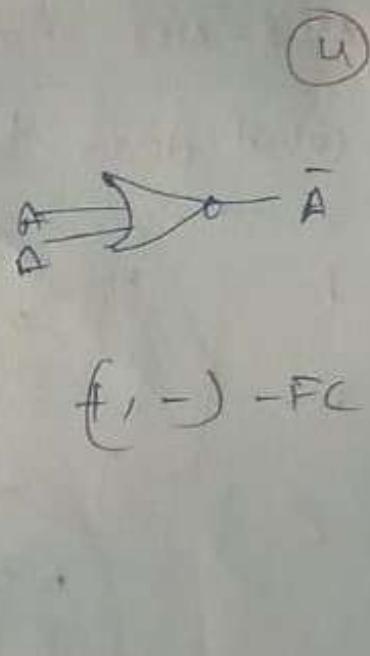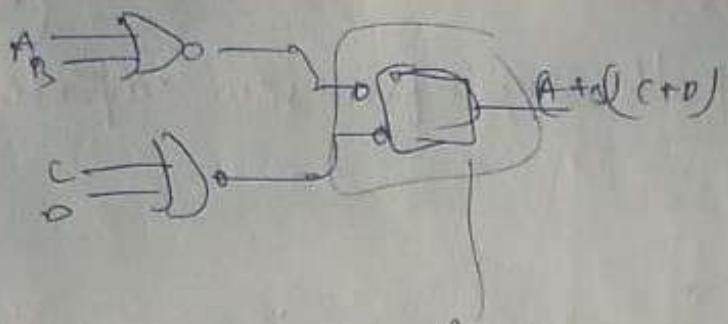



NOR-NOR  
 $\therefore \text{OR-AND} = \text{NOR-NOR realization.}$

Minimum no. of NAND gates Example:-

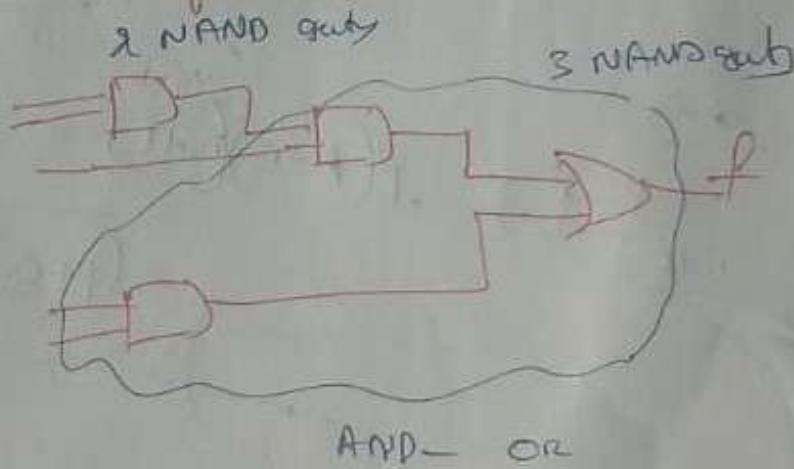Identifying min.no. of two p/p NAND gates required to represent the following



$\Rightarrow 3 \text{ NAND gates of}$

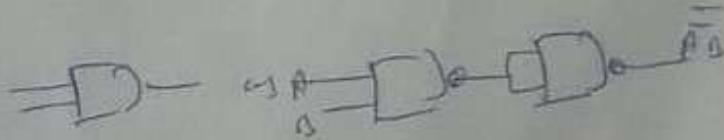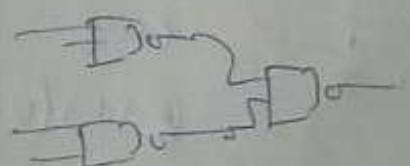


∴ 5 NAND gates required.

7


NOR-NOR example:-

5

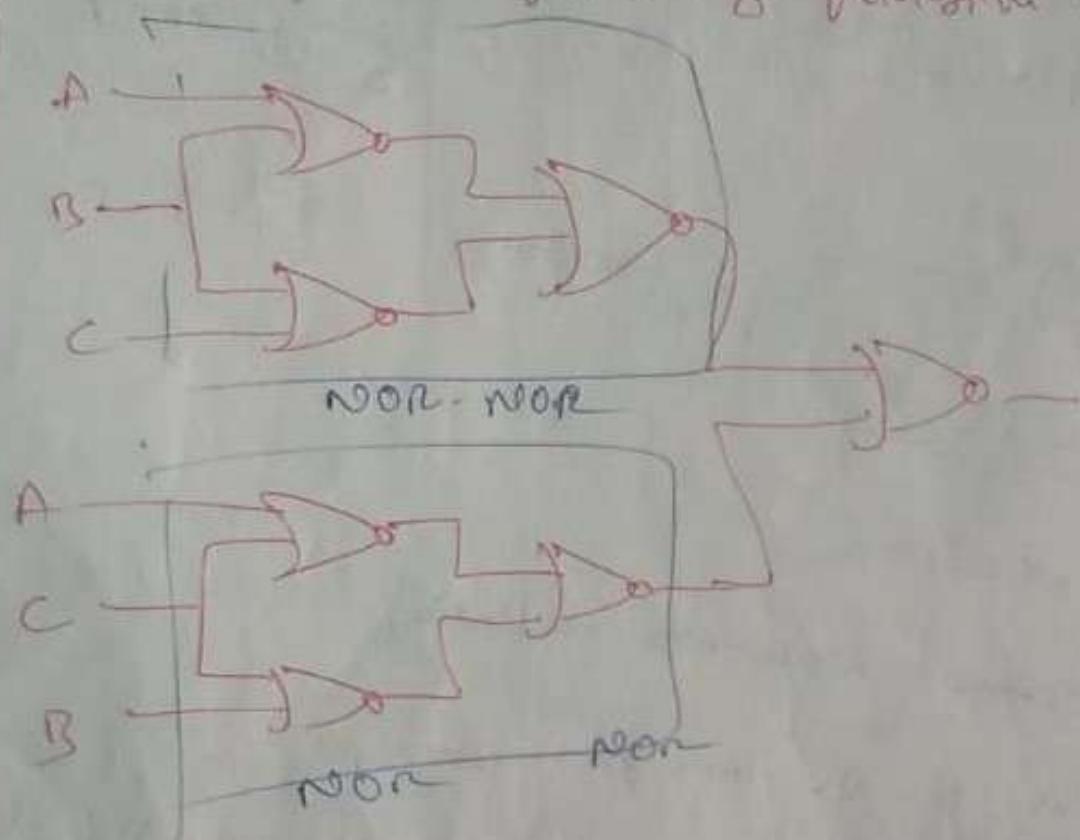What does the following function represent?


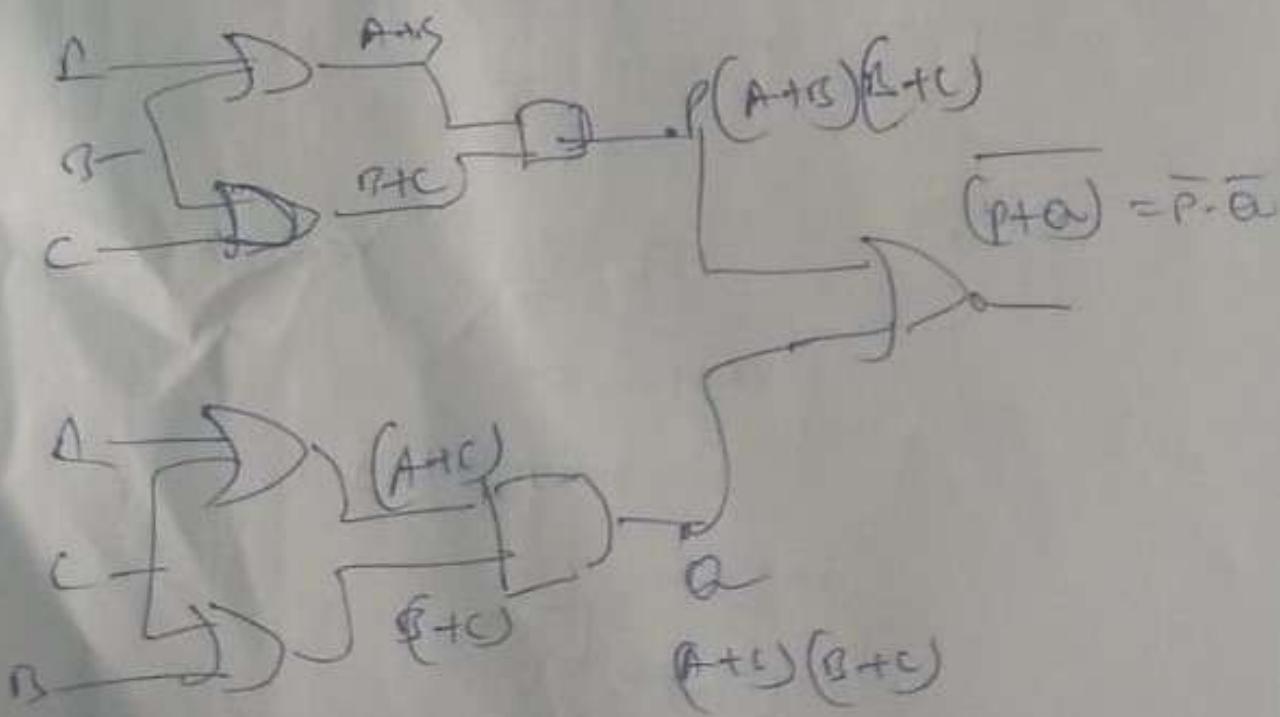
$$\text{NOR} - \text{NOR} = \text{OR-AND}$$



$$P = (A+B)(B+C)$$

$$= AB + AC + BC + BC$$

$$= AB + AC + BC = AC + B$$

~~ABC~~

$$Q = (A+C)(B+C)$$

$$= AB + AC + BC + CC$$

$$= AB + AC + C$$

$$= AB + C$$

$$\overline{PQ} = \overline{(C+A)} \cdot \overline{(B+C)}$$

$$= \overline{B} \cdot \overline{(A+C)} \cdot \overline{C} (\overline{A} + \overline{B})$$

$$= (\overline{B}\overline{A} + \overline{B}\overline{C})(\overline{C}\overline{A} + \overline{C}\overline{B})$$

$$= \overline{B}\overline{A}\overline{C} + \overline{B}\overline{A}\overline{C} + \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}\overline{C} + \overline{B}\overline{C}$$




$$= \overline{B}\overline{A}\overline{C} + \overline{B}\overline{C} = \overline{B}\overline{C}$$

Minimum no. of NOR gates Example

Find the no. of 2 input NOR gates required to represent  $F(P, Q, R) = P + QR$

NOR-NOR = OR-AND (POS)

$$(P+Q)(P+R)$$

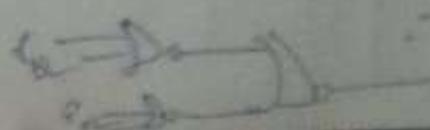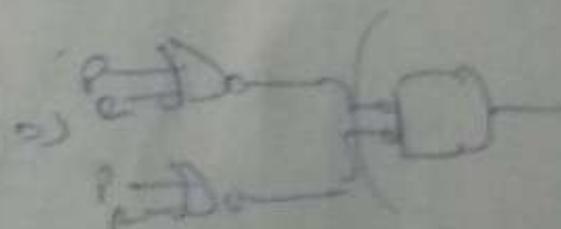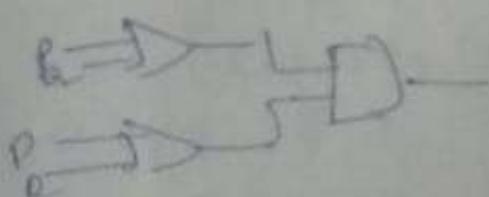


∴ 3 NOR gates  
needed

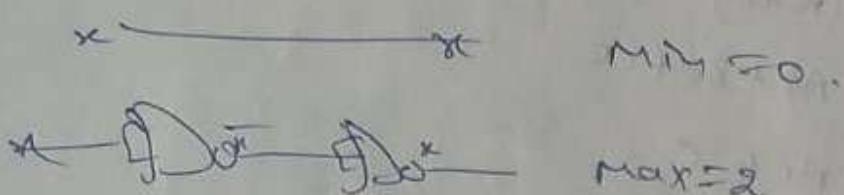(6) Min. no. of NOR gates ~~are~~ required to implement  
 $x + \bar{y} + \bar{z}$

First see if it in Min. form or not

$$\text{or } ((\bar{x}\bar{y} + \bar{y}\bar{z}) = x$$





MIN  $\leq 0$


MAX = 2

(7) Ex-OR and Ex-NOR implementation with NOR and  
 NAND gates


What does the following represent?

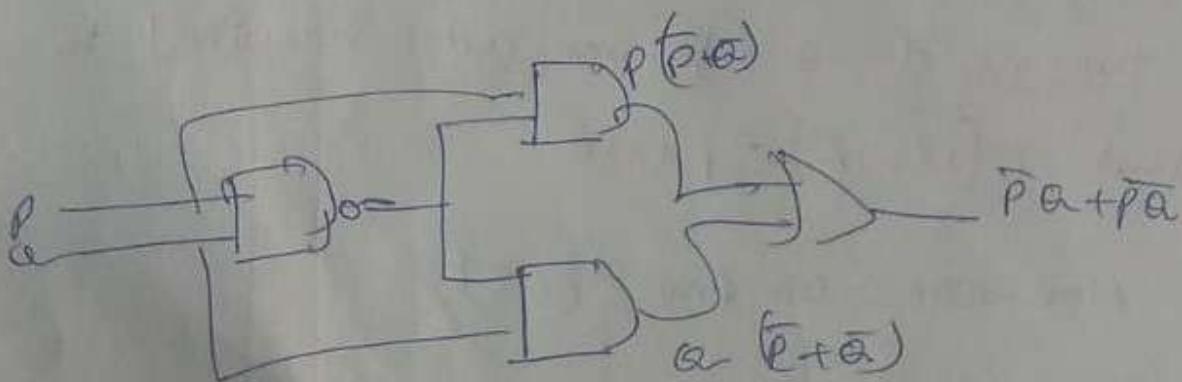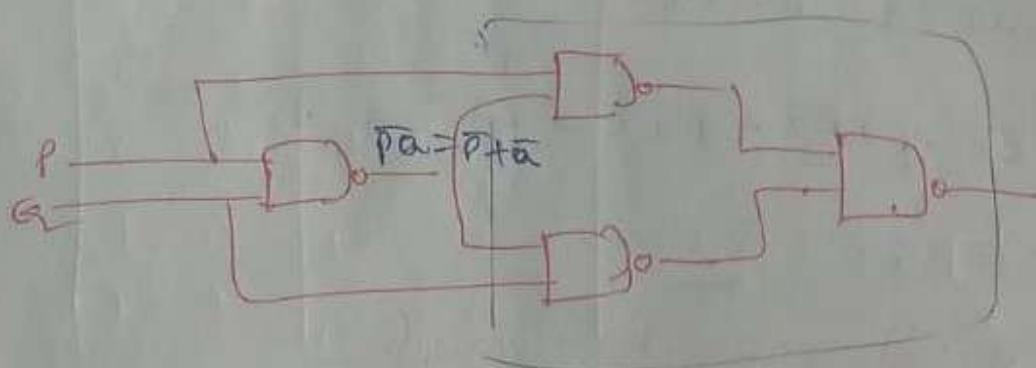

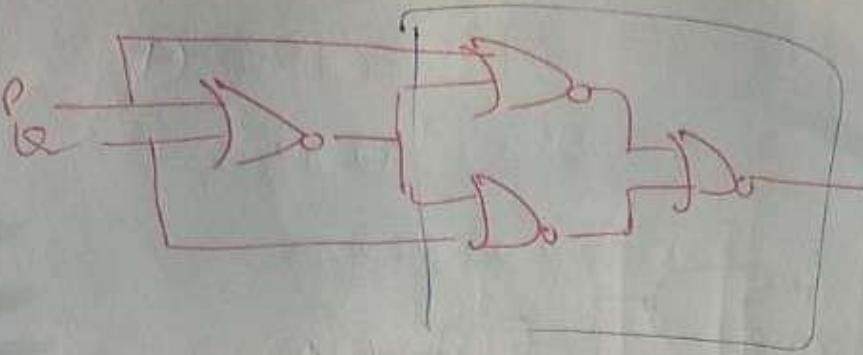Ex-OR  $\rightarrow$  4 NOR gates  
 $\rightarrow$  4 NOR gates



④

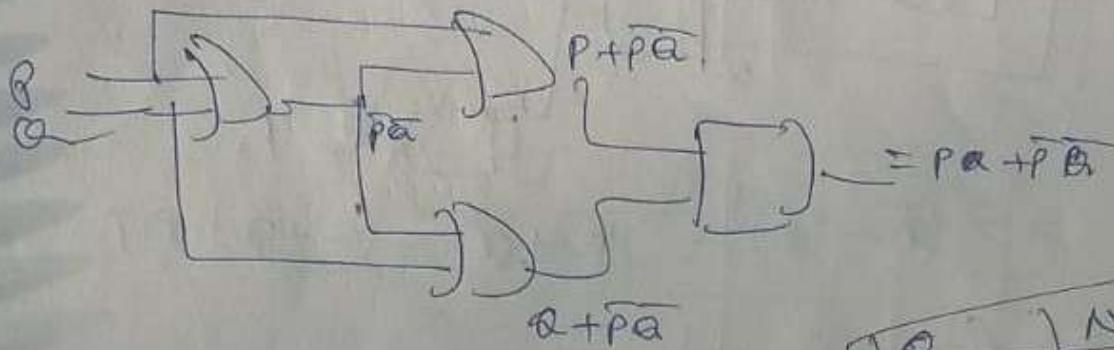


$\Sigma$ -NOR  $\leftrightarrow$  4 NOR gate

$\leftrightarrow$  (4+) NAND gate

		NOR	NAND
X-OR	5	4	
X-NOR	4	5	

### ⑤ Half Adder:-

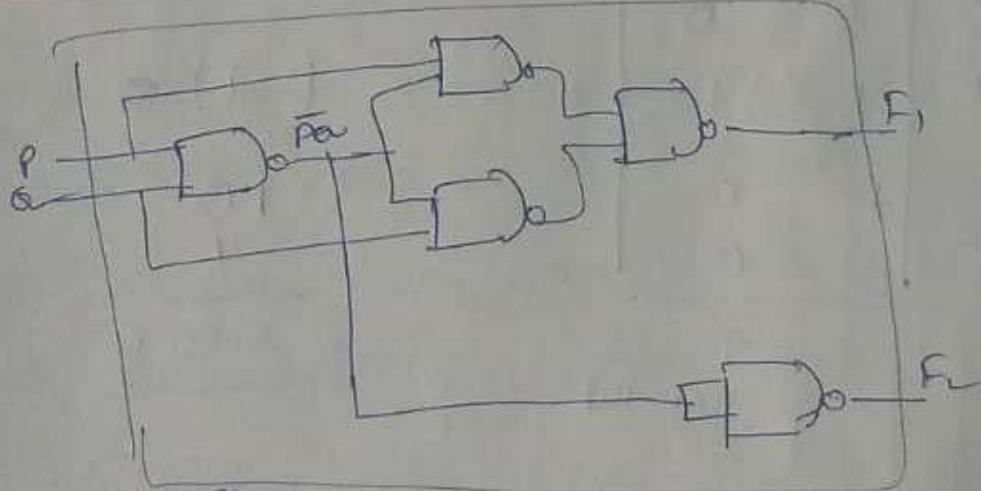

Q

$$F_1 = P \oplus Q$$

$$F_2 = P\bar{Q}$$

Half Adder  $\rightarrow$  Add two bits

Full Adder  $\rightarrow$  Add three bits


P Q	F1	F2
0 0	0	0
0 1	1	0
1 0	1	0
1 1	0	1

↑      ↑

Sum    carry

### Q) Half Subtractor :-

(9)

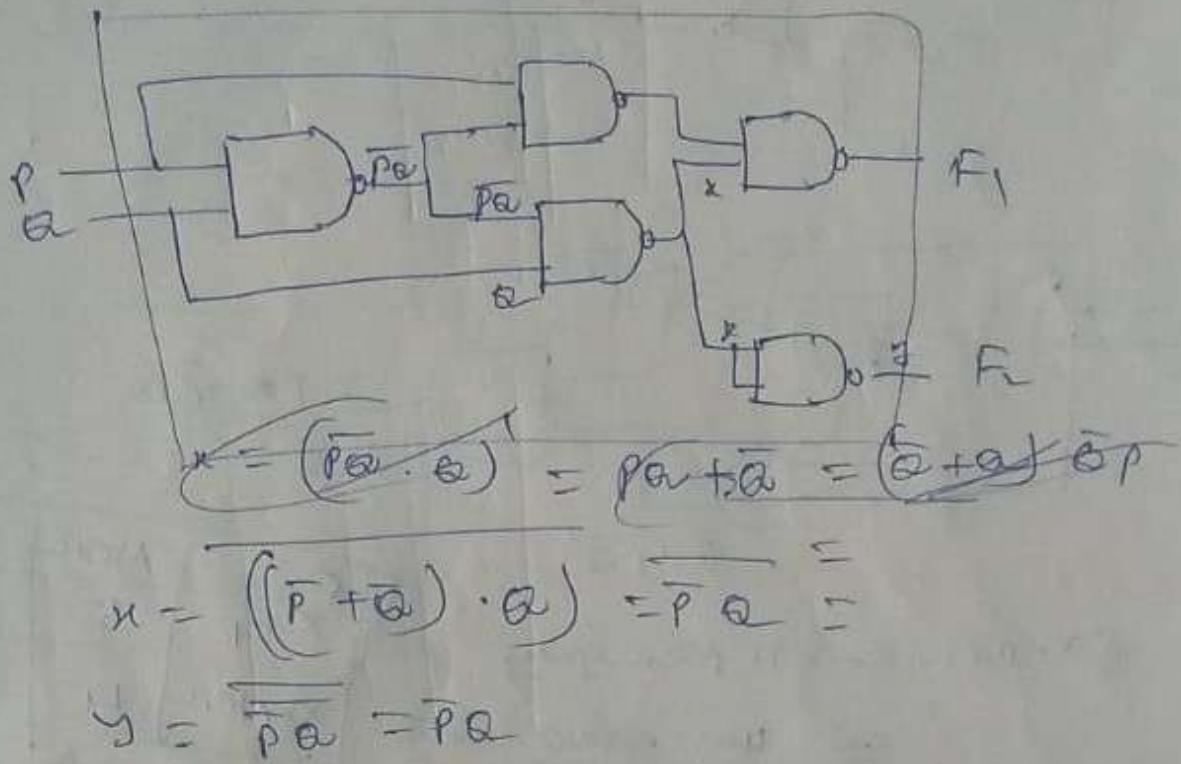


P	Q	F <sub>1</sub>	F <sub>2</sub>
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$$\begin{array}{r} & & 1 \\ & & 1 \\ \Rightarrow & & 1 \\ & & 1 \\ & & \hline 2 - 1 & = 1 \end{array}$$

Borrow

### Comparator:-

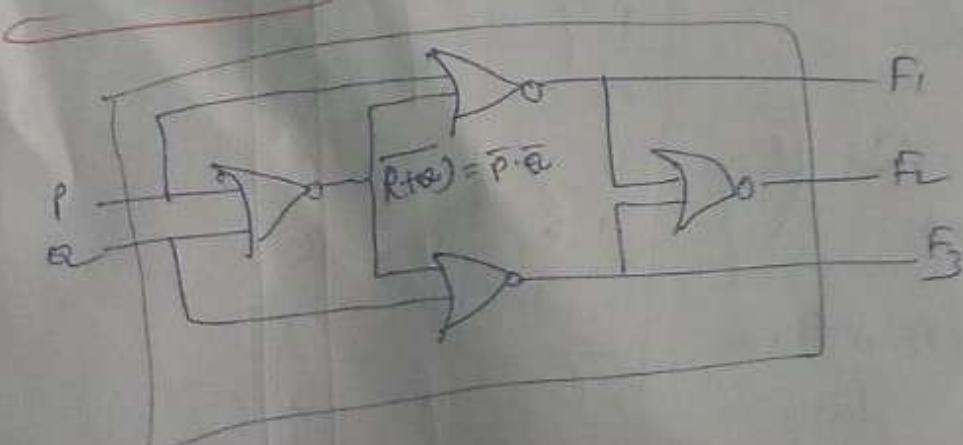

w.r.t.

10

$$F_2 = \overline{p} \bar{q} + p q$$

$$F_1 = \overline{\cancel{p} + \cancel{p} \bar{q}} = \cancel{\bar{p}} = \overline{p + \bar{q}} = \overline{p} \cdot \bar{q}$$


$$F_3 = \overline{q + \bar{p} \bar{q}} = \overline{q + \bar{p}} = \bar{q} \cdot p = p \bar{q}$$

P	Q	F <sub>1</sub>	F <sub>2</sub>	F <sub>3</sub>
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

$\uparrow$        $\uparrow$        $\uparrow$   
 $p \leq Q$      $p = Q$      $p \geq Q$
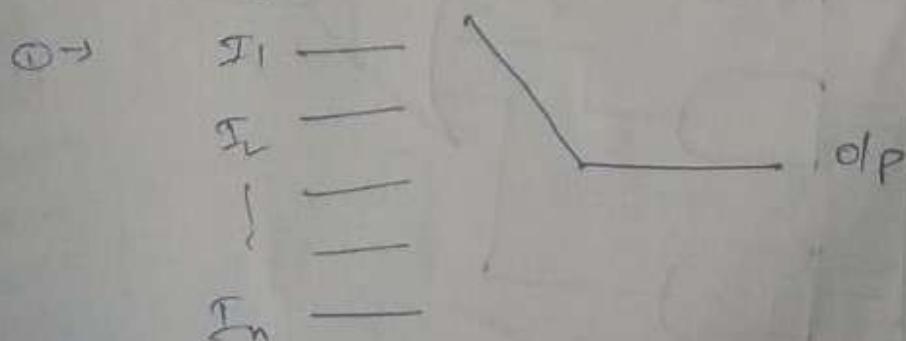
## ① Introduction to MUX:-


- A Multiplexer is an electronic switch that can connect one out of 'n' I/P to O/P.
- It cannot change the logical level of the I/P, it only provides the connection b/w I/P and O/P.
- It is functionally complete, i.e. all boolean functions can be realized using only multiplexer without any other gates.



④  $\rightarrow$  take the iff and produce same as if.

⑤ ~~use~~ my MUXs and implement any cat. (11)

1/13

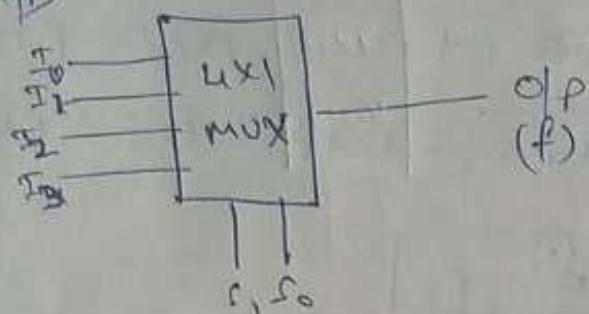

S <sub>1</sub>	S <sub>0</sub>	f(p) / f
0	0	I <sub>0</sub>
0	1	I <sub>1</sub>
1	0	I <sub>2</sub>
1	1	I <sub>3</sub>

↑  
select  
line

$2^n \times 1$  MUX ; when  
 $n = \text{no. of selecting}$

$2^M = \text{no. of ifp}$


1 = ifp.

Characteristic table

$$f = \bar{s}_1 \bar{s}_0 s_0 + \bar{s}_1 s_0 \bar{s}_1 + s_1 \bar{s}_0 \bar{s}_2 + s_1 s_0 \bar{s}_3$$

Realization (Implementation)

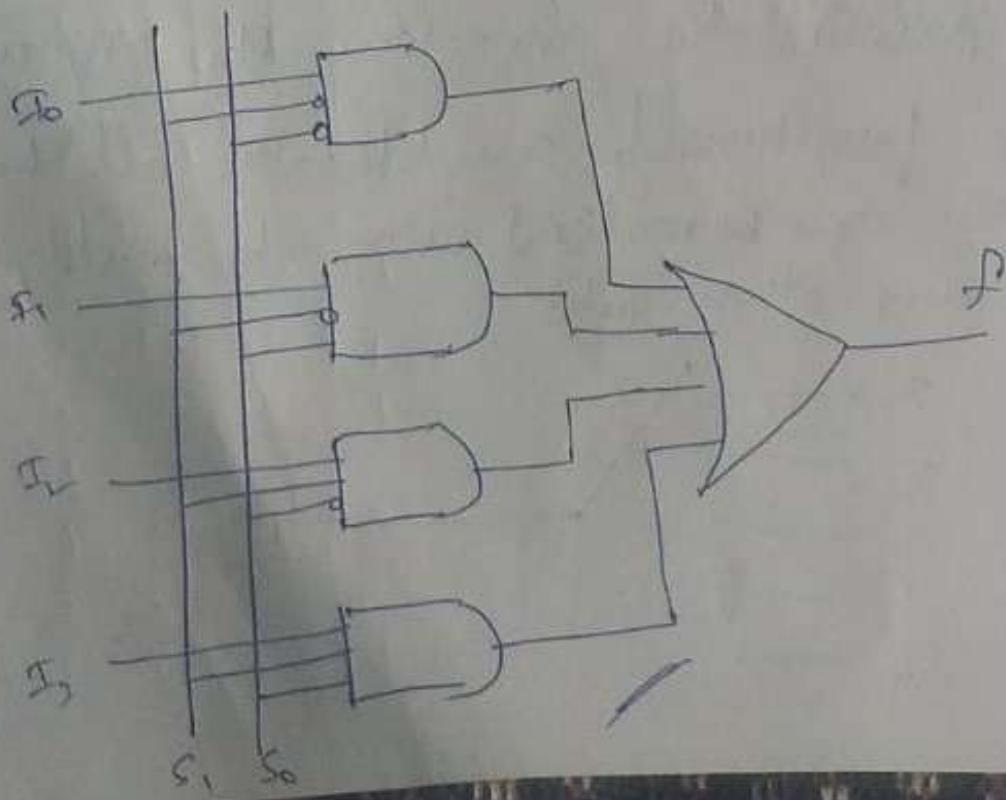$f \in \text{SOP} \Rightarrow \text{AND-OR realization}$




(1) Providing MUX is functionally complete :- (12)

(+) +, -) Showing there three by with any set of operators, called, as functionally complete.

(+, -) - FC  
(+, -) - FC

NOT Implementing using MUX

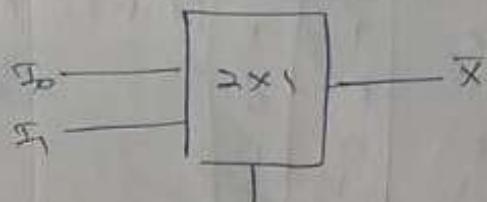


$$f_1 = \bar{x} I_0 + x I_1$$

~~→ X = 1~~

x	$\bar{x}$
I <sub>0</sub>	I <sub>1</sub>
0	1
1	0

$$\bar{x} = \bar{x} \cdot 1 + x \cdot 0$$

AND :-

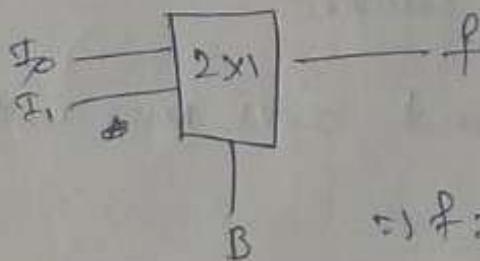

$$\therefore f = \bar{B} I_0 + B I_1$$

A	B	AB
0	0	0
0	1	0
1	0	0
1	1	1

$$f = AB = B(A) + \bar{B}(0)$$

OR :-


A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

$$\begin{aligned}
 f &= A+B = \bar{A}B + A\bar{B} + AB \\
 &= \bar{B}A + B(\bar{A} + A) \\
 &= \bar{B}A + B(1)
 \end{aligned}$$

13

## Implementing Functions with MUX logic

12

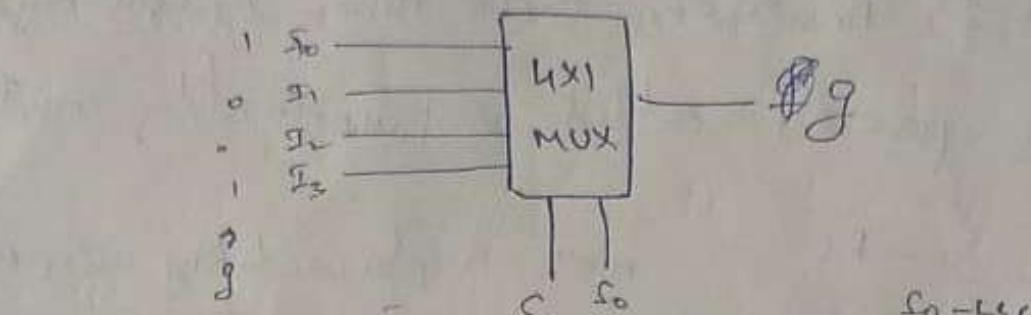

A	B	g	h
0	0	1	1
0	1	0	0
1	0	0	1
1	1	1	0

$$g(A, B) = \frac{B}{A \bar{B} + AB}$$

$$= \overline{A} \overline{B} + \overline{A} B \cup A \overline{B} \cup A B$$

1      2      3      4  
 2      1      2      1

 $S_0 - LS_L$  $S_1 - MS_L$ 

∴  $S_3, \dots, S_0, S_1, S_0$

$\uparrow$   $MS_L$        $\uparrow$   $LS_L$

→ For  $2^m \times 1$  MUX, it need ' $m$ ' selectors.

$2^2 \times 1$  MUX → 2 selectors


$2^4 \times 1$  MUX → 4 selectors

→ We can implement  $2^2 \times 1$  MUX with 3 selectors.

A	B	C	g
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

$$\begin{aligned}
 g &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}\bar{B}C + ABC \\
 &= \underset{\Sigma_0}{\bar{A}\bar{B}(C)} + \underset{\Sigma_1}{\bar{A}B(\bar{C}+C)} + \underset{\Sigma_2}{\bar{A}\bar{B}(B)} + \underset{\Sigma_3}{AB(C)}
 \end{aligned}$$

14

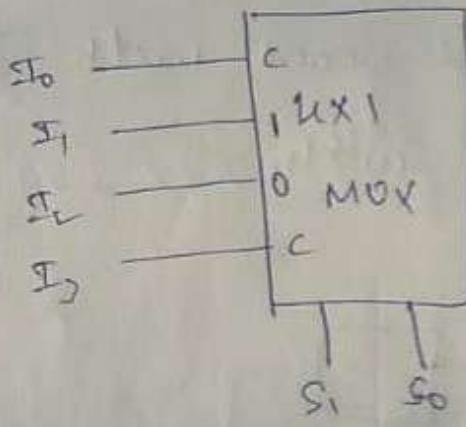

$\therefore 2^m \times 1$  MUX can also implement ~~more~~  $>n$  selector variables.

② ~~OR~~  $2^m \times 1$  MUX with n selector vars.

$$\begin{aligned}
 &\underset{\Sigma_0}{\bar{A}\bar{B}(CD)} + \underset{\Sigma_1}{\bar{A}B(\bar{CD})} + \underset{\Sigma_2}{A\bar{B}(CD)} + \underset{\Sigma_3}{AB(CD)}
 \end{aligned}$$




Whether no. of selected are possible, but it needs more gates to implement this.

Extra:

$$f(A, B, C) = \sum(1, 2, 4, 6, 7)$$

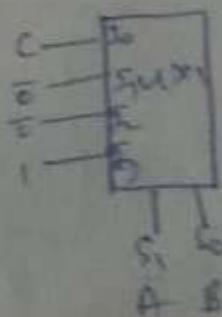
$$\begin{aligned}
 &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC \\
 &= \underset{\Sigma_0}{\bar{A}\bar{B}(C)} + \underset{\Sigma_1}{\bar{A}B(\bar{C})} + \underset{\Sigma_2}{(A\bar{B})(\bar{C})} + \underset{\Sigma_3}{AB(\bar{C}+C)}
 \end{aligned}$$



(15) Multiplexers with Enable Input :-

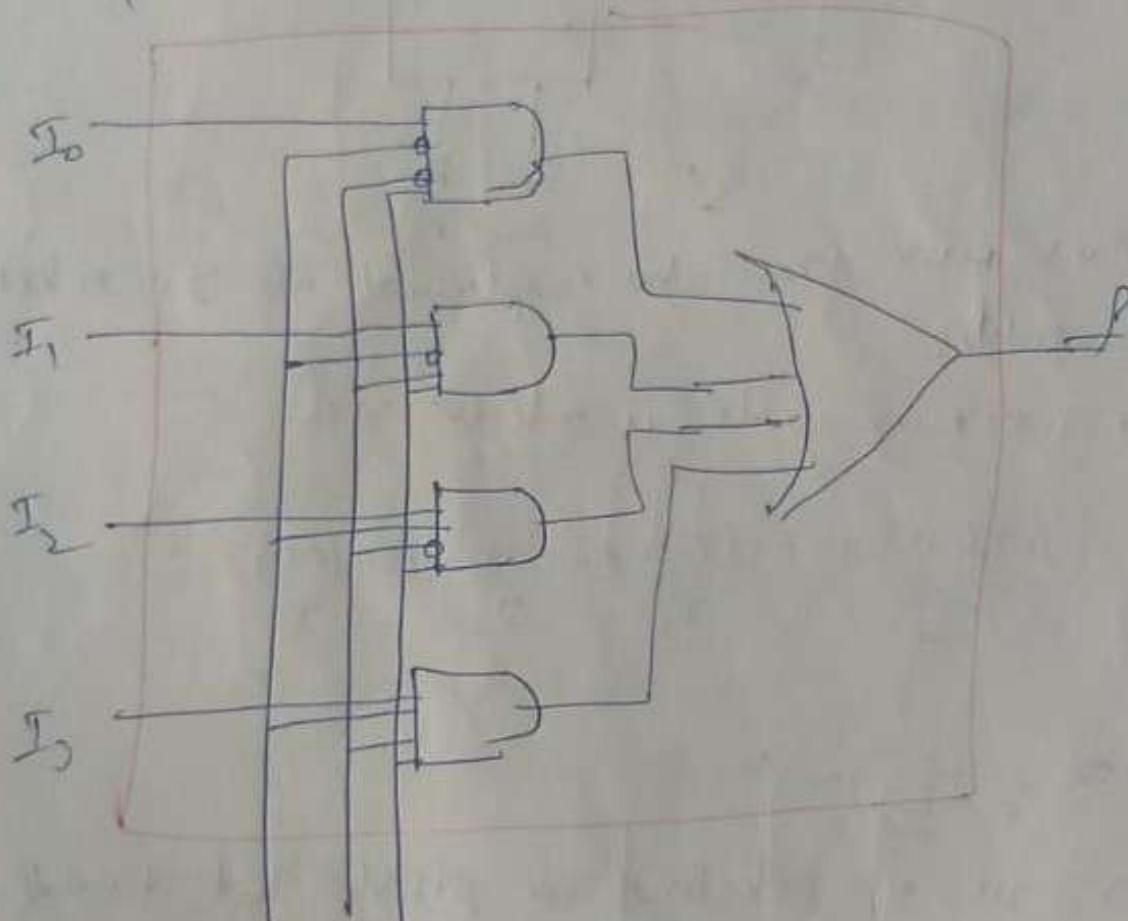(15)

Whenever  $E=1$  then the MUX selects with the if's and produce the corresponding result of. Otherwise not select with the if's and output 0.  
 → It acts like a switch.




	$S_1, S_0$	$E$
$I_0$	0 0	
$I_1$	0 1	
$I_2$	1 0	
$I_3$	1 1	

Q. Ans

$$f = E(I_0 \bar{S}_1 \bar{S}_0 + I_1 \bar{S}_1 S_0 + I_2 S_1 \bar{S}_0 + I_3 S_1 S_0)$$

15 Minimize the functions represented by following MUX

16

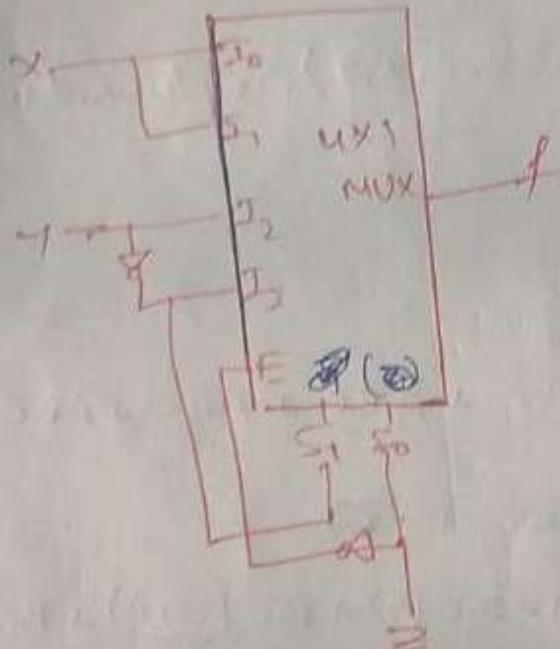

→ Always do write characteristic equation.

$$f_1 = E \left( I_0 \bar{S}_1 \bar{S}_0 + I_1 \bar{S}_1 S_0 + I_2 S_1 \bar{S}_0 + I_3 S_1 S_0 \right)$$

here,  $S_0 = Z$ ;  $S_1 = \bar{Y}$ ;  $E = \bar{Z}$

~~$I_0 = X$~~ ;  $I_1 = Y$

$$I_2 = 1; I_3 = \bar{Y}$$

$$f = \bar{Z} (XY\bar{Z} + XY^2 + \underline{Y\bar{Y}^2} + \bar{Y}\bar{Y}^2)$$



$$= \bar{Z} (XY\bar{Z} + XY^2 + \bar{Y}^2)$$

$$= \bar{Z} (XY(\bar{Z} + 1) + \bar{Y}^2)$$

$$= \bar{Z} (XY + \bar{Y}^2)$$

$$= XY\bar{Z}$$

∴

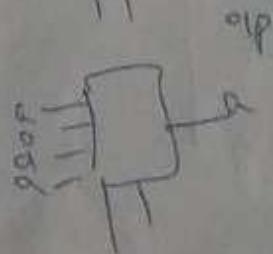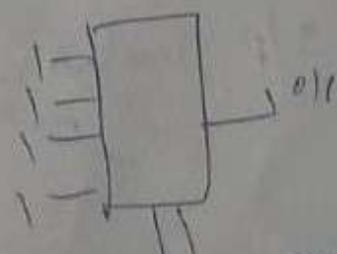

(P) Relationship b/w select lines and products of a MUX

$$F(A, B, C) = \Sigma(2, 3, 5, 6, 7) \text{ Implement using MUX}$$

a)  $S_1 = B, S_0 = C$

b)  $S_1 = C, S_0 = B$

(a)  $(2, 3, 5, 6, 7) = \overline{A} \underline{B} \overline{C} + \overline{A} \underline{B} C + A \overline{B} C + A \overline{B} \overline{C} + A B C$

$$\begin{array}{c} S_1 \quad S_0 \\ \hline B \quad C \end{array} = \overline{B} \overline{C}(0) + \overline{B} C(A) + B \overline{C}(\underline{\overline{A}} + A) + B C(\overline{A} + A)$$

$$= \overline{B} \overline{C}(0) + \overline{B} C(A) + B \overline{C}(1) + B C(1)$$

$$\Rightarrow S_0 = 0; I_0 = A; I_1 = 1; I_2 = 1$$

(b)  $S_1 = C, S_0 = B$

$$\begin{array}{c} C \\ \hline S_1 \quad S_0 \end{array}$$

$$I_0 = 0 \quad 0 - \overline{C} \overline{B} \quad \left| \begin{array}{l} S_0 = 0 \\ I_1 = 1 \end{array} \right.$$

$$I_1 = 0 \quad 1 - \overline{C} B \quad \left| \begin{array}{l} I_0 = 1 \\ I_2 = A \end{array} \right.$$

$$I_2 = 1 \quad 0 - C \overline{B} \quad \left| \begin{array}{l} I_1 = 1 \\ I_0 = 1 \end{array} \right.$$


$$I_3 = 1 \quad 1 - C B \quad \left| \begin{array}{l} I_2 = 1 \\ I_1 = 1 \end{array} \right.$$

$\cancel{\rightarrow}$  If we ~~change~~ change selects then may change I/P values

(18) cascading Multiplexers Ex1:- ( $L \rightarrow R$ )

what is the function in canonical SOP?

(18)

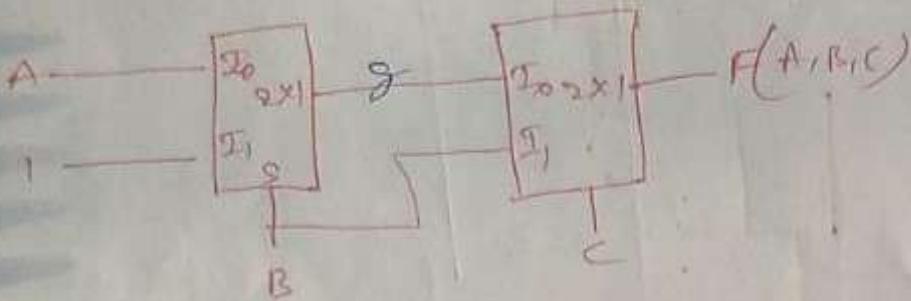

$$y = \bar{B}A + B \cdot 1 = \bar{B}A + B$$

$$F = \bar{C}S + CI_1$$

$$= \bar{C}(\bar{B}A + B) + CB$$


$$= A\bar{B}\bar{C} + \bar{B}\bar{C} + BC$$

$$= \underset{100}{A\bar{B}\bar{C}} + \underset{\bar{A}\bar{B}\bar{C}}{\cancel{A\bar{B}\bar{C}}} + \underset{010}{A\bar{B}C}$$

$$= \Sigma(4, 6, 2, 7, 3)$$

$$= \underline{\Sigma(2, 3, 4, 6, 7)} = \pi(0, 1, 3)$$

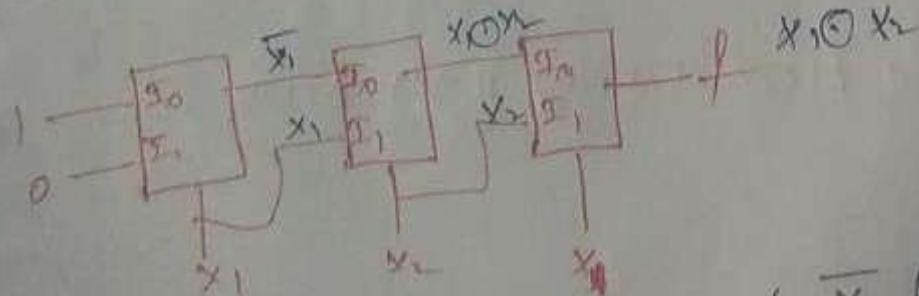(19) cascading Multiplexers Ex2:- ( $L \rightarrow R$ )




$$\begin{aligned} &= \bar{x}_1 \cdot 1 + x_1 \cdot 0 \quad \left| \begin{array}{l} \bar{x}_1 \bar{x}_1 + x_2 x_1 \\ = x_1 \oplus x_2 \end{array} \right. \\ &= \bar{x}_1 \quad \left| \begin{array}{l} \bar{x}_1 (\bar{x}_1 \bar{x}_2 + x_1 x_2) + x_1 x_2 \\ \bar{x}_1 \bar{x}_2 + x_1 x_2 = x_1 \oplus x_2 \end{array} \right. \end{aligned}$$

20

answering MNX Ex 3 :-

19

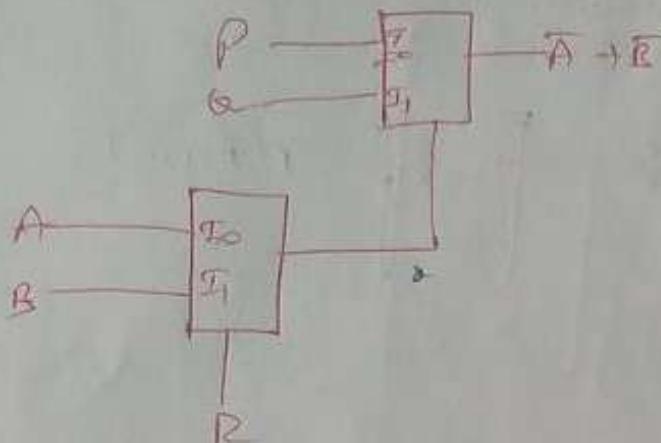

P, Q, R?

$$x = \bar{R}A + RB$$

$$\begin{aligned} & \cancel{\bar{P} + \bar{Q}} \\ & \cancel{(\bar{P}A)P + (\bar{B}A \rightarrow RB)} \\ & = (\bar{R}A + RB)'P + (\bar{R}A + RB)Q \\ & = (\bar{R} + \bar{A})(\bar{R} + \bar{B})P + (\bar{R}A + RB)Q \\ & = R\bar{B}P + \bar{A}\bar{R}P + \bar{A}\bar{B}P + A\bar{R}Q + B\bar{A}Q \end{aligned}$$

T.O.

don't solve it like this go through option


21

Expansion of multiplexers :-

Design 8x1 MUX using 2x1 MUX.

8x1 MUX

20

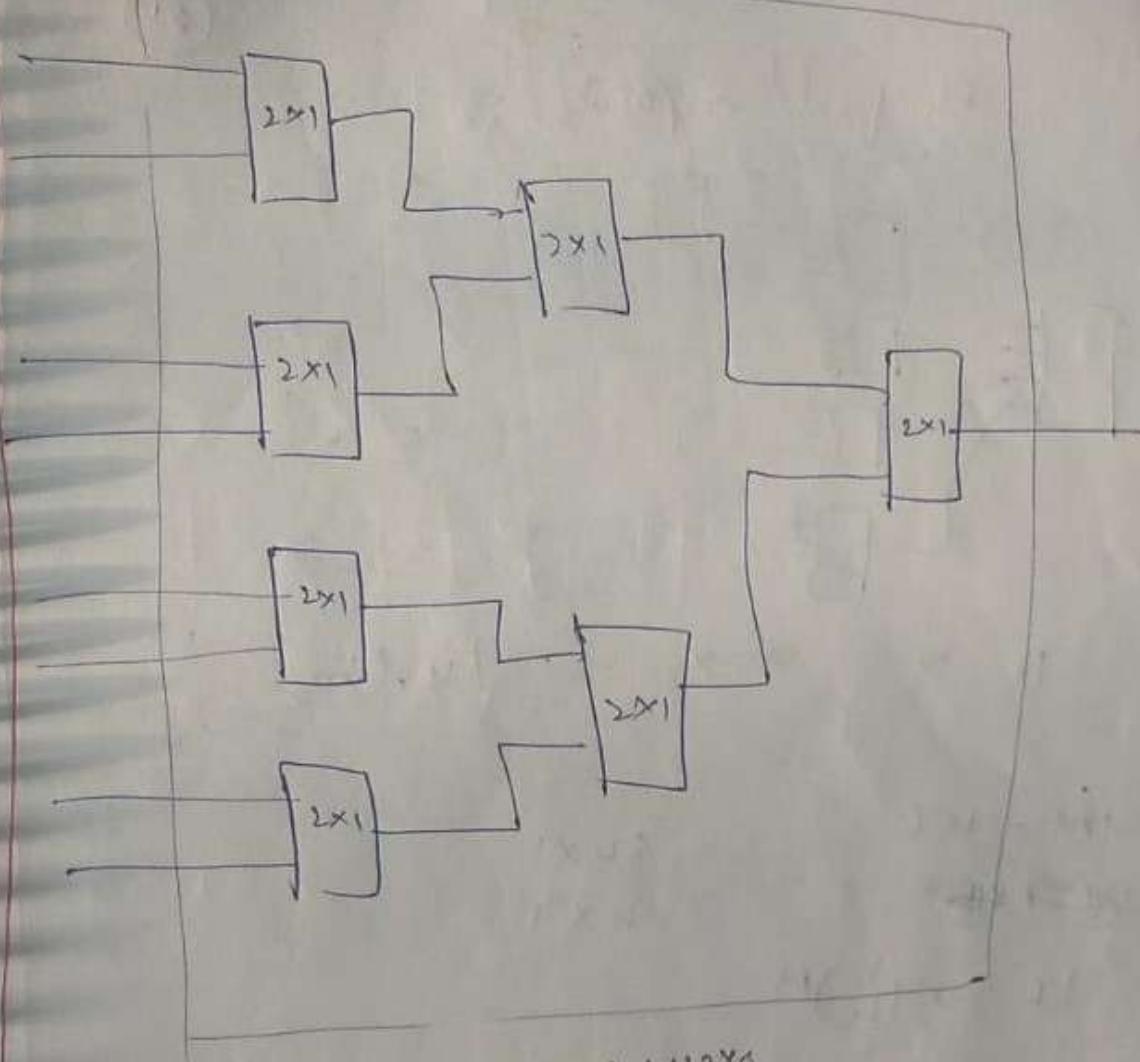

3 levels of 7, 2x1 MUX.

~~8x1 MUX~~  $2 \times 1 M \xrightarrow{\text{conv}} 2 \text{ Lows } \xrightarrow{8 \times 1 UXI}$

$\Rightarrow 1M \rightarrow 2L$

$1L \rightarrow \frac{1}{2}M$

$8L - \frac{8}{2}M \Rightarrow \underline{M}$

$4L - \frac{4}{2}M \Rightarrow \underline{M}$

$2L - \frac{2}{2}M \rightarrow 1M$

$$\text{No. of MUX} = \frac{n+l+1}{2} = 7$$

$M = \text{Multiplexer}$

~~8x1 UXI~~

$1M \rightarrow 2L$

$1L \rightarrow 2M$

$32L - \frac{32}{2}M \rightarrow 8M$

$8L - \frac{8}{2}M \rightarrow 2M$

$4L - \frac{4}{2}M \rightarrow 1M$


$$\text{No. of MUX} = 8 + 1 = 11$$

→ The last mux uses its full capacity.

21

32 × 1

with full capacity

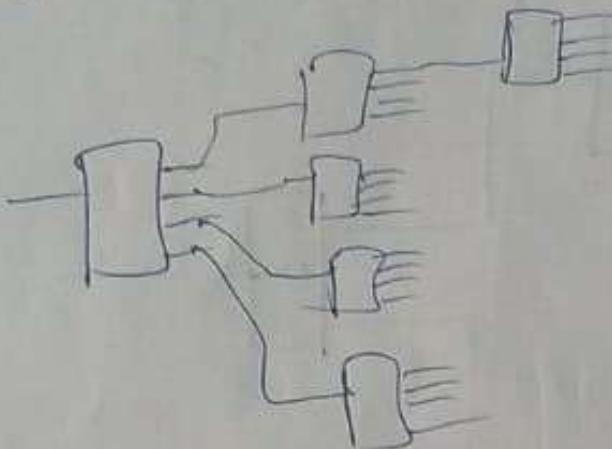

$4 \times 4 \times 4 = 64 \text{ bits}$

$1M - 4L$

~~4L~~

$64 \times 1$

$n \times 1$

$$1L \rightarrow (\frac{1}{4})^M$$

$$64L \rightarrow \frac{64}{4} M = 16M$$

$$16L \rightarrow \frac{16}{4} M = 4M$$

$$4L \rightarrow \frac{4}{4} M = 1M$$

$$\therefore \text{No. of MUX} = 16 + 4 + 1 = 21$$

Even more details

How many levels?

How many MUX's?

Implement  $M \times 1$  MUX using  $N \times 1$  MUX.

(22)

$N \times 1$  MUX covering  $N$  Lines

$$\Rightarrow N \text{ Lines} - 1 \text{ MUX} \quad | \begin{array}{l} N^L = 1M \\ L = (\frac{1}{N})^M \end{array}$$

$$\Rightarrow N^L = \left(\frac{M}{N}\right)^M \text{ MUX}$$

Level 1  $\frac{M}{N}^L = \left(\frac{M}{N} \times \frac{1}{N}\right) \text{ MUX}$

Level 2  $\left(\frac{M}{N} \times \frac{1}{N}\right)^L = \left(\frac{M}{N} \times \frac{1}{N} \times \frac{1}{N}\right) \text{ MUX}$

Level  $\left(\frac{M}{N}\right)^L = \left(\frac{M}{N^k}\right)^{\text{MUX}}$

$$\frac{M}{N^k}$$

when  $\frac{M}{N^k} \leq 1$  then stopped it.

$$\Rightarrow k \geq M$$

$$k \log N \geq M \Rightarrow k \geq \log_N M \Rightarrow k = \lceil \log_N M \rceil$$

No. of MUXs at level  $k = \frac{M}{N^k}$

Total Demultiplexers ( $M_{UX}$ ) =  $\sum_{k=1}^{\lceil \log_N M \rceil} \left( \frac{M}{N^k} \right)$

① 8x1 MUX using 2x1 MUX

$$M = \frac{1}{N}$$

$$\text{No. of levels} = \lceil \log_N M \rceil = \lceil \log_2 8 \rceil = 3$$

$$\text{No. of branches} = \sum_{k=1}^3 \frac{M}{N^k}$$

$$= \frac{8}{2^1} + \frac{8}{2^2} + \frac{8}{2^3} = u + r + 1 = 7$$

② 32x1 MUX using 4x1 MUX

$$\text{No. of levels} = \lceil \log_4 32 \rceil = \lceil \frac{5}{2} \rceil = 3$$

$$\text{No. of branches} = \frac{32}{4^1} + \frac{32}{4^2} + \frac{32}{4^3}$$


$$= 8 + 2 + 1 = 11$$

③ 64x1 MUX using 8x1

$$\text{No. of levels} = \lceil \log_8 64 \rceil = \lceil \frac{6}{2} \rceil = 3$$

$$\text{No. of MUXs} = \frac{64}{8^1} + \frac{64}{8^2} + \frac{64}{8^3} = 16 + 4 + 1 = 21$$

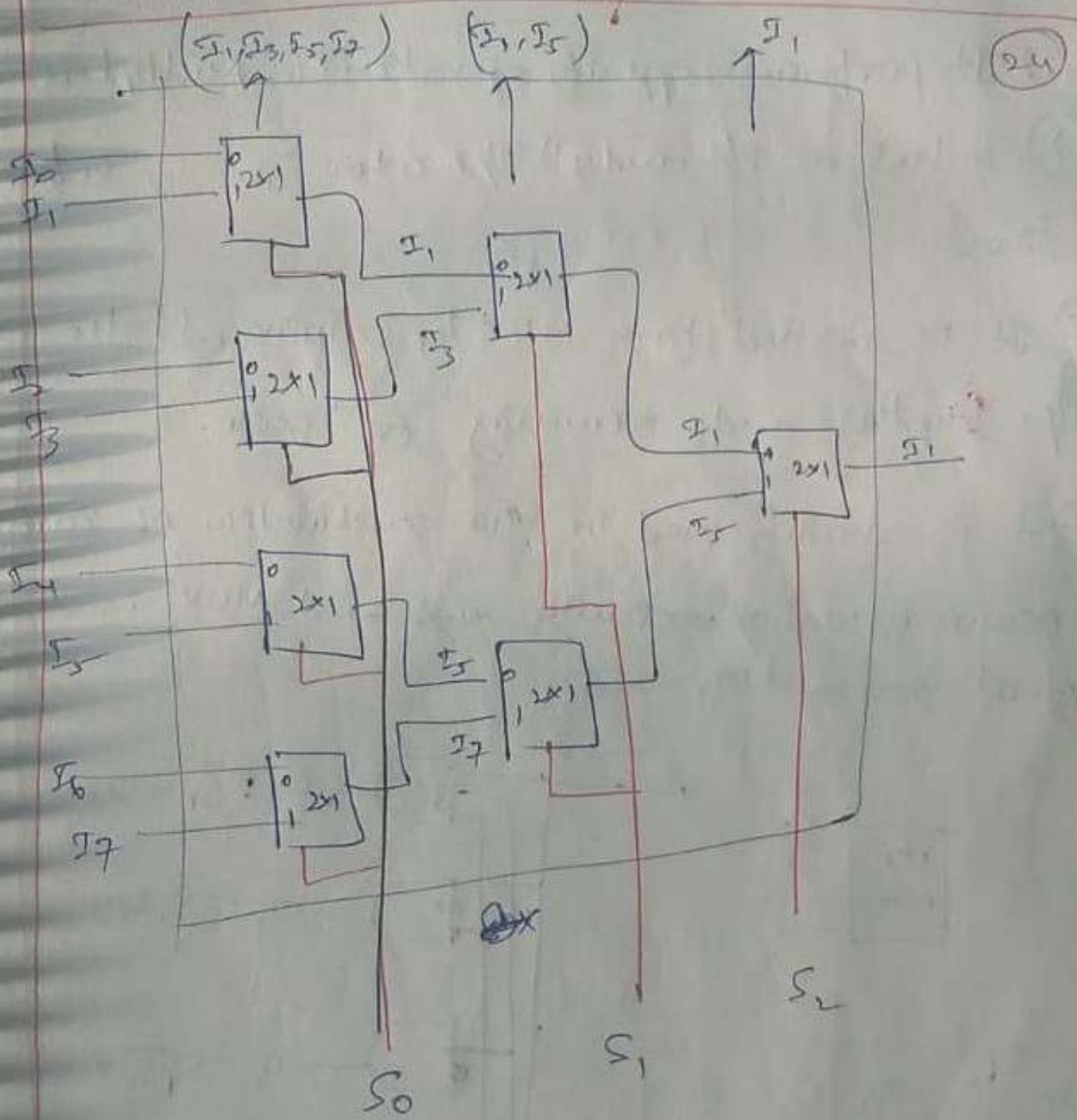21 Assigning Select Lines while expanding the MUX :-



For example :  $S_2 \ S_1 \ S_0$        $\rightarrow I_1$  selected  
      0    0    1

$S_2 \ S_1 \ S_0$        $\rightarrow I_6$  selected  
      1    1    0


$S_0 = 0 \rightarrow I_1 \ I_2 \ I_3$


$S_1 = 1 \rightarrow I_4 \ I_5$

$S_2 = 1 \rightarrow I_6$
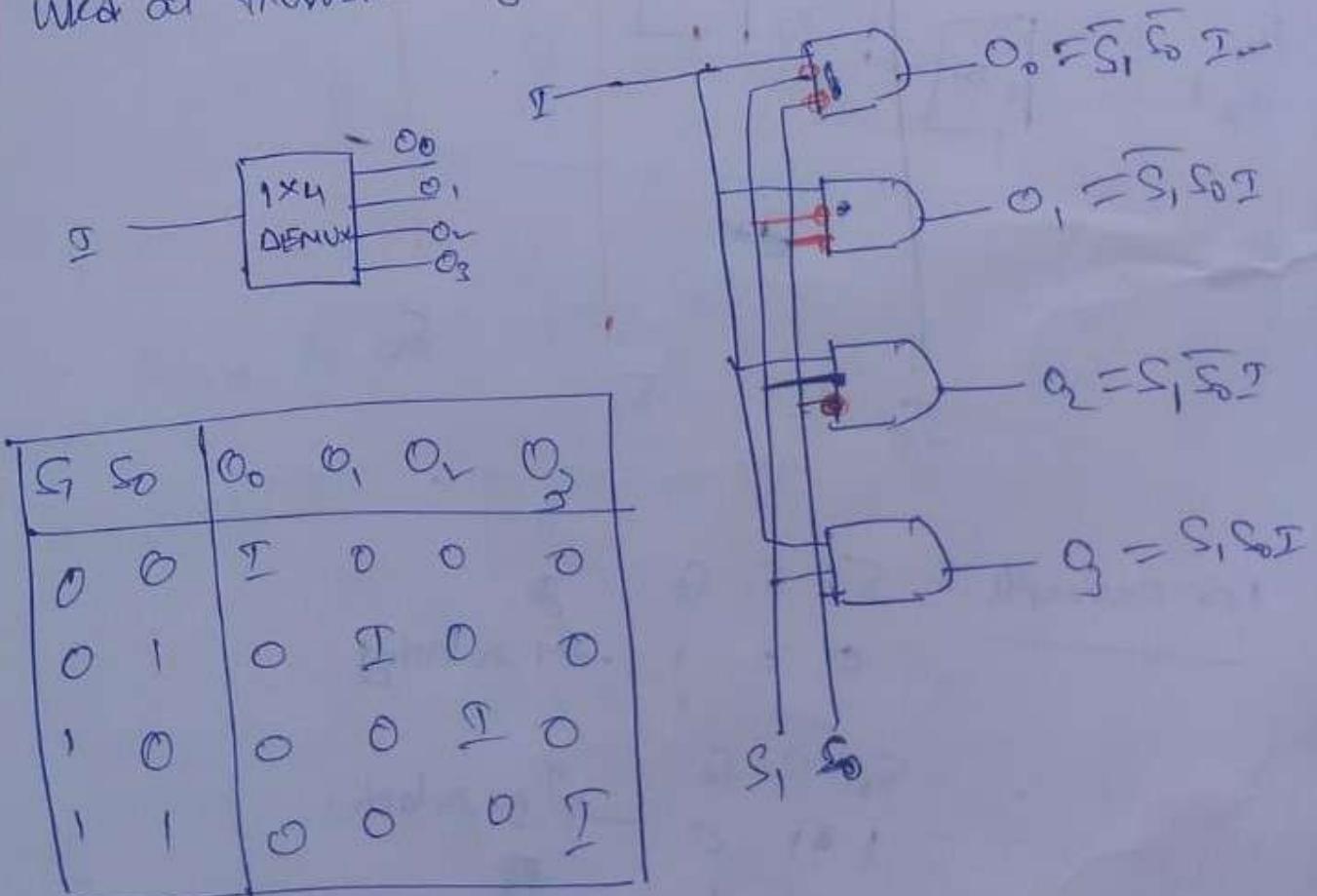
## 29 Introduction to Demultiplexer


- ① It performs opposite operation of multiplexer.
- ② It has one input and  $2^n$  outputs where 'n' is select lines.
- ③ It is derived from MUX by joining all the outputs together and removing 'OR' gate.
- ④ It is mainly used in the construction of switches.
- ⑤ DEMUX is used at receiving end and MUX is used at transmitting end.



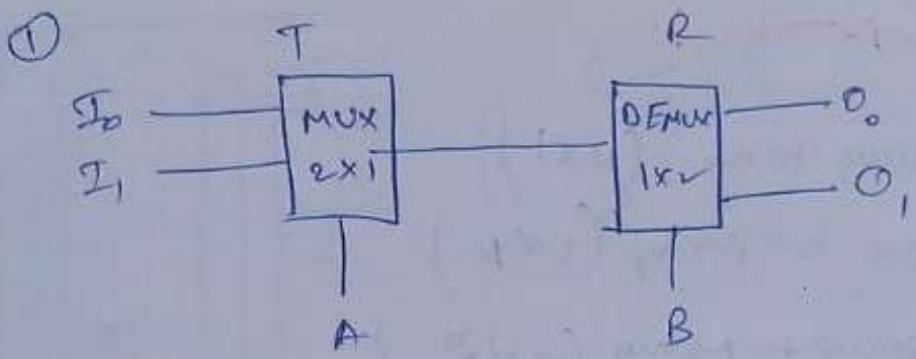


A	B (S.C.)
0	$(I_0 \rightarrow O_0)$
0	$(I_0 \rightarrow O_0)$
1	$(I_1 \rightarrow O_0)$
1	$(I_1 \rightarrow O_1)$

add connection (C.C.)

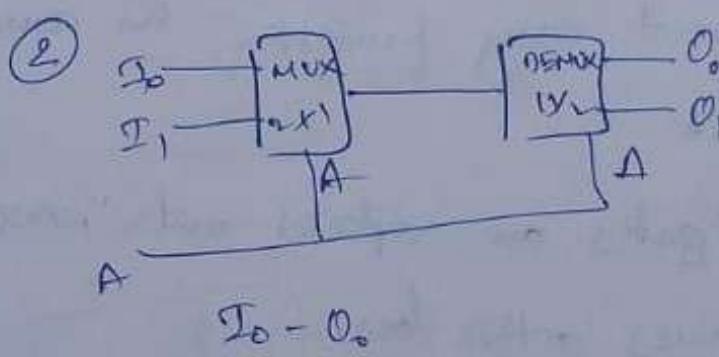


Straight connection

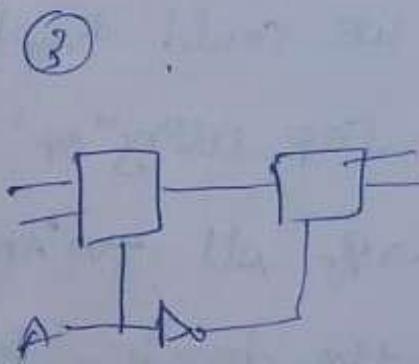

$I_0 \rightarrow O_1$   
 $I_1 \rightarrow O_0$

Cross connection

④ SC & CC

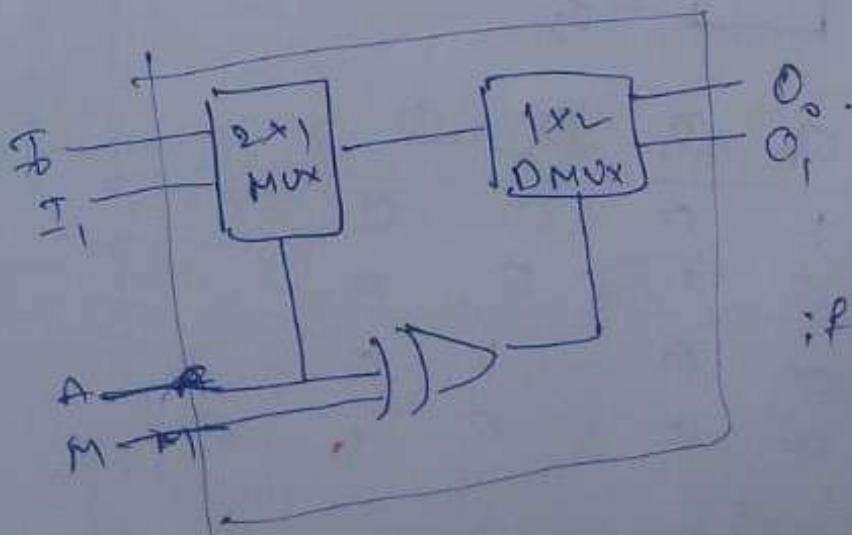

$f_N = 0 - SC$   
 $M = 1 - CC$


## ④ Sequential Circuits

51

①
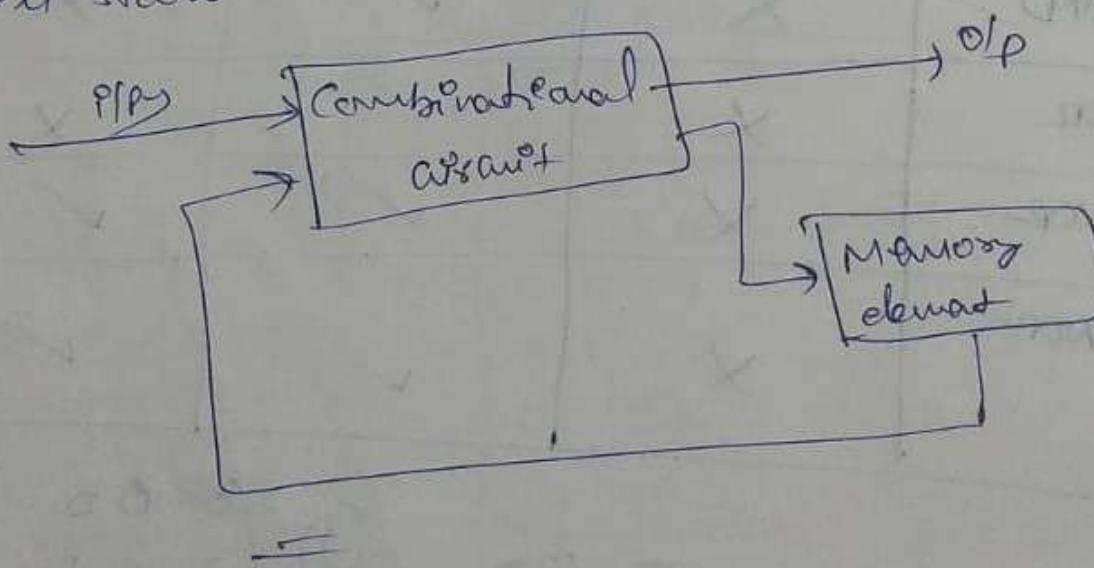
### ① Introduction:-

- ① The external O/p of a Sequential circuit depends on external I/p's and on present contents of "memory elements".
- ② The present contents of the memory elements are called present state and the new contents of memory elements are obtained by taking external I/p's and present state. This is called next state.



②


### Latch and Flip-Flop :-

- ① A 1 bit memory cell is a memory stored in some medium in which one bit of information can be stored (or) returned until necessary and thereafter its contents can be replaced by

new values.

- ② The basic building block of digital memory circuit  
is known as flip-flop.

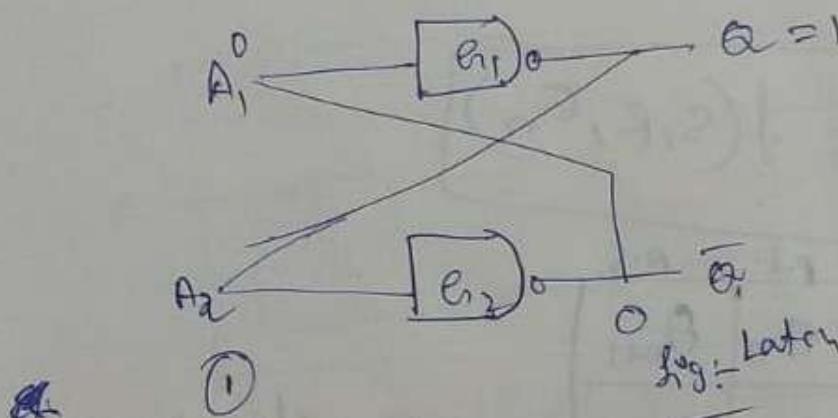- ③ It has 2 stable states which are known as '1' & '0'. so it is also called Bi-stable Multi-vibrator.




→ Latch means Latch.

if Q=1 then A<sub>1</sub>=1  $\Rightarrow$  Q̄=0  $\Rightarrow$  A<sub>2</sub>=1  $\Rightarrow$  Q=1  
until the S/P changes the Q/P does not change

→ Using latch we build a FF.

③

SR FF:-

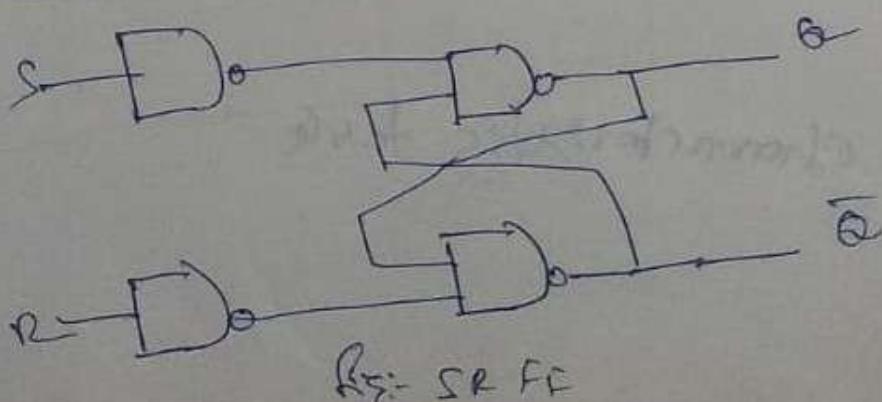


$$Q_n \rightarrow Q_{n+1}$$

③

Present State      Next State

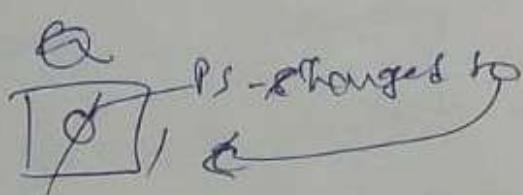Actually there are same state. that means



O  $\rightarrow$  1

$$Q_{n+1} = f(S, R, Q_n)$$

S	R	Q <sub>n</sub>	Q <sub>n+1</sub>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	?
1	1	1	?

P.S.      P.S.      N.S.

No change (J) Latch  
 $Q_{n+1} = Q_n$

Reset (making it 0)

Set (making it 1)

Indeterminate state  
 (R)  
 Invalid state.

Fig: characteristic table


$Q_n$	00	01	11	10
0	0	0	1	1
1	1	1	0	0

(4)

$Q_n$	00	01	11	10
0	0	0	0	1
1	1	1	0	0

~~$S\bar{R} + Q_n\bar{R}$~~
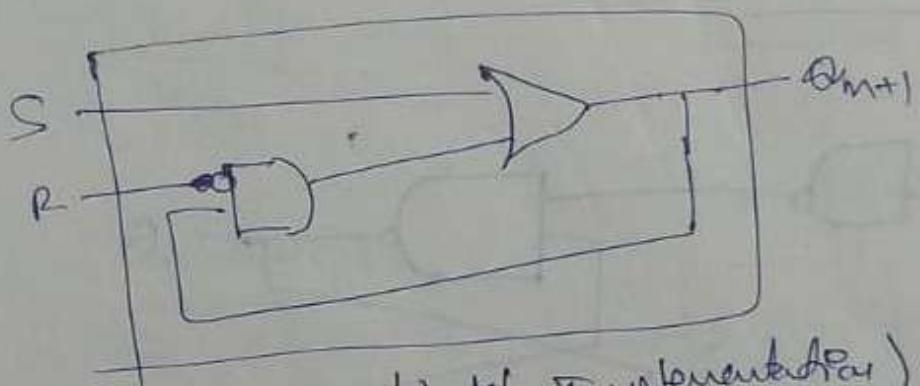
$$\Rightarrow Q_{n+1} = S + Q_n\bar{R} \rightarrow \text{characteristic equation}$$



(realistic Implementation)

Excitation table:




$Q_n$	$Q_{n+1}$	$S$	$R$
0	0	0	0
0	1	1	0
1	0	0	1
1	1	0	0

function table :-

S	R	$Q_{n+1}$
0	0	$Q_n$
0	1	0
1	0	1
1	1	∅

- (3)
- i) FF diagram
  - ii) characteristic table
  - iii) characteristic equation
  - iv) realization
  - v) Excitation table
  - vi) function table.




(4) clocked FFs:-

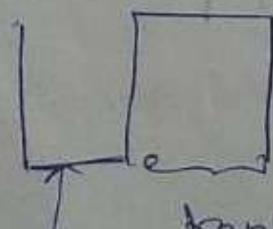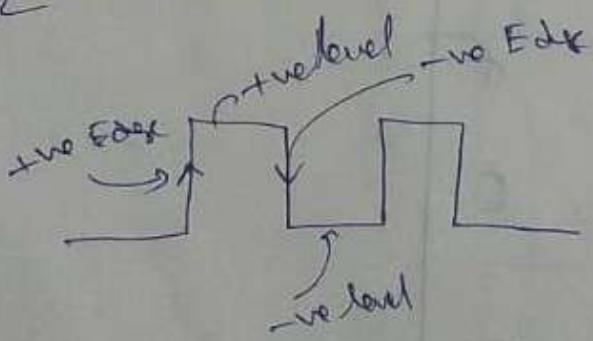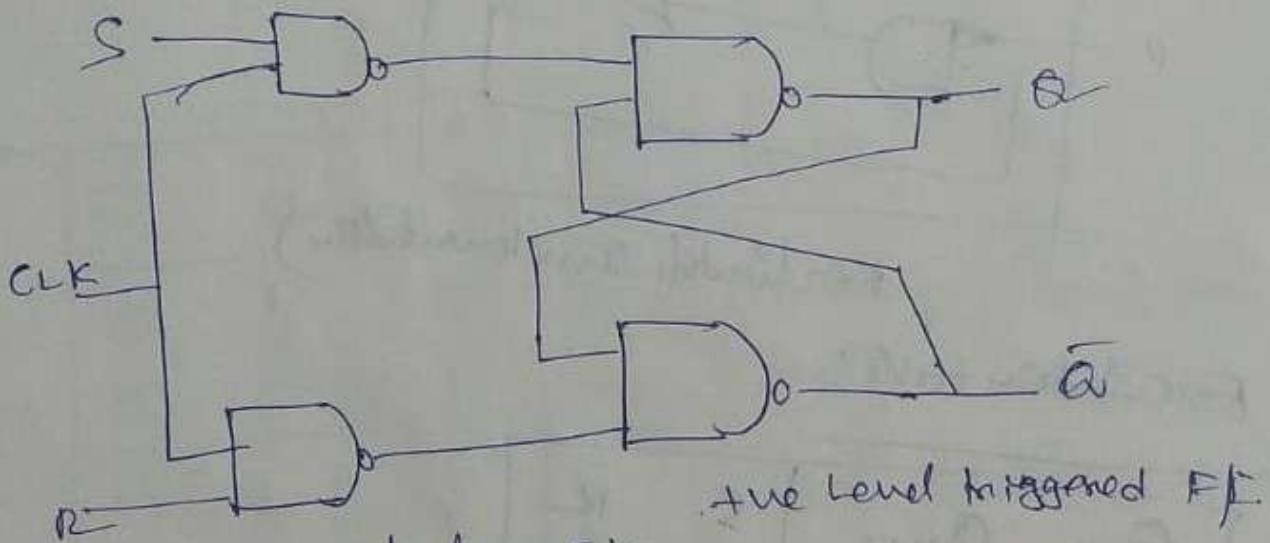

transparent Mode  
flip effects the Qp  
Latch mode

→ The FF which triggered at the level >  
called as +ve level FF.

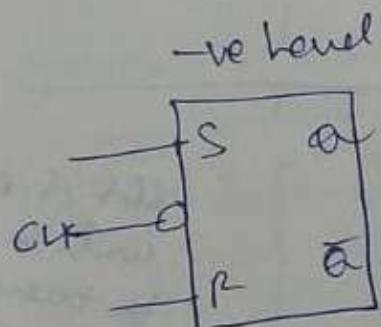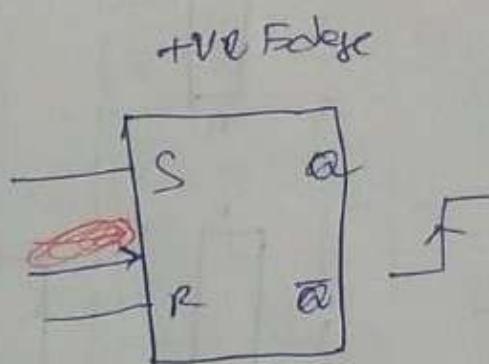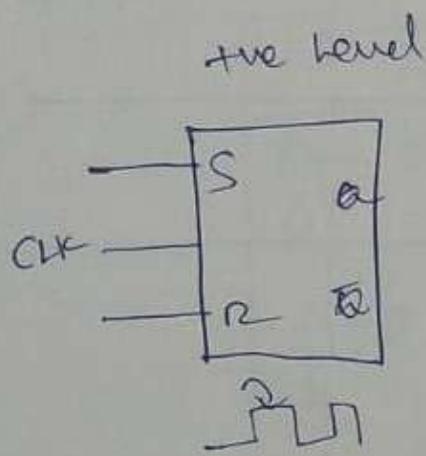
→ Most popular FFs are Edge triggered FB.




⑤ Positive Level Triggered. :-



Transposed Mode  
Latch Mode

TM: FF most  
LM: FF ~~most~~ Latched.

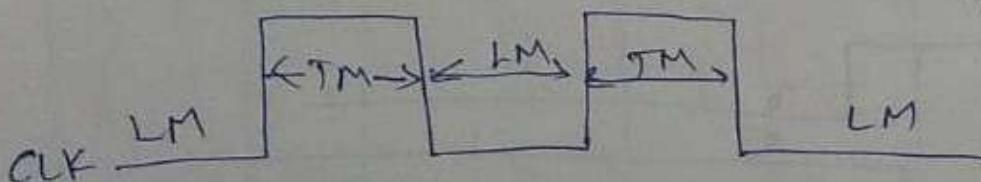

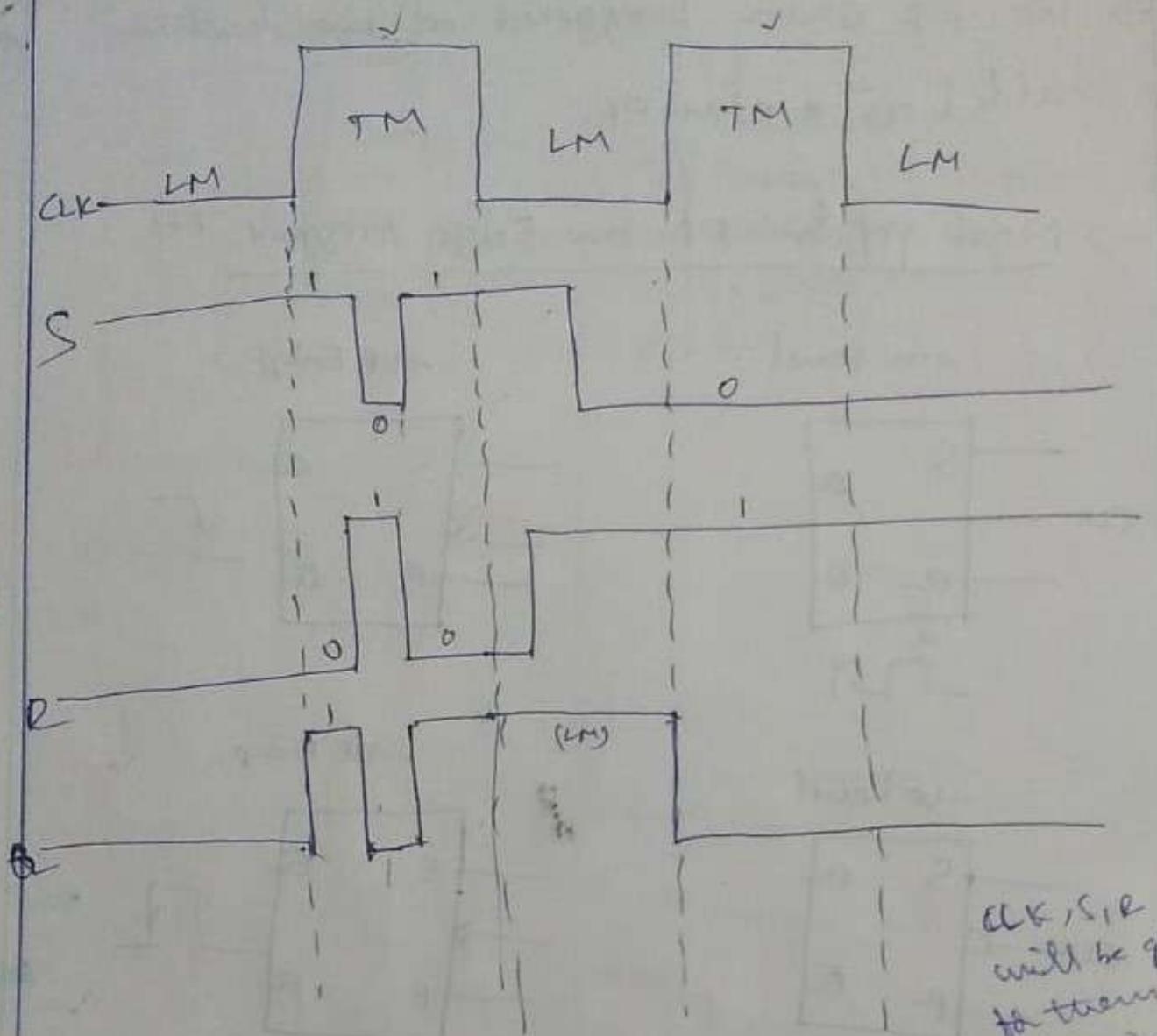

(6) Edge Triggered FF:- +ve Edg

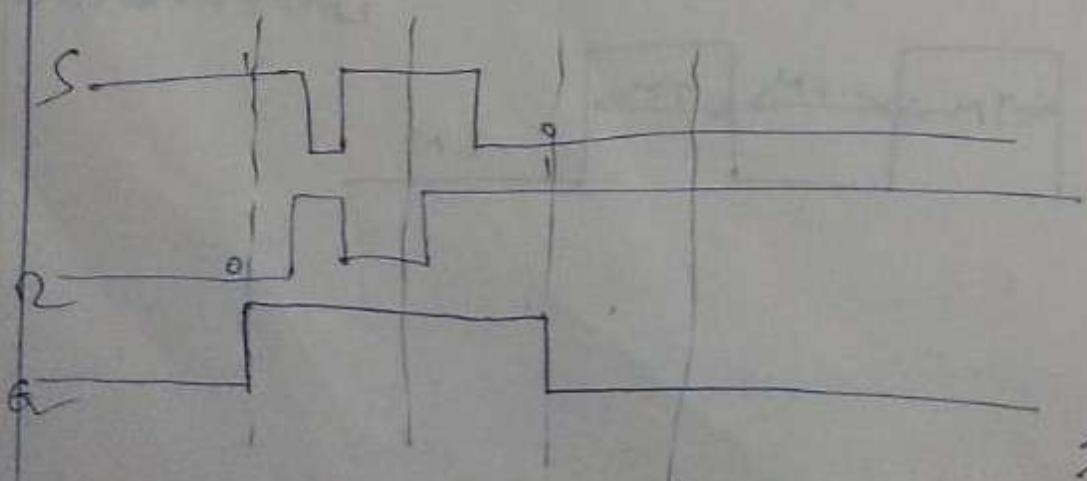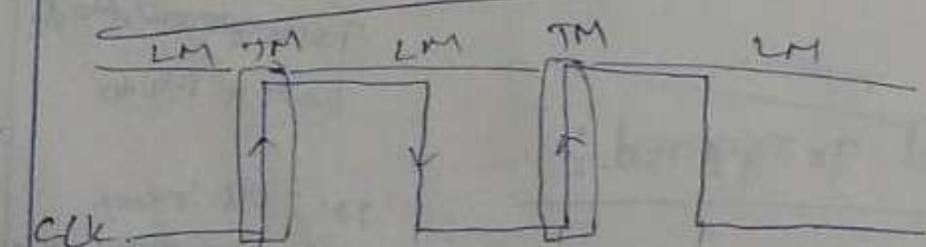

## ⑦ JK Flip Flop:-

- JK FF is same as SR FF ( $J=S$ ,  $K=R$ ). It is defined for  $J=K=1$  also and the FF performs complementation.

Function table:-

J	K	$Q_{n+1}$
0	0	$Q_n$
0	1	0
1	0	1
1	1	$\bar{Q}_n$

Characteristic table :-

J	K	$Q_n$	$Q_{n+1}$
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Characteristic Sequence:-


JK	00	01	11	10
$Q_{n+1}$	0	1	1	0
$Q_n$	1	D	D	1

$$Q_{n+1} = \bar{Q}_n J + Q_n K$$


$$\Rightarrow Q_{n+1} = J \bar{Q}_n + K Q_n$$

Excitation table:-

$Q_n$	$Q_{n+1}$	J	K
0	0	0	0
0	1	1	0
1	0	0	1
1	1	0	0

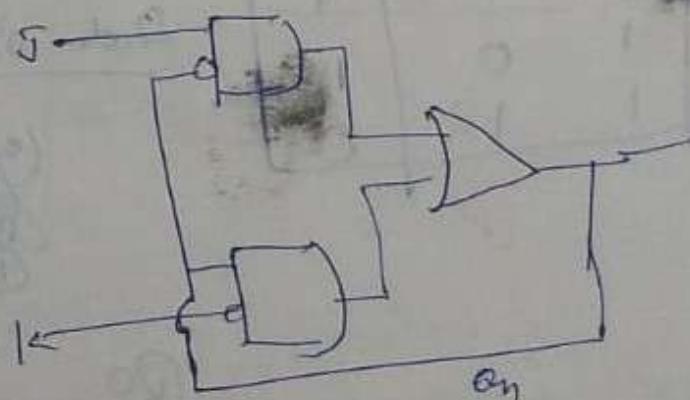


State Diagram: - (From Q)

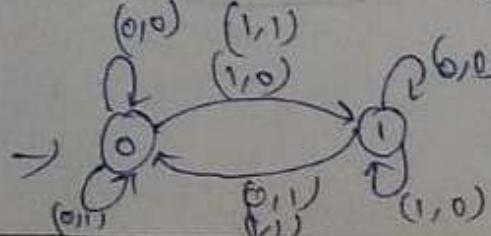

for Implementation

(8)

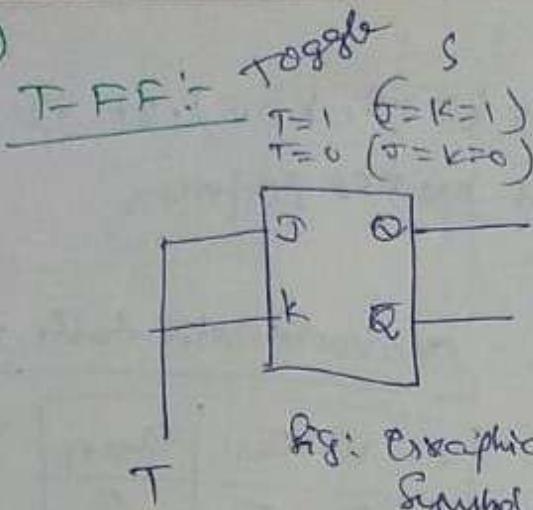function table

T	$Q_{n+1}$
0	On
1	On

latching  
complementer

so called as Toggle FF

Characteristic table :-

T	$Q_n$	$Q_{n+1}$
0	0	0
0	1	1
1	0	1
1	1	0



Characteristic equation

$$Q_{n+1} = T Q_n + T \cdot \bar{Q}_n$$

$$\overline{Q_{n+1}} = T \oplus Q_n$$

Excitation table :-

$Q_n$	$Q_{n+1}$	T
0	0	0
0	1	1
1	0	1
1	1	0

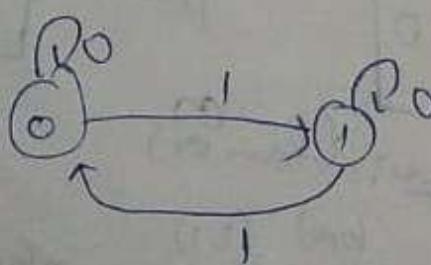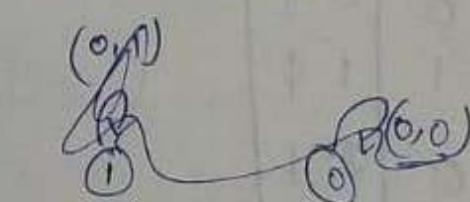State Diagram

(9)


function table

T	$Q_{n+1}$
0	On
1	On

latching  
complementer

so called as Toggle FF

⑥

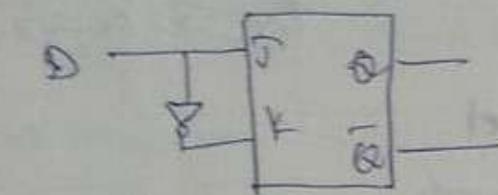
D-FF :-

$$D = 0 \quad (J=0; K=1)$$

$$D = 1 \quad (J=1; K=0)$$

Characteristic table :-

D	$Q_n$	$Q_{n+1}$
0	0	0
0	1	0
1	0	1
1	1	1

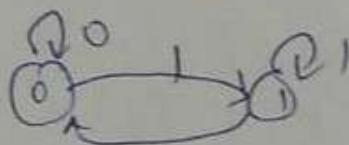State Diagramm :-Excitation table :-

$Q_n$	$Q_{n+1}$	D
0	0	0
0	1	1
1	0	0

Functional table :-

D	$Q_{n+1}$
0	0
1	1

Characteristic equation :-

$$Q_{n+1} = D\bar{Q}_n + DQ_n$$

~~$$= D(\bar{Q}_n + Q_n) = D$$~~

$$\therefore Q_{n+1} = D$$



∴ called as Buffer (delay).

Example in flip flop :-

Q6 the characteristic equation of a FF

$Q_n = \bar{x}_1 \bar{Q} + \bar{x}_2 Q$ . Define the behaviour of that.

Sol:- function table :-

11

$x_1$	$x_2$	$Q_n$
0	0	1 - set
0	1	$\bar{Q}$ - toggle
1	0	$Q$ - latch
1	1	0 - reset

$$Q_n = \bar{x}_1 Q + x_2 \bar{Q}$$


characteristic table:-

excitation table:-

$x_1$	$x_2$	$Q$	$Q_n$
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

$Q$	$Q_n$	$x_1$	$x_2$
0	0	1	0
0	1	0	0
1	0	0	1
1	1	0	0


State Diagram

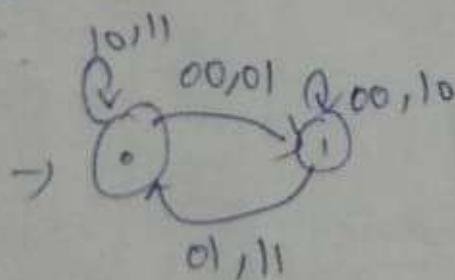

Q

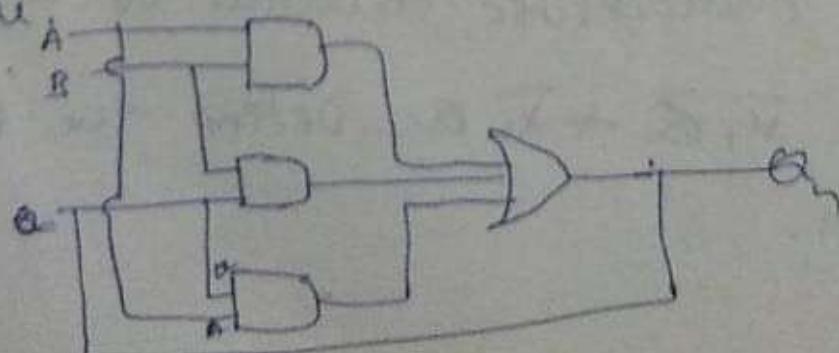Example:-

consider the following realization. construct excitation table.



$$\text{Set } Q_n = AB + BA + AA$$

$$Q_n = AB + (B+A)A$$

~~desired function table :-~~

Characteristic table:-

A	B	$Q_n$
0	0	0
0	1	0
1	0	0
1	1	1

Reset

Latching

Latching

Set

A	B	$Q_n$
0	0	0
0	1	0
1	0	0
1	1	1
1	0	0
0	1	1
1	1	1

State diagram:-

Excitation table:-

$Q_n$	$Q_n$	A	B
0	0	0	0
0	1	1	0
1	0	0	0
1	1	1	0
0	0	1	0
1	1	0	1

Excitation table

$Q_n$	$Q_n$	A	B
0	0	0	0
0	1	1	0
1	0	0	0
1	1	1	0

00 -> 00

10 -> 10


00 -> 00, 01  
11 -> 01, 10, 11

00 -> 00, 01  
11 -> 01, 10, 11

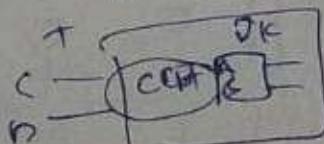(12)

Introduction to FF Inter Conversion:-


- ① Get the characteristic table of the target FF.
- ② Replace the next state using excitation of the given FF.
- ③ Obtain the expression for the S/P or the given FF and realize them.




JK  $\rightarrow$  T FF

T	$Q_n$	$Q_{n+1}$	J	K
0	0	0	0	0
0	1	1	0	0
1	0	1	1	0
1	1	0	0	1

for J

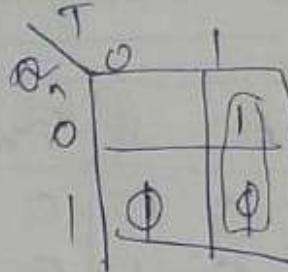


for K

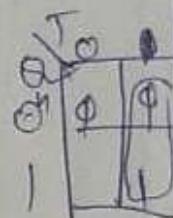


$J = T$

$K = T$

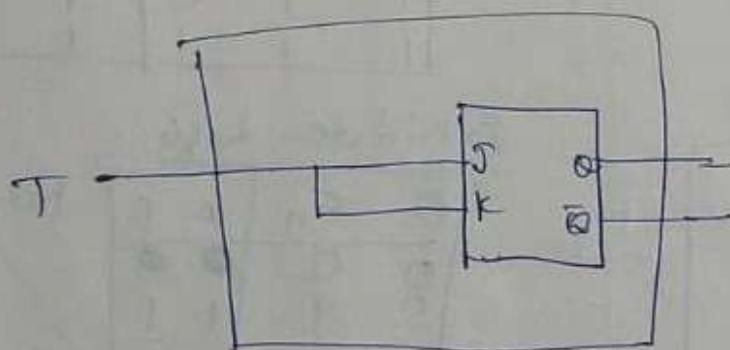

TFF  $\rightarrow$  JK FF:-

Conversion (Combinational  
ckt wkd)

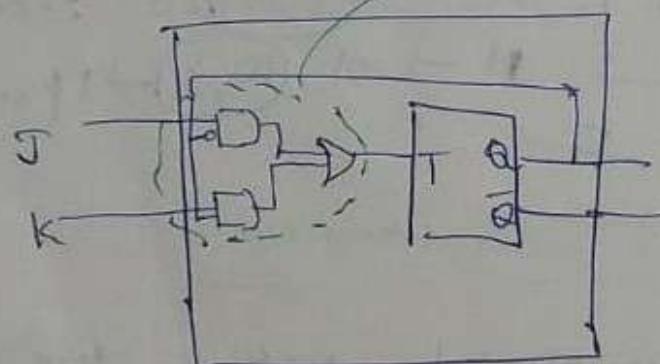

for T

J	K	$Q_n$	$Q_{n+1}$	T
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	1
1	0	1	0	0
1	1	0	1	1
1	1	1	0	1


$Q_n$	00	01	11	10
0	1	0	1	0
1	0	1	0	1

$$T = \bar{J}Q_n + KQ_n$$
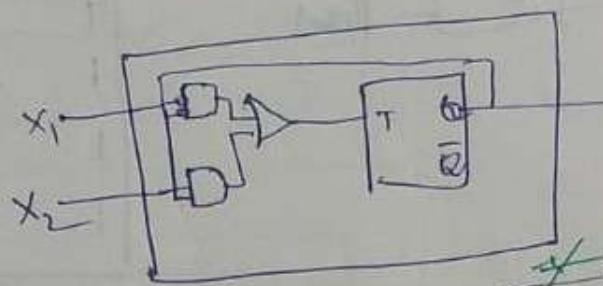
### (13) Interconversion of FF

A new FF  $x_1, x_2$  has characteristic exp.

$$Q_n = \bar{x}_1 \bar{Q} + x_2 Q. \text{ realize it with T-FF.}$$



\* excitation func.

function-table:-

$x_1$	$x_2$	$Q_n$
0	0	1
0	1	0
1	0	0
1	1	0

set  
com toggle  
Reset

$x_1$	$x_2$	$Q$	$Q_n$	T
0	0	0	1	1
0	0	1	1	0
0	1	0	1	1
0	1	1	0	1
1	0	0	0	0
1	0	1	1	0
1	1	0	0	0
1	1	1	0	1


$x_1, x_2$	00	01	11	10
$Q_n$	1	1		
1	1	1		

$$T = \bar{x}_1 \bar{Q} + x_2 Q$$

\* characteristic table.

(14)  $x_1, x_2 \rightarrow T$  FF Ex



$$Q_n = \bar{x}_1 \bar{Q} + x_2 Q.$$

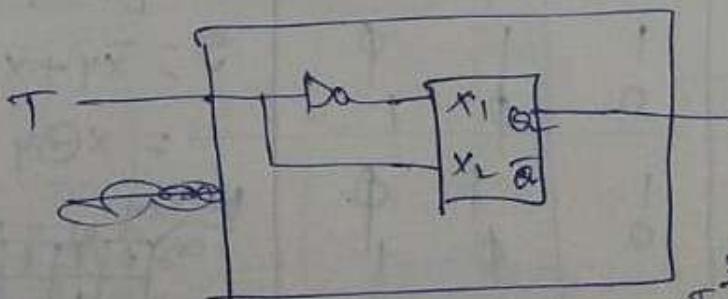

T	Q	$Q_n$	$x_1, x_2$
00	0	0	0 0
01	1	0	0 1
10	1	1	1 0
11	0	1	1 1

function-table

$x_1$	$x_2$	$Q$	$Q_n$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

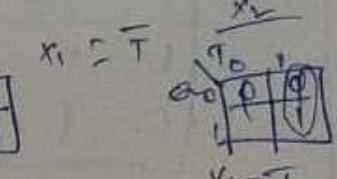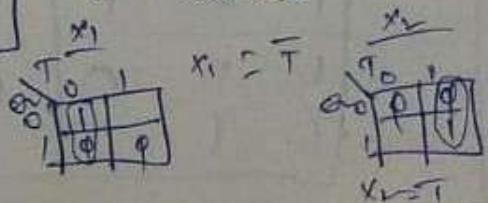



## Function table of $X_1 X_2$

$X_1$	$X_2$	$Q_n$	
0	0	1	Set
0	1	0	Reset
1	0	0	Latch
1	1	0	Reset

## Characteristic table of $X_1 X_2$ (15)

$X_1$	$X_2$	$Q$	$Q_n$
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	0	0
1	1	1	0
1	1	0	0

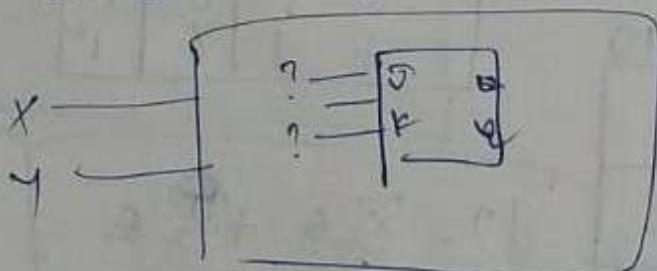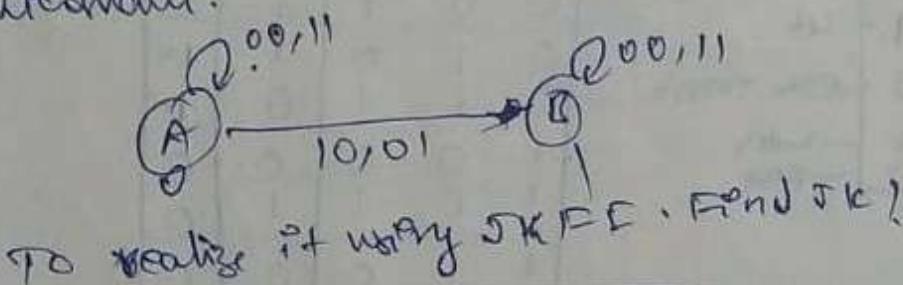(15) An  $X, Y$  FF is represented by the following state diagram.



$X$	$Y$	$Q_n$	$Q_{n+1}$	$J$	$K$
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	1	0
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	0	0	1
1	1	0	0	0	0
1	1	1	1	0	0

$\overline{Q_n}$	00	01	11	10
0	1	1	1	1
1	0	0	0	0

$$\begin{aligned} J &= \overline{X}Y + X\bar{Y} \\ &= X \oplus Y \end{aligned}$$

$\overline{Q_n}$	00	01	11	10
0	0	0	1	1
1	1	1	0	0

$$K = X \oplus Y$$


XN FF function table :-

x	y	$Q_{n+1}$
0	0	$Q_n$
0	1	$\bar{Q}_n$
1	0	$\bar{Q}_n$
1	1	$Q_n$

XN FF GT:-


(16)

~~$J \neq K \text{ or } Q_{n+1}$~~

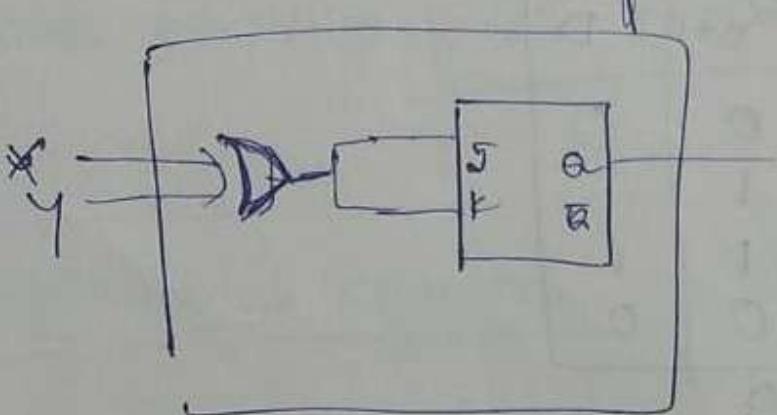

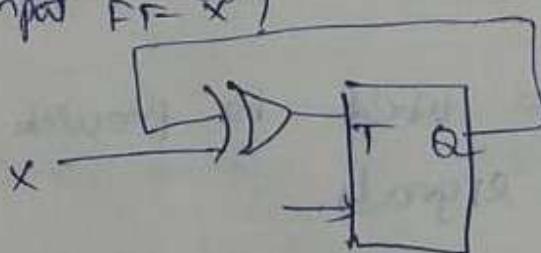(16) Ex

What is the behaviour of the following  
one-input FF ( $x$ )?




- DFF       T FF       Inverted DFF       Inv. TFF

Characteristic table :-

x	$Q_n$	$Q_{n+1}$	T
0	0	0	0 - entry
0	1	0	1
1	0	1	0 - entry
1	1	1	0 - exit

$$T = x \oplus Q_n$$

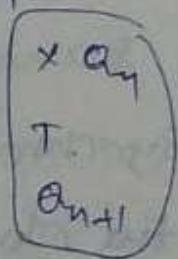


calculate  
process.

$\uparrow$   
DFF

m

(17)

Ex5

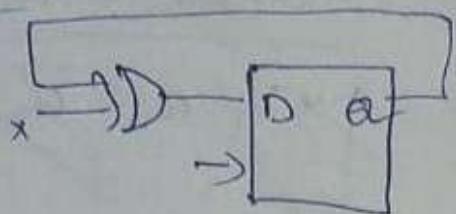

- a) OFF      b) T FF      c) Inv. OFF      d) Inv. T FF

 $x \text{ ET} \downarrow$ 

$x$	$Q_n$	$Q_{n+1}$	D
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

$$P = x \oplus Q_n$$

(18)

## Introduction to counters

- The counters are used to provide accurate timing and control signals.
- There are of two types:
  - a) Synchronous      b) Asynchronous
- In synchronous counters, all the FF responds to the same clock instance.
- In asynchronous counters, the output of one FF drives the clock of another FF.
- Synchronous counters are faster than Asynchronous counters.

→ Due to simplicity of design, Asynchronous counters are used in IC fabrication. (18)


→ The simplified version of synchronous counter is called shift counter.

→ The basic element in shift counter is D-FF.

→ The Ring counter and Johnson counter are further simplified version of shift counter.

### (19) Asynchronous and Synchronous counters:-

Synchronous counter:-

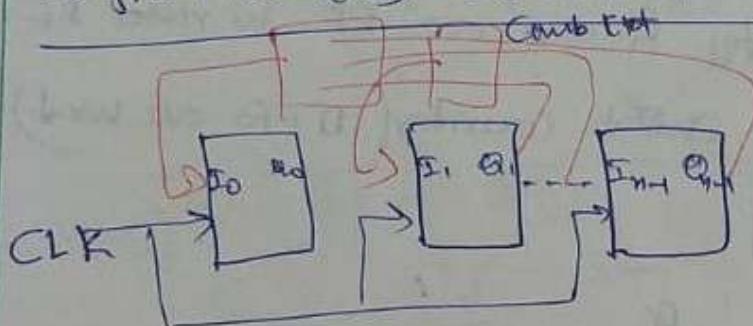


Propagation delay in synchronous counter is,

$$T_{pd\text{syn}} = T_{ff} + T_{\text{combinational}}$$

$$\therefore T_{clk} \geq T_{pd\text{syn}}$$

Asynchronous counter:-

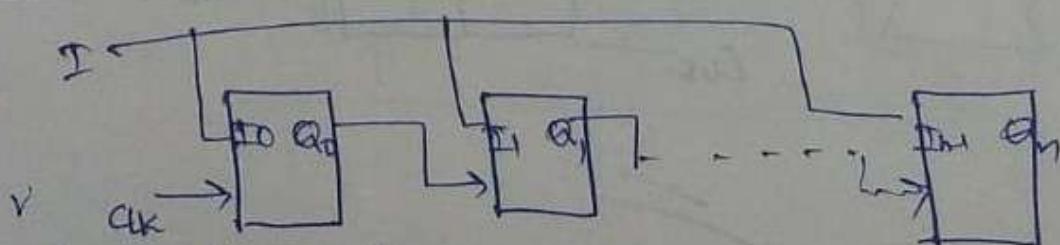

Propagation delay in Asynchronous counter is

$$T_{pd\text{asyn}} = N * T_{ff} + T_{\text{combinational}} \Rightarrow T_{clk} \geq T_{pd\text{asyn}}$$

## Q. Shift Counters:-

$$\rightarrow I_p = f(Q_0, Q_1, \dots, Q_{N-1}) ; 0 \leq p \leq N-1$$

$\rightarrow$  Its design is more complex. So simplification are done as follows:

$$\textcircled{i} \quad I_p = Q_{p-1} : 0 \leq p \leq N-1$$


$$I_1 = Q_0$$

$$I_2 = Q_1$$

$$I_3 = Q_2$$

 $\vdots$ 

$$I_N = Q_{N-1}$$

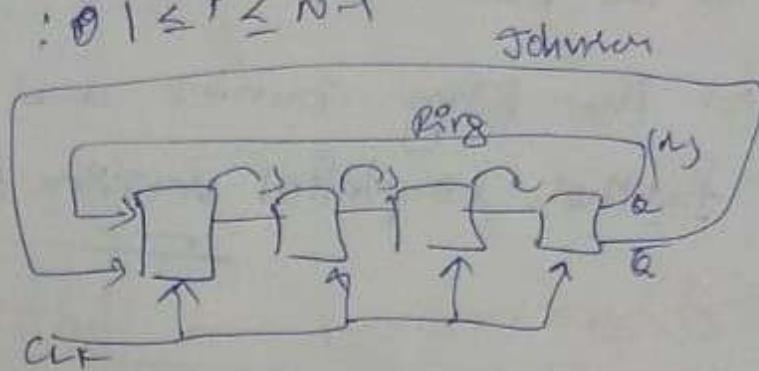

Johnson

Here, data is shifted from one FF to next FF.  
So this is called shift counter (D FFs are used).

$$\textcircled{ii} \quad I_0 = f(Q_{N-1})$$



$$I_0 = f(Q_{N-1})$$

$$I_0 = Q_{N-1}$$


(Ring counter)

$$I_0 = \overline{Q_{N-1}}$$

(Johnson  
counter)

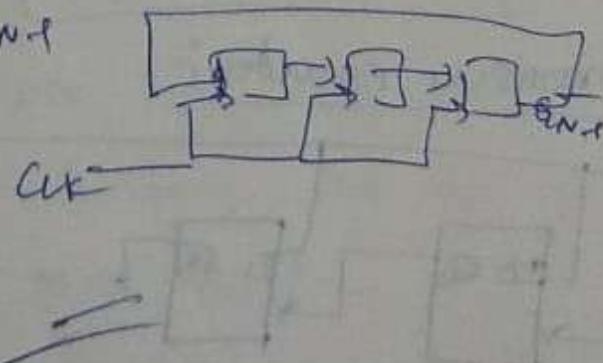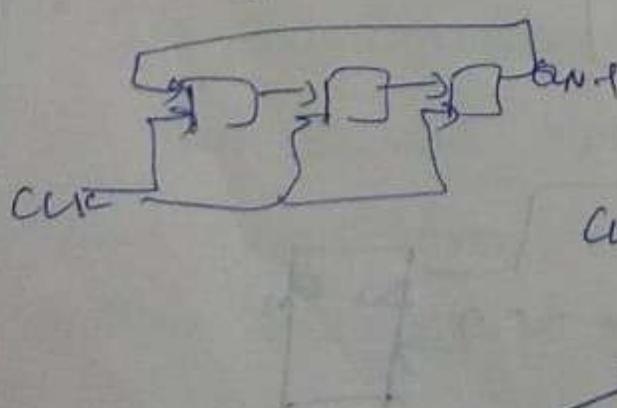

## (21) Mod 2 Ring Counter:

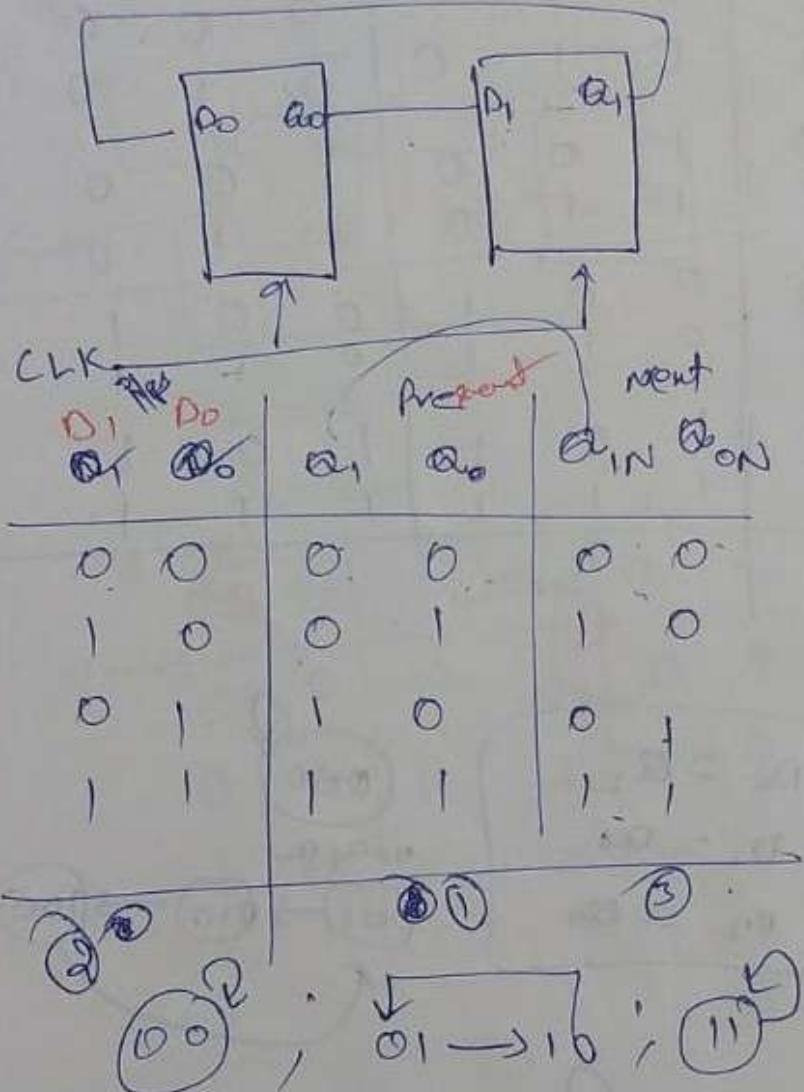

$P_S \rightarrow S/P \rightarrow N.S.$   
N.S.  
 $P_S \rightarrow S/P$

$$D_0 = 01$$


$$D_1 = 00$$

$N = \text{no. of states}$

mod 2 nearly divisible by 2

mod 2

## (22) Mod 3 Ring Counter:

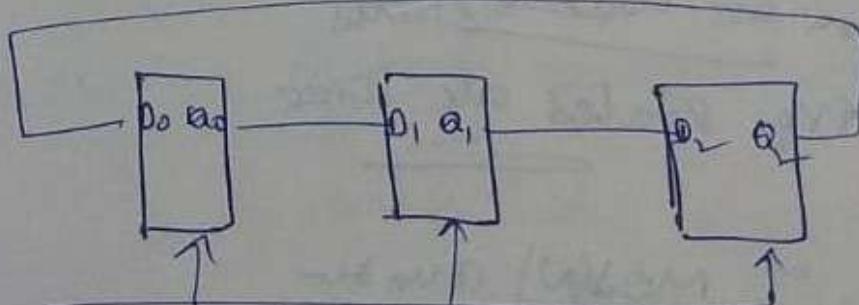

Present State $Q_2\ Q_1\ Q_0$			Next state $Q_{2N}\ Q_{1N}\ Q_{0N}$			D <sub>2</sub> D <sub>1</sub> D <sub>0</sub>		
0	0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	1	0
0	1	0	1	0	0	1	0	0
0	1	1	1	1	0	1	1	0
1	0	0	0	0	1	0	0	1
1	0	1	0	1	1	0	1	1
1	1	0	1	0	1	1	0	1
1	1	1	1	1	1	1	1	1




(1)

(2)

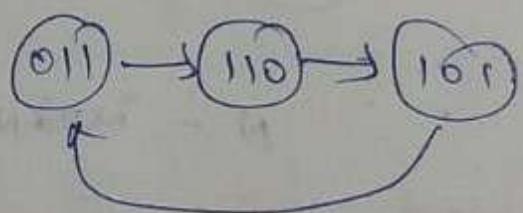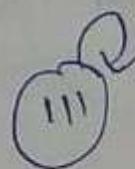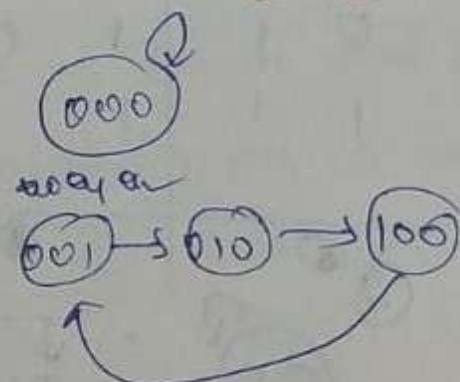(3)

 $Q = 10$  $D \rightarrow Q$ 

$$\begin{aligned}D_0 &= Q_2 \\D_1 &= Q_0 \\D_2 &= Q_1\end{aligned}$$



We are getting  $(Mod\ n)$ .


Even though we have 8 states  
we are counting states are three

∴  $Mod(N)$  Counter

27

## Mod n Johnson counter

22

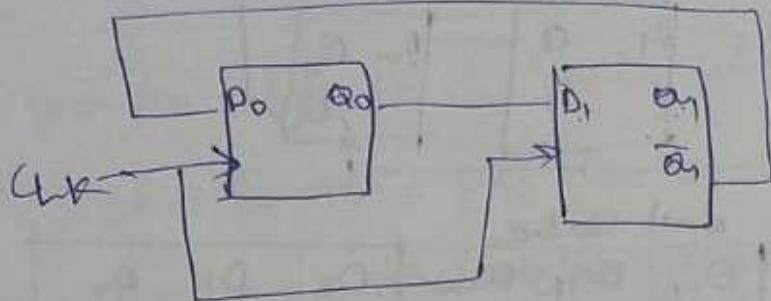


$$D_0 = \overline{Q}_1$$

$$D_1 = Q_0$$

<u>P.S.</u>		<u>N.S.</u>		<u>D<sub>1</sub>, D<sub>0</sub></u>	
$Q_1$	$Q_0$	$Q_1, N$	$Q_0, N$	$D_1$	$D_0$
0	0	0	1	0	0
0	1	1	1	1	0
1	0	0	0	0	0
1	1	1	0	1	0

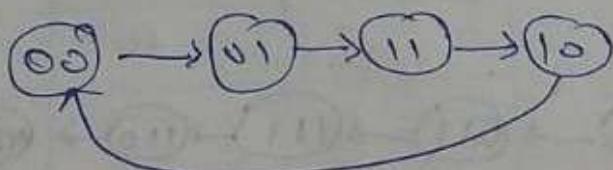(1)                    (2)                    (3)




Act as a Mod 4 counter (that means)

$\frac{N}{2}$  FB  $\Rightarrow$  Mod ( $2^N$ ) counter ✓


Mod ( $2^N$ ) X

$n$  SF  $\Rightarrow$   $2^n$  states

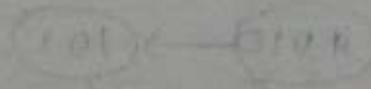


(24)

### Mod 6 Johnson Counter:-

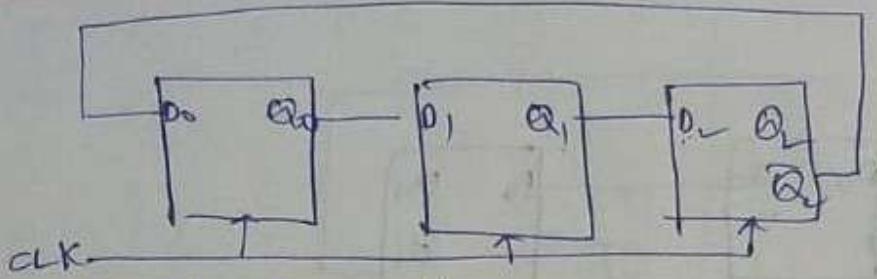


Present State			Next State					
$Q_2$	$Q_1$	$Q_0$	$Q_{2N}$	$Q_{1N}$	$Q_0N$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	1	0	0	1
0	0	1	0	1	1	0	1	1
0	1	0	1	0	1	1	0	0
0	1	1	1	1	1	1	1	1
1	0	0	0	0	0	0	0	0
1	0	1	0	1	0	0	1	0
1	1	0	1	0	0	1	0	0
1	1	1	1	1	0	1	1	0
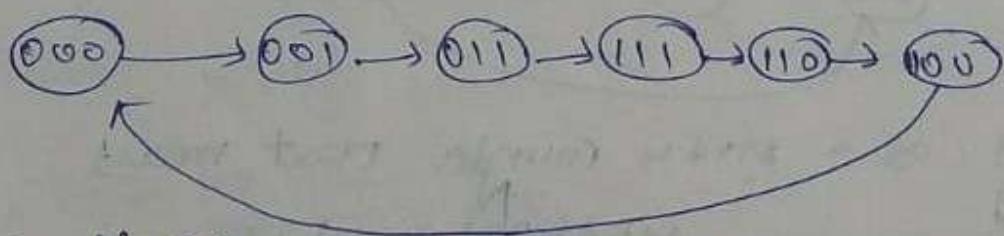
$$D_0 = \overline{Q_2} ; D_1 = \overline{Q_0} ; D_2 = Q_1$$



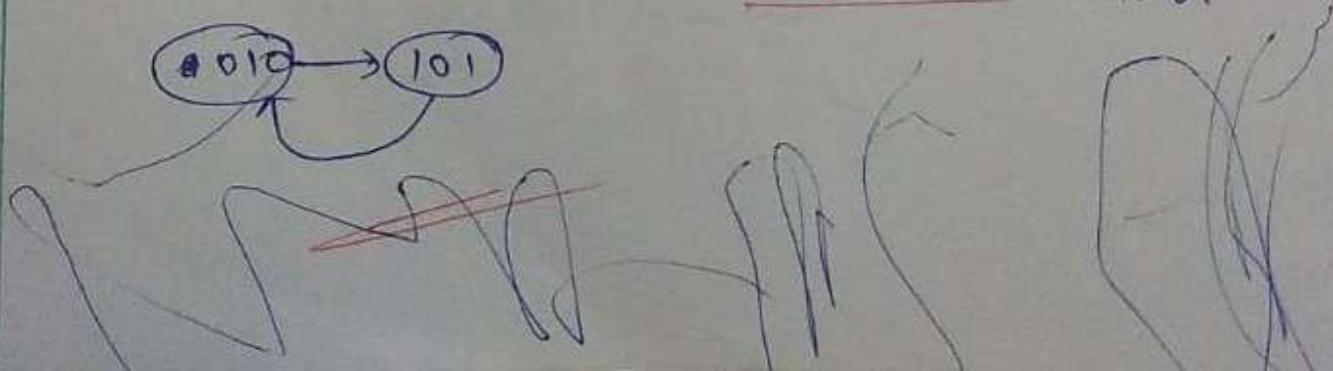$N$  FB acts as Mod 6 counter  
that means Mod( $2N$ ) counter.




25) Mod 4 Gray counter using T-FF:-

24

Design a Counter:-

- ① get the state table from state diagram.
- ② Identify the FF to be used and replace the concerned next state using excitation table to associated FF.
- ③ get the expression and realize them.

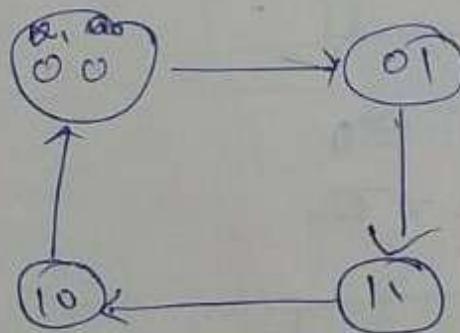~~Design a Synchronous counter for the following using T-FF.~~



Note: only one bit is changed when move from one state to next state.

P.S. N.S. Excitation table

$Q_1 Q_0$	$S_{IN} S_{EN}$	$T_1$	$T_0$
0 0	0 1	0	1
0 1	1 1	1	0
1 0	1 0	0	1
1 1	0 0	1	0


Step 3:

$$\Rightarrow T_1 = \overline{Q}_1 Q_0 + Q_1 \overline{Q}_0 = Q_1 \oplus Q_0$$

$$\Rightarrow T_0 = \overline{Q}_1 \overline{Q}_0 + Q_1 Q_0 = Q_1 \oplus Q_0$$

Step 3.ii


~~∴ Min. no. of FF [Log N]~~

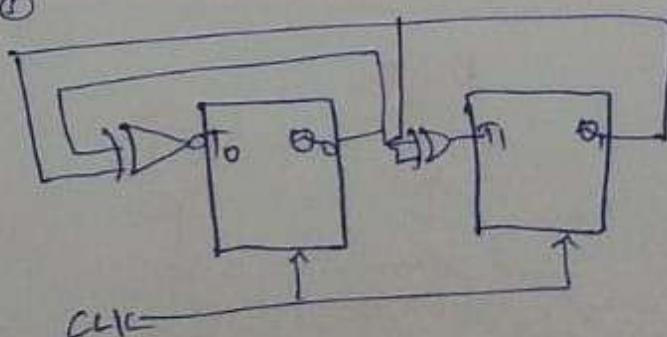

26

## MOD 4 binary counter using D-FFs:-

25

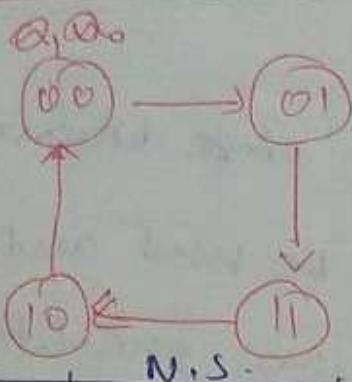

P.S.


N.S.

Excitation table of DFF

$Q_1, Q_0$	$D, N Q_0 N$	$D_1, D_0$
0 0	0 1	0 1
0 1	1 1	1 1
1 0	1 0	1 0
1 1	0 0	0 0

$$D_1 = \bar{Q}_0 \bar{Q}_1 + Q_1 Q_0 = Q_0$$

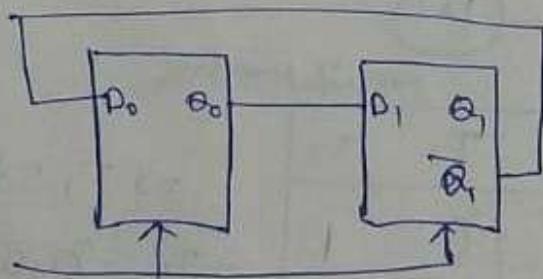
$$D_0 = \bar{Q}_1 \bar{Q}_0 + \bar{Q}_1 Q_0 = \bar{Q}_1$$



Compare to T-FFs. We use D-FF for better performance  
since no need a extra combinational chk.

27

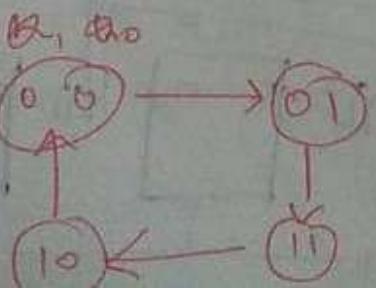
## MOD 4 binary counter using 1D and 1T-FFs:-



$D_1$	$D_0$	$Q_1, N$	$Q_0, N$	$D_1$	$T_0$
0	0	0, 1	1	0	1
0	1	1	1	1	0
1	1	1	0	1	1
1	0	0	0	0	0


$$D_1 = Q_0$$
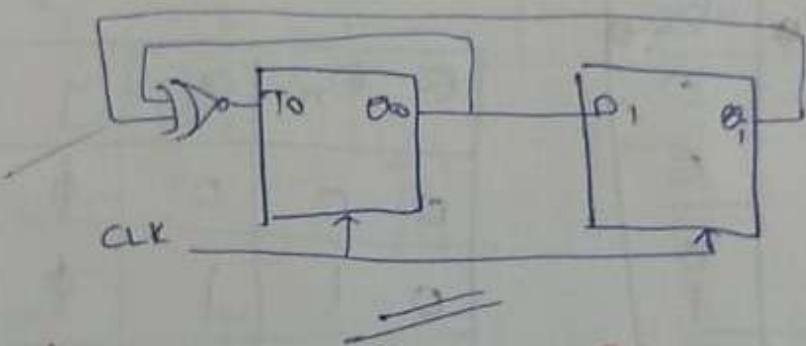
$$T_0 = \overline{Q}_1 \overline{Q}_0 + Q_1 Q_0 = Q_1 \oplus Q_0$$




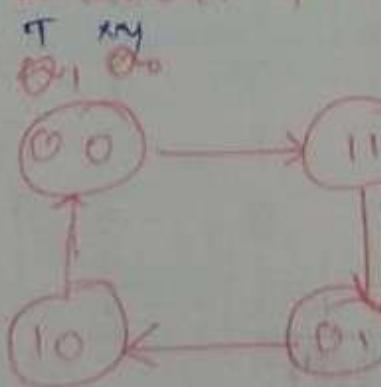Q8 Counter using two different FFs:

Consider the following state diagram which is to be designed using T-FF for MSB and ~~XNOR~~ <sup>FF</sup> for LSB. The behaviour of XNOR is given below:



F.T.R		$\oplus_n$
x	y	$\oplus_n$
0	0	0
0	1	0
1	0	1
1	1	1

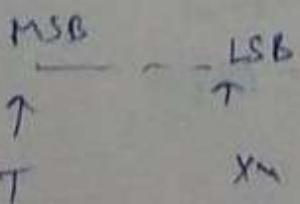

$\alpha_1$	$\alpha_0$	$\alpha_{1N}$	$\alpha_{0N}$	T	X	Y
0	0	1	1	1	1	ψ
1	1	0	1	1	φ	1
0	1	1	0	1	φ	0
1	0	0	0	1	0	φ

FT  
functional table  $\rightarrow$  characteristic table  $\rightarrow$  excitation table  
CT ET

x	y	$\alpha_1$	$\alpha_{0N}$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

$\alpha$	$\alpha_{0N}$	x	y
0	0	0	φ
0	1	1	φ
1	0	φ	0
1	1	φ	1


C.T.

$\alpha_1$	$\alpha_0$	x
0	0	1
0	1	φ
1	0	φ


$$x = \overline{\alpha_1}$$

$\alpha_1$	$\alpha_0$	y
0	0	0
0	1	φ
1	0	1


$$y = \alpha_1$$

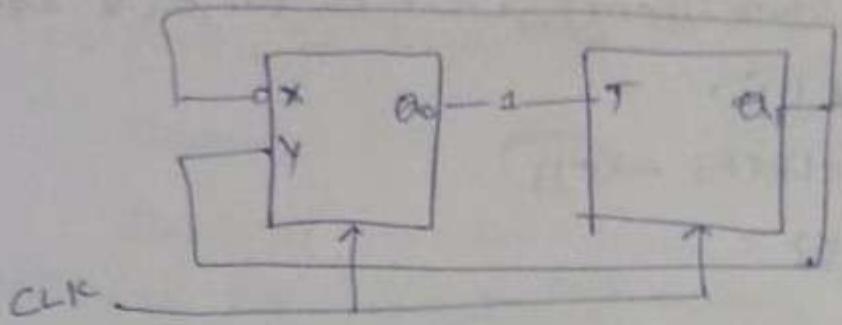

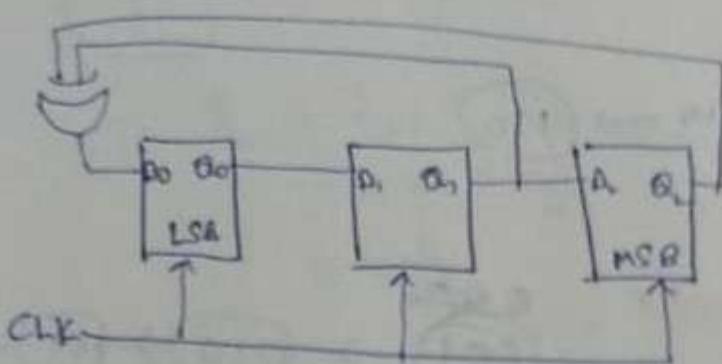Q) Model on Analyzing Counting States and Sequence Generation:




Sol:-

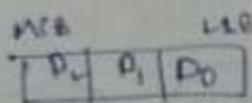

P.S.			N.S.		
Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>2N</sub>	Q <sub>1N</sub>	Q <sub>0N</sub>
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	1
0	1	1	1	1	1
1	0	0	0	0	1
1	0	1	0	1	1
1	1	0	1	0	0
1	1	1	1	1	0
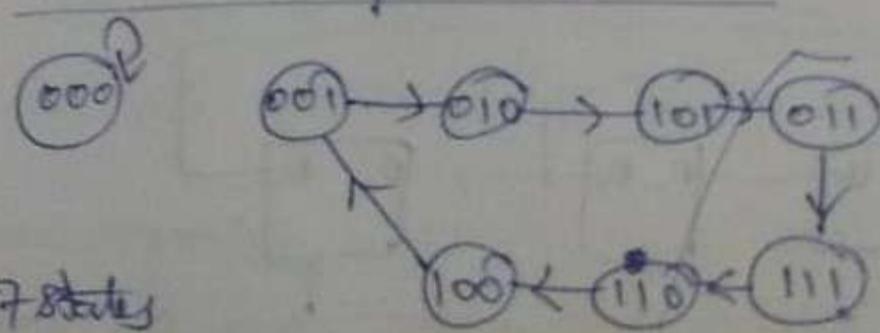
$$\begin{aligned} B_{1N} \cdot D_0 &= Q_2 Q_1 Q_0 \\ B_{1N} \cdot D_1 &= Q_0 \\ Q_{0N} &= B_1 \cdot B_2 = Q_1 \end{aligned}$$



acting as  
mod 7 counter

∴ 7 states

- Q. If initial state is  $001$ , what is the state after 29  
 4 clocks  $\rightarrow 111$   
 $\rightarrow 001, 10$  clocks  $\rightarrow 011$   
 $(7+3)$   
 $\rightarrow 001, 43$  clocks  $\rightarrow 010$   
 $(42+1)$   
 $\rightarrow 001, 25$  clocks  $\rightarrow 111$   
 $(21+4)$   
 $\rightarrow 001, 117$  clocks  $\rightarrow 110$   
 $(7+16+5)$

### Sequence generator


if tap at  $Q_0$  :-

consider  $Q_0$  bit at all

8 states only

sequence

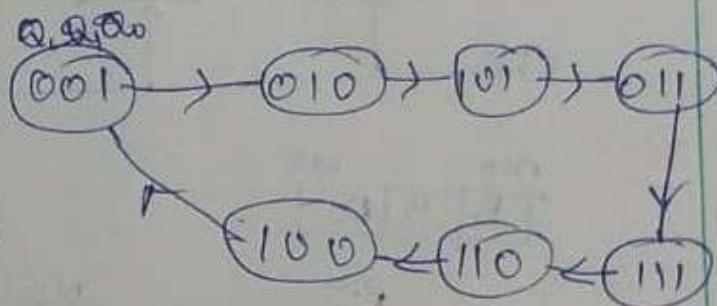$1 \ 0 \ 1 \ 1 \ 1 \ 0 \ 0 \mid 1 0 1 1 1 0 0 \mid \dots$




if tap at  $Q_1$ : consider  $Q_1$  bit at all states only

$0 \ 1 \ 0 \ 1 \ 1 \ 0 \mid 0 \ 1 \ 0 \ 1 \ 1 \ 0 \mid \dots$

if tap at  $Q_2$ :  $0 \ 0 \ 1 \ 0 \ 1 \ 1 \mid 0 \ 0 \ 1 \ 0 \ 1 \ 1 \mid \dots$

### Deriving the Clock Frequency:-

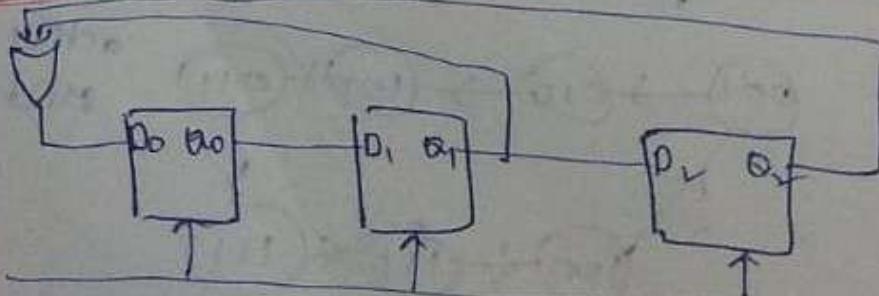


Time period for propagation for signal,

through FF,  $T_{FF} = 15\text{ns}$

through comb. act,  $T_{com} = 5\text{ns}$

which of the following ~~and~~<sup>frequency</sup> ensures proper counting.

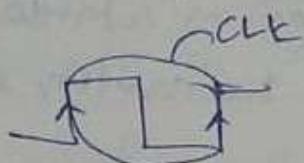- ~~a) 40 MHz~~ b) 60 MHz c) 90 MHz d) 300 MHz



$$\textcircled{12} \quad T_{clk} \geq T_{FF} + T_{com}$$

$$\geq 15\text{ns} + 5\text{ns}$$

$$\geq 20\text{ns}$$

$$f_{clk} \leq \frac{1}{20\text{ns}}$$

$$\leq \frac{1}{20 \times 10^{-9}}$$

$$\leq 50 \text{ MHz}$$

$$f_{clk} \leq \frac{1}{T_{clk}}$$



$$\frac{1000}{20 \times 10^{-9}}$$

### (31) Self Starting and Free Running


→ A counter is said to be self-starting if it is possible to enter counting loops irrespective of the initial state.

→ A counter is said to be free running if it contains all possible states in the counting loop.

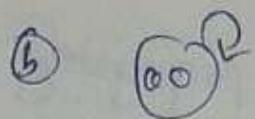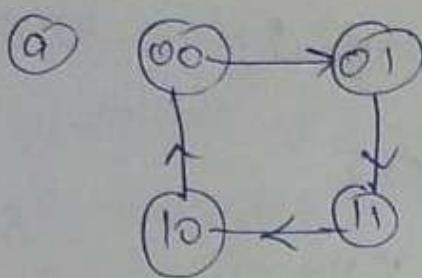→ A free running counter is a ~~not~~ self-starting counter but not vice-versa.





free running &  
self-starting

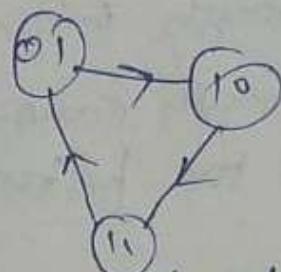

~~not self starting~~

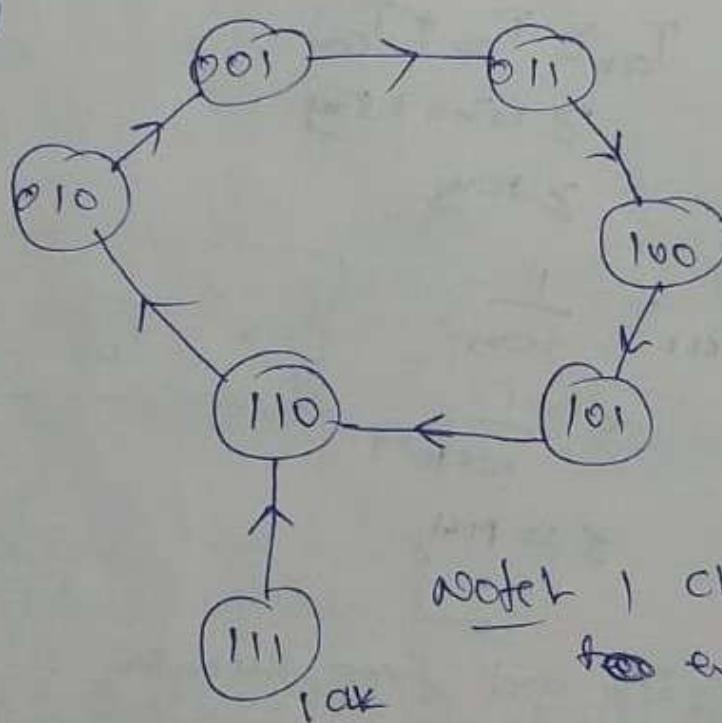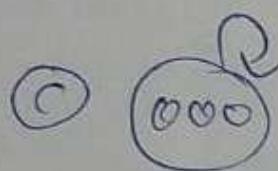
~~free~~  
00 is outside of  
the counting states




note 1 CLK taken  
to enter into counter  
state

not Self-starting Counter

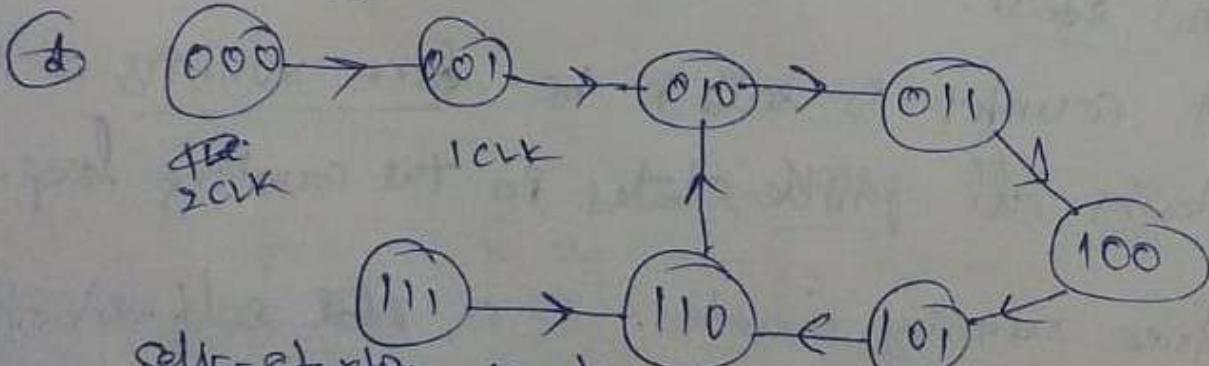000, 001, 111 are outside of the  
counting states.




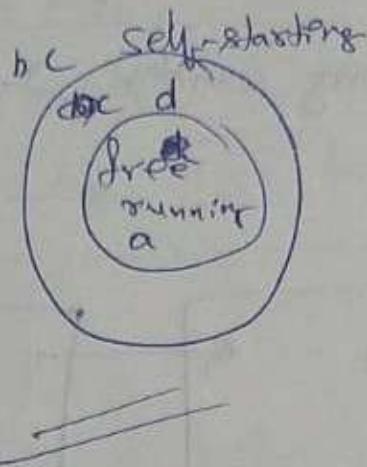Self-starting counter  
000, 001, 111 are outside of the counting states.




32 Example on self-starting and free running counter:

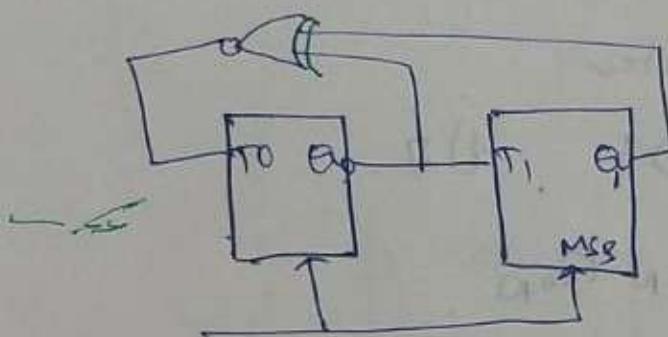A Identify if the following counter is self-starting or free running.



Sol

$Q_1, Q_0$	$\theta_{IN}$	$\theta_{ON}$	$T_1$	$T_0$
0 0	0	1 1	0	1
0 1	1	1 1	1	0
1 0	1	0 0	0	0
1 1	0	0 0	1	1

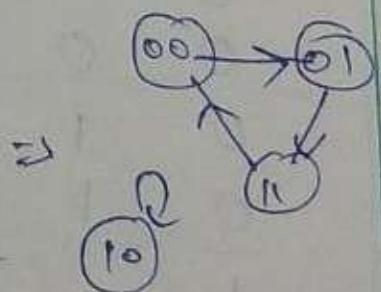

neither self-starting  
nor free-running

$$T_1 = \theta_{00}$$

$$\theta_{ON} = \theta_{00}; T_0 = 0$$

$$T_0 = Q_0 \oplus Q_1$$

$$= \overline{Q_0}; T_0 = 1$$


$$\theta_{IN} = \theta_{11}; T_1 = 0$$

$$= \overline{Q_1}; T_1 = 1$$

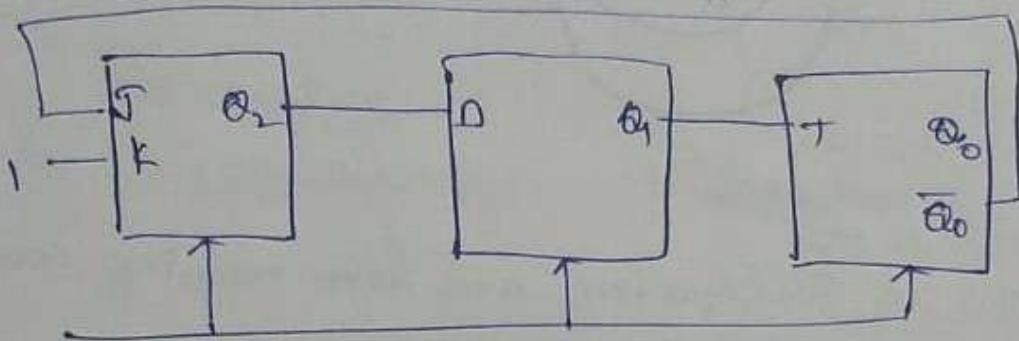(33)

counter using 3 different flip flops (FFs) :-

consider the following counter , Initially,  $Q_2, Q_1, Q_0 = 000$



① What will be the states after 4 clock

- (a) 000    (b) 010    (c) 011    (d) 101

② Module of the counter

- (a) 4    (b) 5    (c) 6    (d) 7.

33  $Q_2 \ Q_1 \ Q_0 | Q_{N+1} \ Q_N \ Q_0$

0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	1	0	1
0	1	1	0	0	0
1	0	0	0	1	0
1	0	1	0	1	1
1	1	0	0	1	1
1	1	1	0	1	0

$$Q_{1N} = D = \bar{Q}_2$$


$$Q_{0N} = Q_0; \quad T=0 \quad Q_1 = 0$$

$$= \bar{Q}_1; \quad T=1 \quad Q_1 = 1$$

$$\theta_{2N} =$$

TFF acts also


function a  
toggle(NOT)

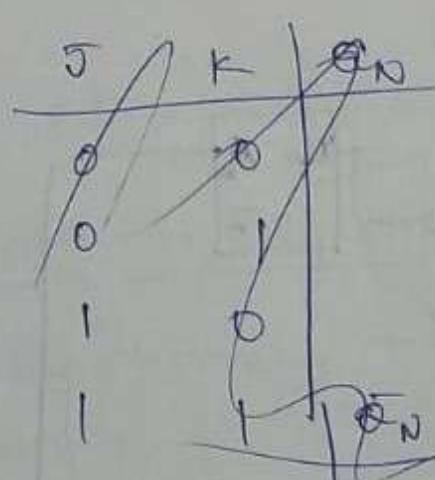

J	K	$Q_N$
0	1	$\bar{Q}_2$
1	1	$\bar{Q}_1$

$\bar{Q}_2$	K	$Q_{1N}$
0	1	0
1	1	$\bar{Q}_1$

$\bar{Q}_2$	K	$Q_{1N}$
1	1	0
0	1	$\bar{Q}_1$

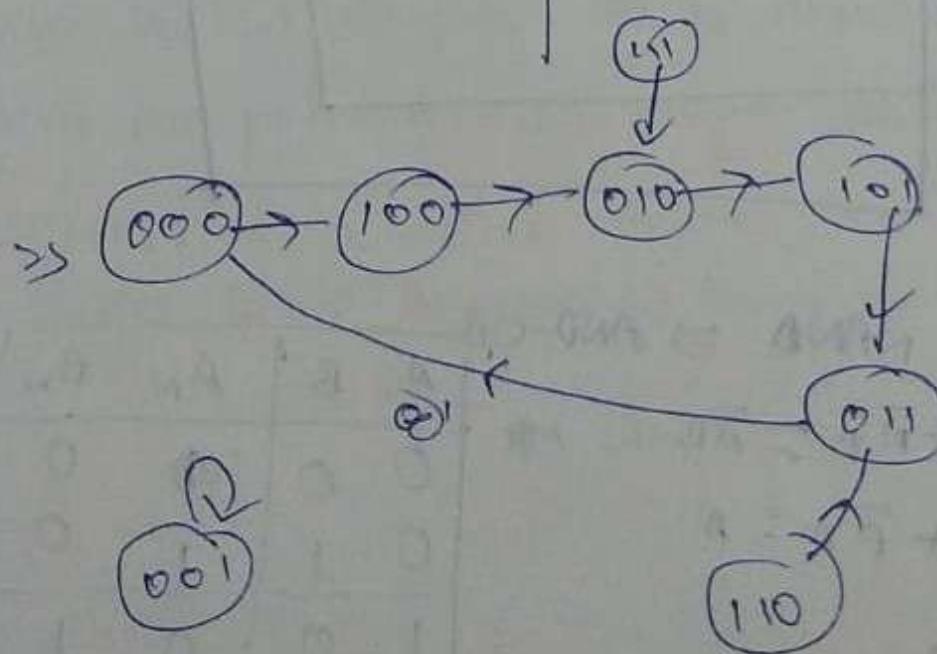


both not free running  $\Rightarrow$  self-starting

34
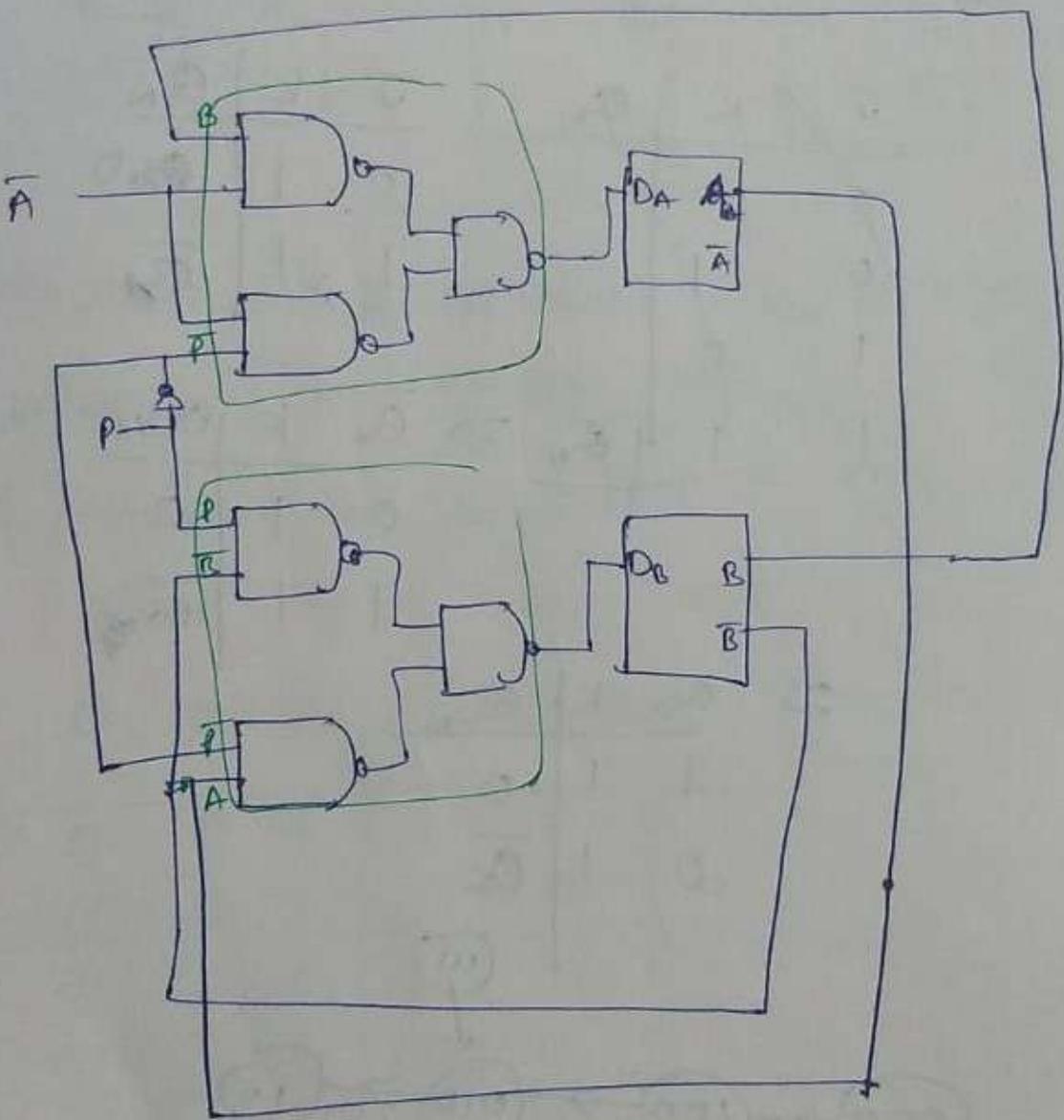
### Example on Combinational ckt's and FF's

35

Consider the following counter, if  $P=0$ ,  
the counting sequence of AB is ?



NAND - NAND  $\Rightarrow$  AND-OR


$$D_A = \overline{A}B + \overline{A}\overline{P} = \overline{A}B + \overline{A} = \overline{A}$$

$$D_B = P\overline{B} + \overline{P}A = A$$

$$B_N = D_B = A$$

$$A_N = D_A = \overline{A}$$

A	B	A_N	B_N
0	0	1	0
0	1	1	0
<hr/>		<hr/>	
1	0	0	1
1	1	0	1

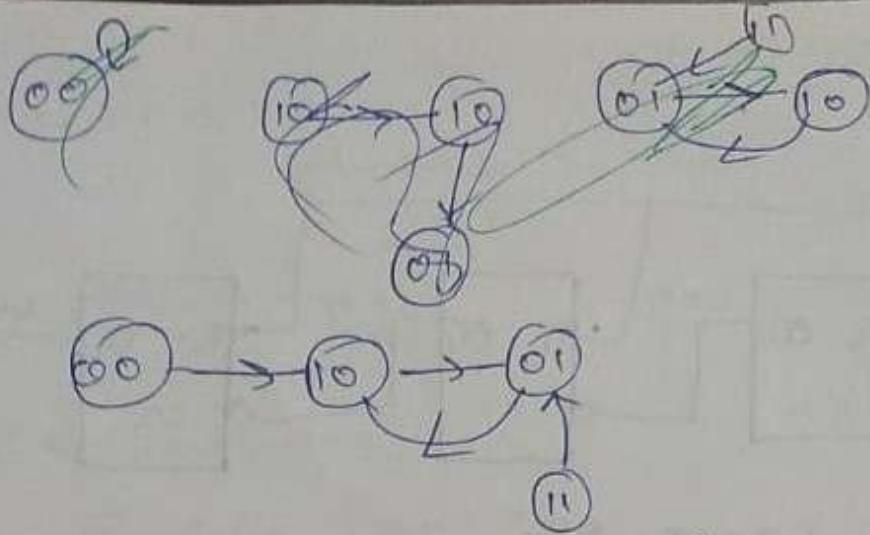


self & tailing but not free running.

### 25) Introduction to Asynchronous Counters:-


- The asynchronous counters are also called as Ripple counter.
- The basic FF is 'T' and basic counting is binary up counting. (1-2-3-4-5-...-0)
- The up counters are used for implementing incrementation.
- Due to the simpler design, asynchronous counters are preferred in IC counter fabrication.
- IC 7490 is a decade counter i.e.,  $\frac{1}{10}$  counter  
IC 7492 is a Hexadecimal Counter i.e.,  $\frac{1}{16}$  counter.

=

(36) Mod 8 up counter:-

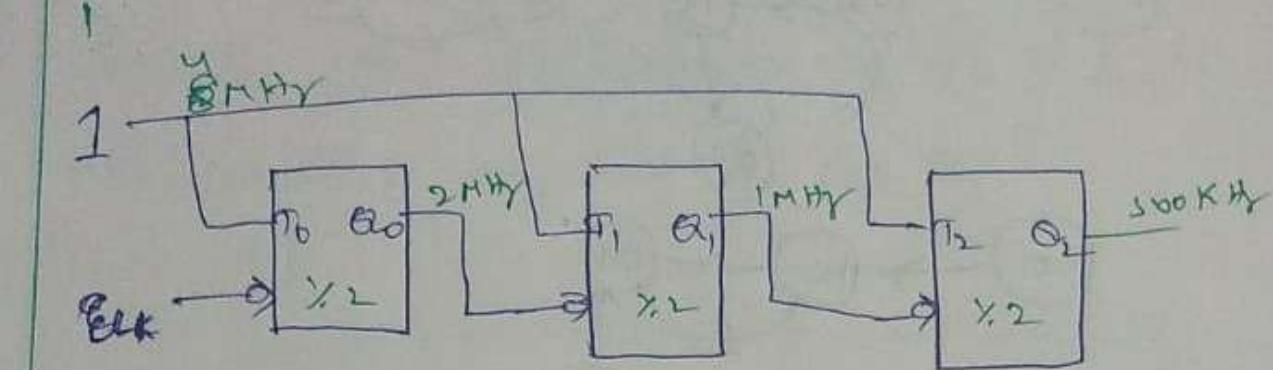

"→ edge triggering FF"

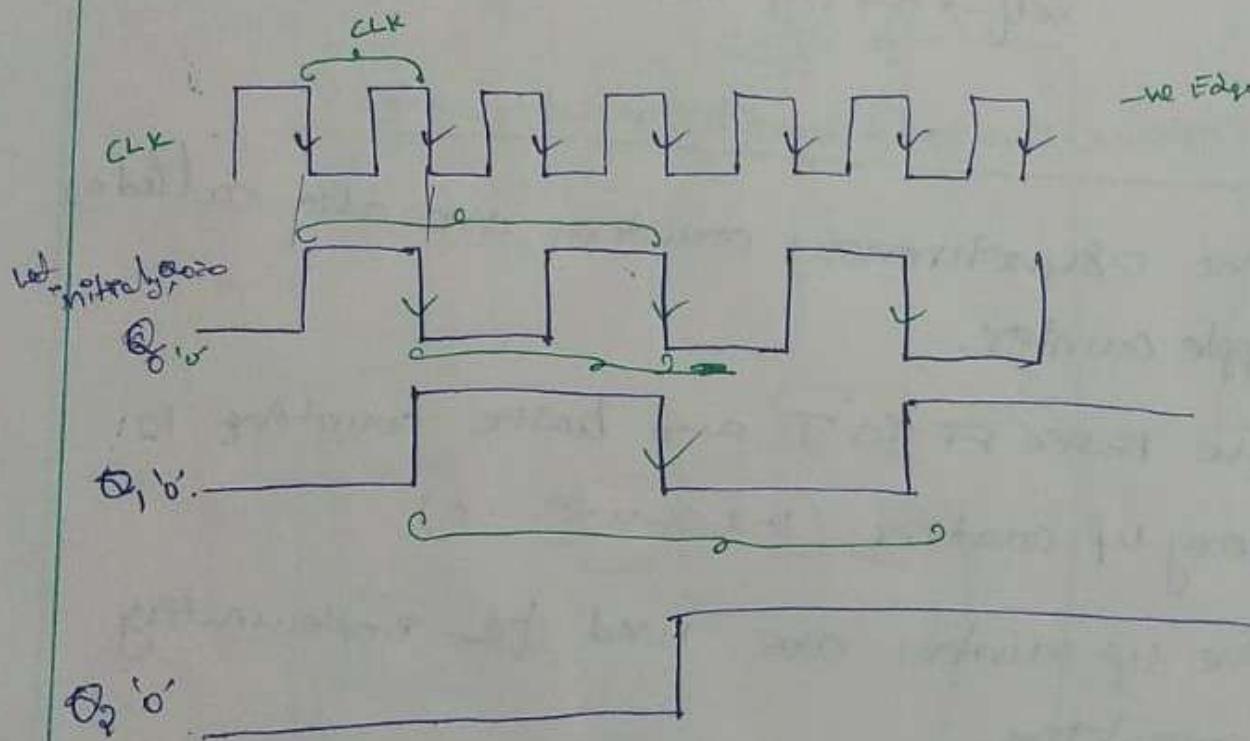

$$\therefore \text{Time period, } T_0 = 2 \times T_{\text{clk}}$$

$$\text{frequency } f_0 = \frac{1}{T_0} \times f_{\text{clk}}$$

$$\text{Time period, } T_1 = 2 \times T_0$$

$$\text{freq. } f_1 = \frac{1}{T_1} \times \text{freq. } f_0$$

$$= \frac{1}{4} \times \text{freq. } f_{\text{clk}}$$

$$\text{freq. } f_2 = 2 \times T_1$$

$$\text{freq. } f_2 = \frac{1}{2} \times \text{freq. } f_1 = \frac{1}{8} \times \text{freq. } f_{\text{clk}}$$

if  $Q_2 = \text{HOLD}$  then

$Q_1 \leftarrow 1 \rightarrow \text{STUCK}$


Exam pointer view :-

$$Q_{DN} = \bar{Q}_2 ; \text{ every clock}$$

$$Q_{IN} = \bar{Q}_1 ; Q_0 : 1 \rightarrow 0$$

$$Q_{2N} = \bar{Q}_2 ; Q_1 : 1 \rightarrow 0$$

	<u>Q<sub>2</sub></u>	<u>Q<sub>1</sub></u>	<u>Q<sub>0</sub></u>	<u>Q<sub>2N</sub></u>	<u>Q<sub>1N</sub></u>	<u>Q<sub>0N</sub></u>	
(0)	0	0	0	0	0	1	(1)
(1)	0	0	1	0	1	0	(2)
(2)	0	1	0	0	1	1	(3)
(3)	0	1	1	1	<u>0</u>	0	(4)
(4)	1	0	0	1	0	1	(5)
(5)	1	0	1	1	1	0	(6)
(6)	1	1	0	1	<u>0</u>	1	(7)
(7)	1	1	1	<u>0</u>	<u>0</u>	0	(8)

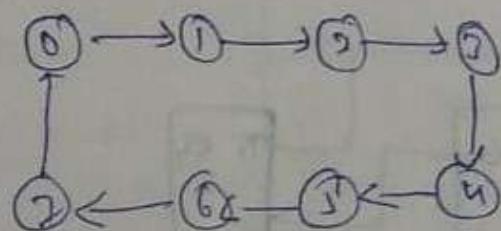


free running & self-starting Counter

Mod 8 counter (0 to 7)

37

### Mod n up counter :-

39

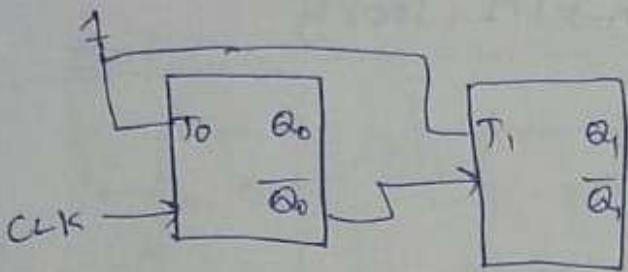

g



$$\theta_{0N} = \bar{Q}_0 ; \text{ for every clock}$$

$$\theta_{1N} = \bar{Q}_1 ; \bar{Q}_0 : 0 \rightarrow 1$$

PS

$\rightarrow Q_0 : 1 \rightarrow 0$   
NS

$Q_1$	$Q_0$	$\theta_{1N}$	$\theta_{0N}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	0

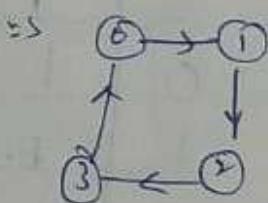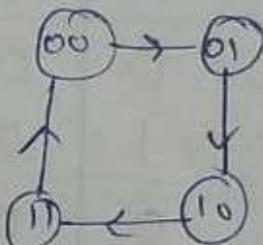


free running  
self starting

Mod n counter

38

### Mod n down counter:-


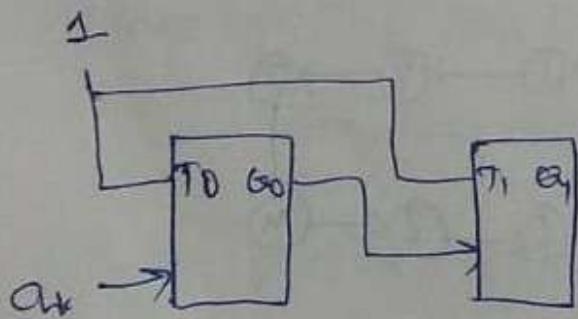


Ex:

$$\theta_{0N} = \bar{Q}_0 ; \text{ for every clock}$$


$$\theta_{1N} = \bar{Q}_1 ; \bar{Q}_0 : 0 \rightarrow 1$$

$Q_1$	$Q_0$	$Q_{IN}$	$Q_{NIN}$
0	0	1	1
0	1	0	0
1	0	0	1
1	1	1	0

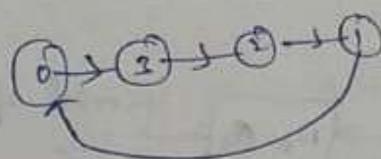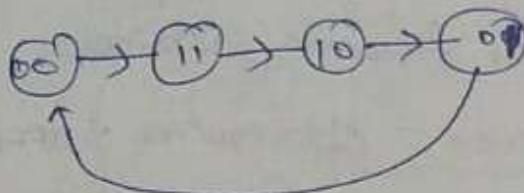

Free running self-starting

### 39 Mod 8 random Counter:-

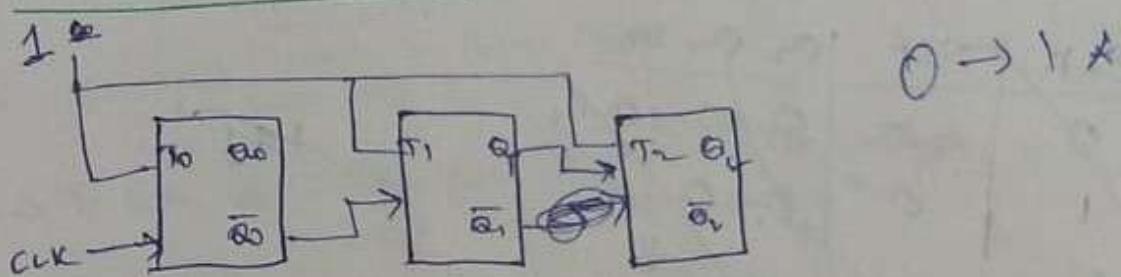


(Q1) If the initial state  $Q_2Q_1Q_0 = 101$ , what will be state after n clock cycles?

$Q_{0N} = \bar{Q}_0$ ; for every clock

$Q_{1N} = \bar{Q}_1$ ;  $\bar{Q}_0: 0 \rightarrow 1$

$Q_0: 1 \rightarrow 0$

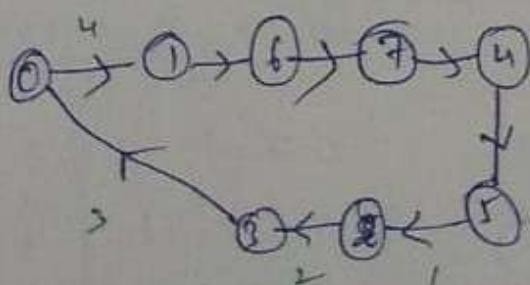$Q_{2N} = \bar{Q}_2$ ;  $Q_1: 0 \rightarrow 1$



$\therefore \underline{001}$

$Q_2$	$Q_1$	$Q_0$	$Q_{IN}$	$Q_{NIN}$	$Q_{2N}$	$Q_{1N}$	$Q_{0N}$
0	0	0	0	0	1		
1	0	0	1	1	↑	0	
2	0	1	0	0	1		1
3	0	1	1	0	0		0
4	1	0	0	1	0		1
5	1	0	1	0	1	↑	0
6	1	1	0	1	1	1	1
7	1	1	1	1	0	0	0


(40)

## Applications of FFs:-

- ① Shift registers  $\rightarrow$  used as "sequential memory".  
Ex:- Accumulator in MP.

- ② counters  $\rightarrow$  ① used to count no. of pulses  
 ② used as frequency divider

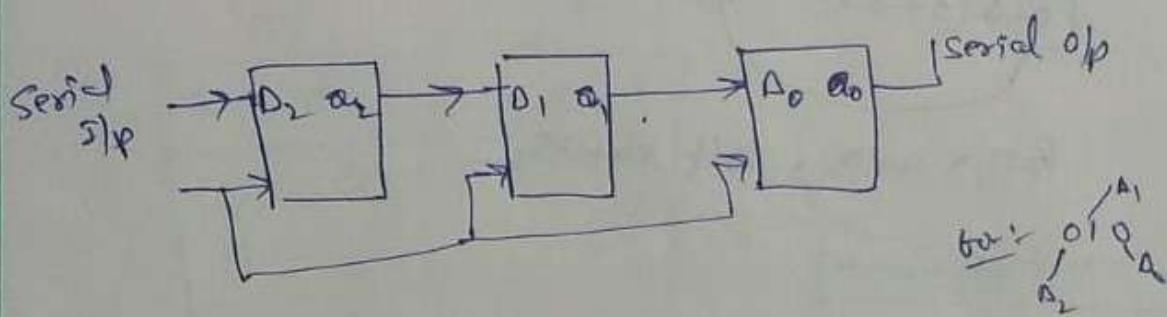(41) 3 bit Shift Right register:- (It requires 3 DFFs)



CLK	SIP	Q <sub>2</sub> Q <sub>1</sub> Q <sub>0</sub>
0	-	0 0 0
1	0	0 0 0
2	1	0 0 0
3	0	0 0 0
4	1	0 0 0
5	0	0 0 0
6	1	0 0 0
7	0	0 0 0

101

ba 101

CLK	SIP	Q <sub>2</sub> Q <sub>1</sub> Q <sub>0</sub>
0	-	0 0 0
1	1	0 0 0
2	0	0 1 0
3	1	1 0 1

→ 'n' clock are required to put n bit data on register in SIP shift 'n' register

SOP :- (Serial Out)

CLK	Q <sub>n</sub> Q <sub>n-1</sub> ... Q <sub>0</sub>	Q <sub>n</sub>
0	0 1 0 0	0 → 1
1	0 0 1 0	0 → 0
2	0 0 0 1	0 → 1 → 0

already at the of

2 clocks are required for 3 bits

∴ (n-1) clock required for shift n reg.

~~SIP~~ SIP + n CLK

S<sub>20</sub> - n-1, CLK


n+1 = (n-1) CLK

\* (S<sub>20</sub>+S<sub>19</sub>)

→ If we go with PIPs then 1 CLK is enough.

L2 Examples on Shift Right Register:-

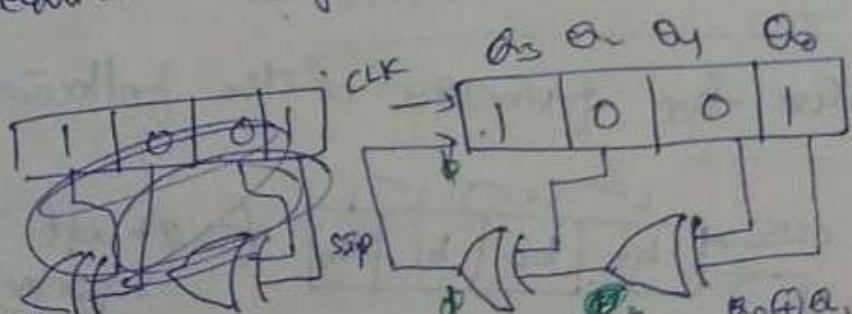In the following right shift register, determine the no. of clocks required to bring it to the initial state of '1001'



clk	SIP	Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
0	-	1	0	0	1
1	1	1	1	0	0
2	1	1	1	1	0
3	0	0	1	1	1
4	1	1	0	1	1
5	0	0	1	0	1

7	1	1	0	0	1
8	-	-	-	-	-


∴ After 7 clocks

Q3

Ex 2:-

u3

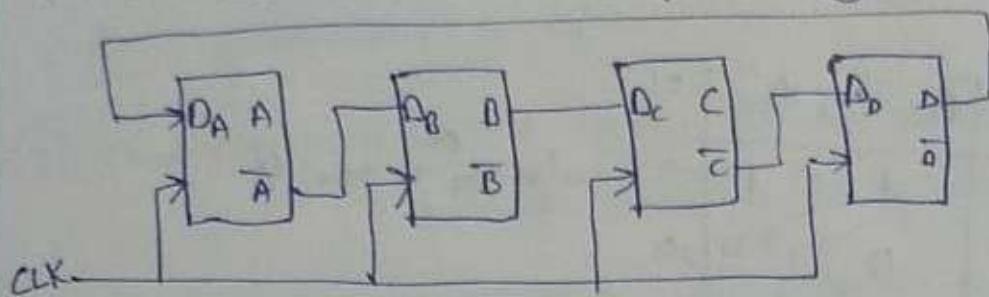Initial value of  $ABCD = 0000$ , then what are the sequence of numbers the following circuit is counting



Sol:

$$D_A = D$$

$$D_B = \bar{A}$$

$$D_C = B$$

$$D_D = \bar{C}$$


CLK	A	B	C	D
0	0	0	0	0
1	0	1	0	1
2	1	1	1	1
3	1	0	1	0
4	0	0	0	0
5	0	1	0	1

∴  $0 - 5 - 15 - 10$

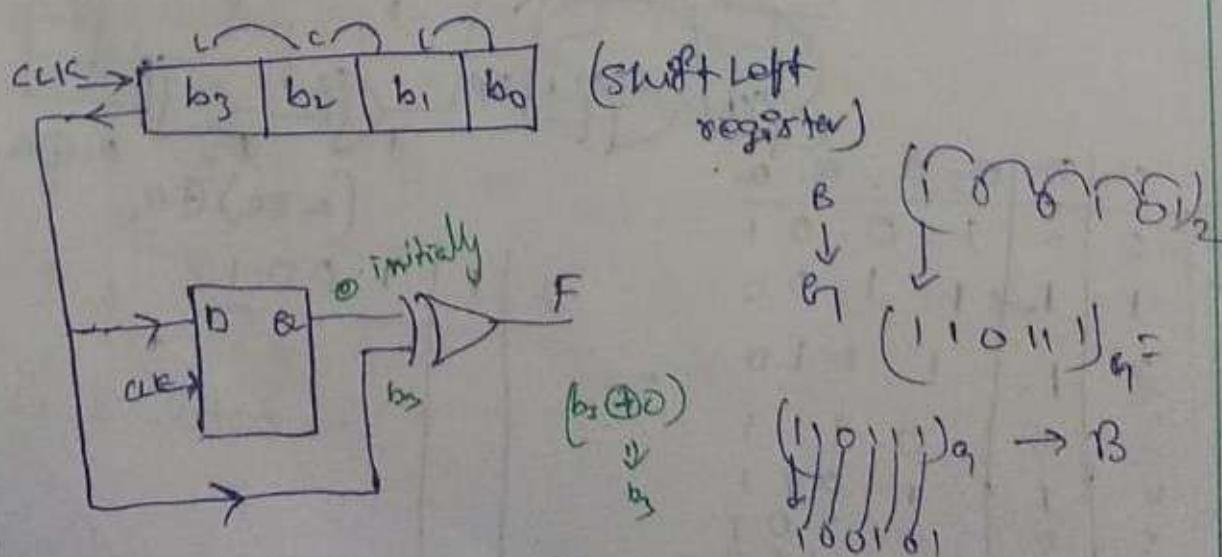Q4

Binary to Gray Converter:-

Determine the function of the following circuit.





Sol:

$b_3$	$b_2$	$b_1$	$b_0$
$b_2$	$b_1$	$b_1$	$b_0$
$b_1$	$b_0$	$b_0$	$b_0$
$b_0$	$b_0$	$b_0$	$b_0$

Q ①  $b_3$  initially



44
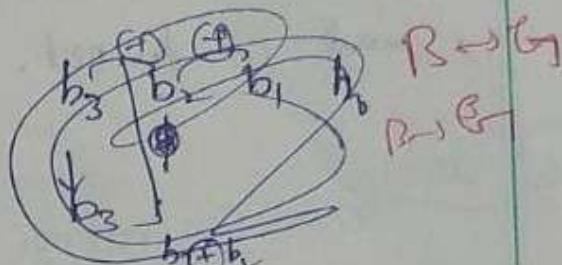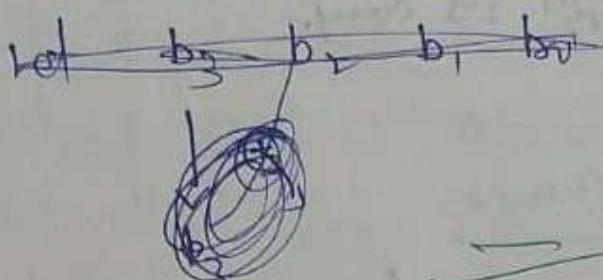
$$(b_3) (b_2 \oplus b_1) (b_2 \oplus b_1) / (b_1 \oplus b_0)$$



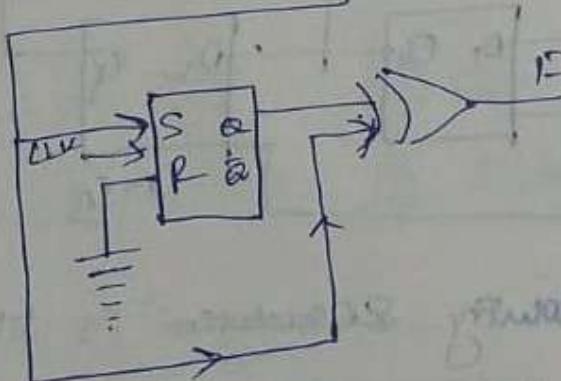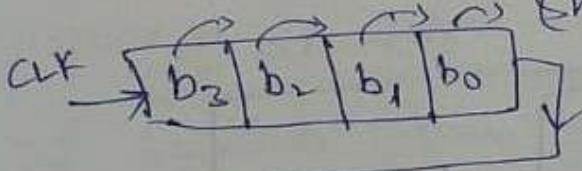Q 45 Finding 2's complement:-

What is the function of the following circuit?  
(Shift right register)



Q Initially at  $a = 0$ ,

$R = 0$  always

$$\boxed{b \oplus 0 = b; b \oplus 1 = b'}$$

$$b_0 \oplus 0 = b_0$$

P	I	0	0	0
---	---	---	---	---

1st - 0010.

2nd - 0001

3 - 0000

$\frac{S}{R}$  - Latch

1 0 - Set

$\begin{array}{|c|c|c|} \hline 0 & 1 & 0 & 0 \\ \hline 1 & 1 & 0 & 0 \\ \hline \text{con't. sec} & & & \\ \hline \end{array}$

P	I	0	0	0
---	---	---	---	---

if F:  $\boxed{11100}$

second  $\boxed{0100}$

ex-5 0001

~~HFD~~ 2's comp ~~HFD(001)~~ - 0001  
0001  
↓  
0001


Hint from LSB end, write as it is upto first 1, next complement. to get 2's comp.

(46)

2001

on Counting sequence:-

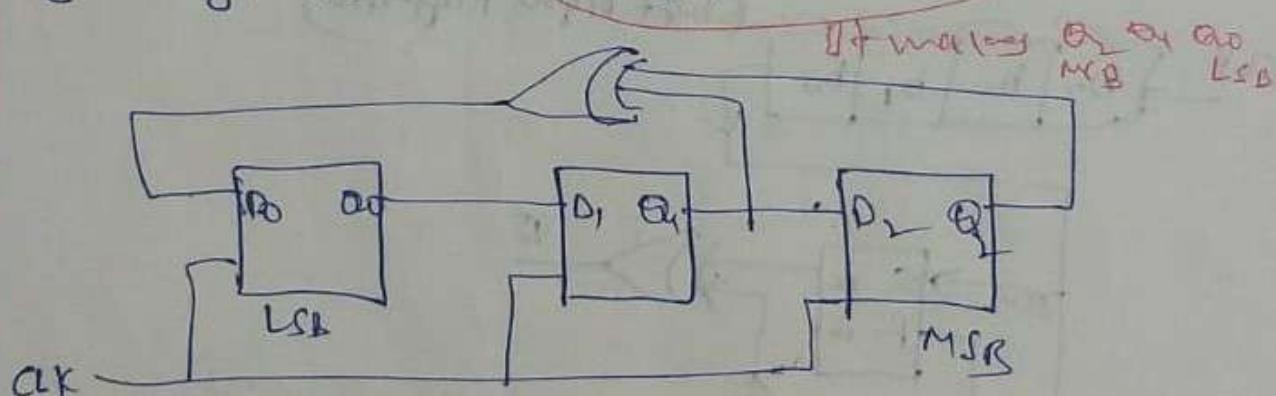Consider the circuit given below with initial state  $Q_0 = 1, Q_1 = Q_2 = 0$ . The state of the circuit is given by the value  $4Q_2 + 2Q_1 + Q_0$ .



Which of the following ~~sequence~~ is the correct state sequence of the circuit(crt)?

- (A) 1, 3, 4, 6, 7, 5, 12
- (B) 1, 2, 5, 3, 7, 6, 4
- (C) 1, 2, 5, 6, 12, 5, 4
- (D) 1, 6, 15, 7, 2, 3, 4

$Q_{2N} = D_2 = Q_1$


$Q_{1N} = D_1 = Q_0$

$Q_{0N} = D_0 = Q_1 \oplus Q_2$

$\alpha_2$	$\alpha_1$	$\alpha_0$	$\theta_{IN}$	$\theta_{IN}$	$\theta_{IN}$
0-0	0	0	0	0	0
1-0	0	1	0	1	0
2-0	1	0	1	0	1
3-0	1	1	1	1	1
4-1	0	0	0	0	1
5-1	0	1	0	1	1
6-1	1	0	1	0	0
7-1	1	1	1	1	0

(iv) Start with  
 $\alpha_1 \alpha_0 \alpha_0$   
 $0 \quad 0 \quad 1$


46

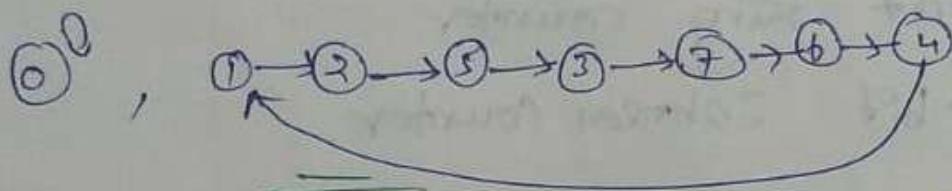

Q7 Question on SR-Latch SR latch made by cross coupling two NAND gates

If  $S=R=0$ , then it will result in


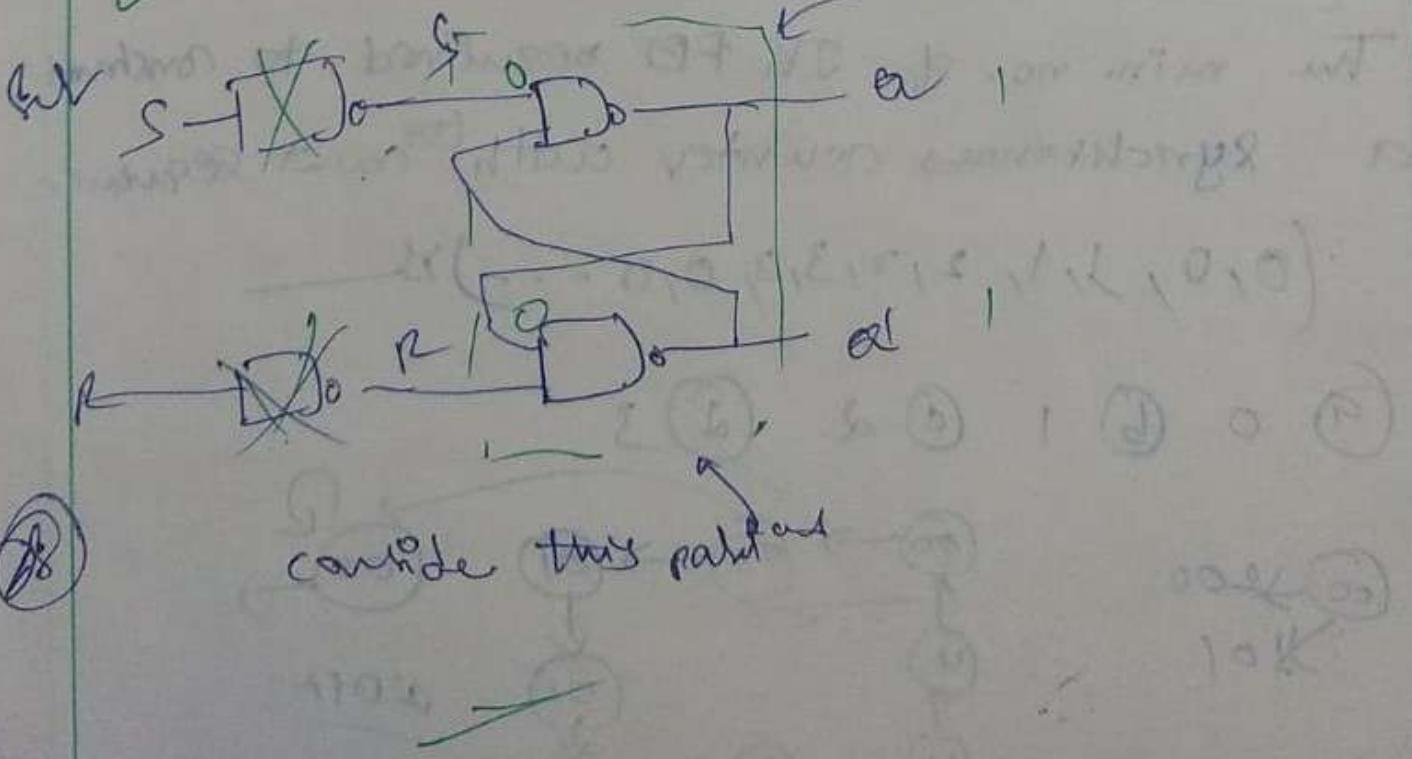
- (a)  $\alpha=0, \bar{\alpha}=1$       (b)  $\alpha=1, \bar{\alpha}=0$
- (c)  $\alpha=1, \bar{\alpha}=1$       (d) Indeterminate state.



48) 2014 on Counter

Let  $K = 2^n$ , a circuit is built by giving the output of an  $n$ -bit binary counter as IP to an  $n$  to  $2^n$  bit decoder. This circuit is converted to a

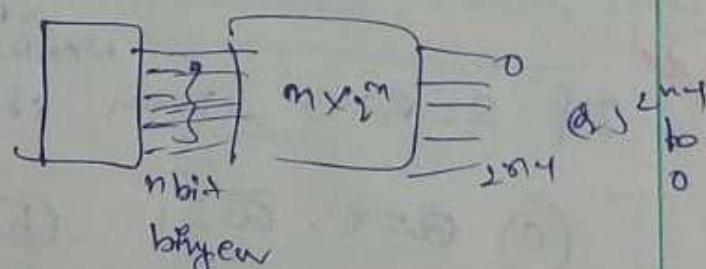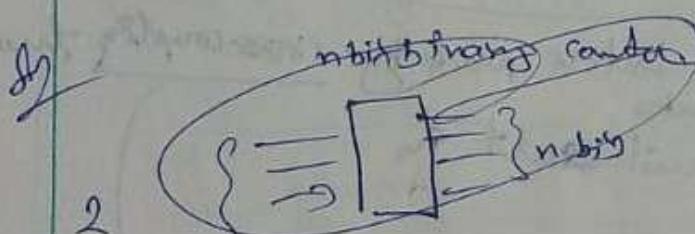- (a)  $K$ -bit binary up counter
- (b)  $K$ -bit binary down counter
- (c)  $K$ -bit ring counter
- (d)  $K$ -bit Johnson counter.




49) 2015)


on Sequence Generation:-

The min. no. of JK FF required to construct a synchronous counter with count sequence

$(0, 0, 1, 1, 2, 2, 3, 3, 0, 0, \dots)$

(a) 0 (b) 1 (c) 2 (d) 3

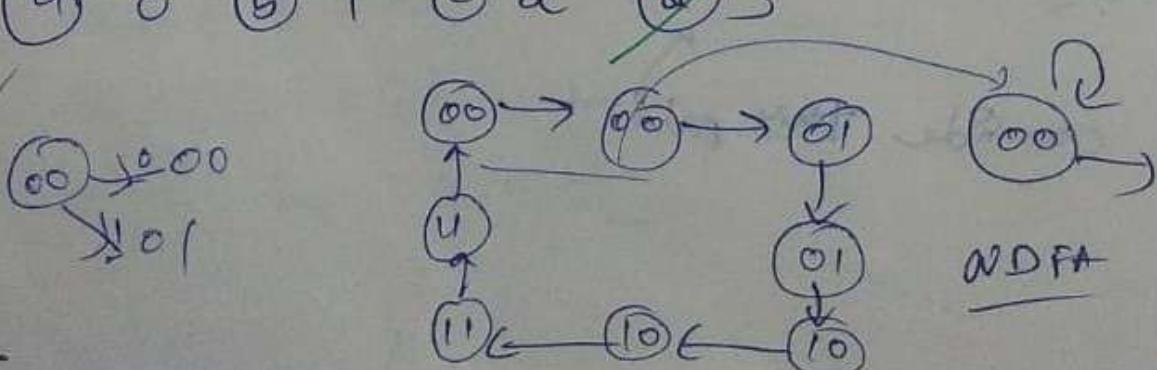

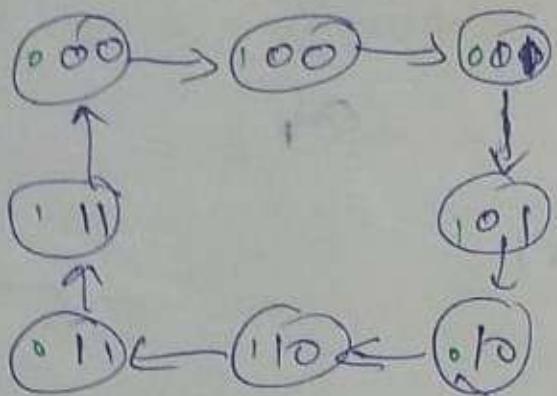

S.C. 8

14

two odd going edge, add 1's  
4 outgoing edge add 2's  
2 outgoing edges add K's  
K " " " add log K

DFA but not consider first FF

50

2015

On bit sequence


A true edge triggered D-FF is connected to a true edge triggered JK-FF as follows. The Q output of the D-FF is connected to both J and K inputs of the JK-FF, while the Q output of the JK-FF is connected to the D input of the D-FF. Initially, the output of the D-FF is set to logic one and the output of the JK-FF is cleared. Which one of the following is the bit sequence (including initial state) generated at the Q output of the JK-FF, when F<sub>D</sub> and F<sub>J</sub> are connected to a free running common clock? Assume that J=K=1 is the toggle mode and J=K=0 is the state holding mode of the JK-FF. Both the FFs have non-zero propagation delays.

a) 011011011...

b) 0100100...

c) 011101110...

d) 011001100...

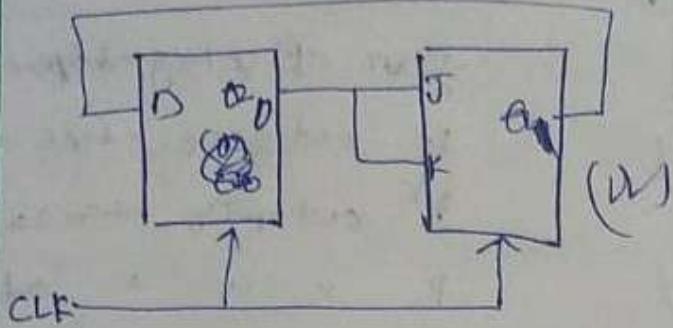


$$\alpha_{1N} = 0 = \alpha_0$$

$$\alpha_{0N} = 5\alpha_0 + 5\alpha_0$$

$$= \alpha_1\bar{\alpha}_0 + \alpha_1\alpha_0$$

$$\alpha_{0N} = \alpha_0 \oplus \alpha_1$$

$\alpha_1$	$\alpha_0$	$\alpha_{1N}$	$\alpha_{0N}$
0	0	0 0	0
0	1	1 0	1
1	0	0 1	1

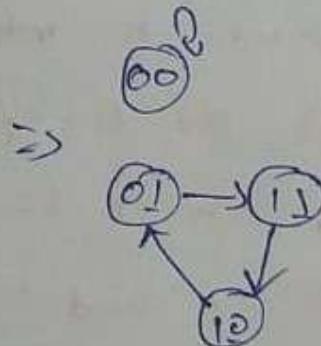

~~we tap at 01 when 10110110 ...~~

initial state is general,  $\frac{\alpha_1 \alpha_0}{1 0}$  then subtract  
at 10 on way

$10 \rightarrow 01 \rightarrow 11 \rightarrow 10 \rightarrow 01 \rightarrow 11 \dots$

~~tap at 5th  $\alpha_0$~~



~~0 1 10110110 ...~~

## Q1) M Sequence generation

50

We want to design a synchronous counter that counts the sequence 0-1-0-2-0-3 and then repeats the sequence. Min. no. of JK FFs required to implement this counter is —

- a) 1    b) 2    c) 4    d) 5

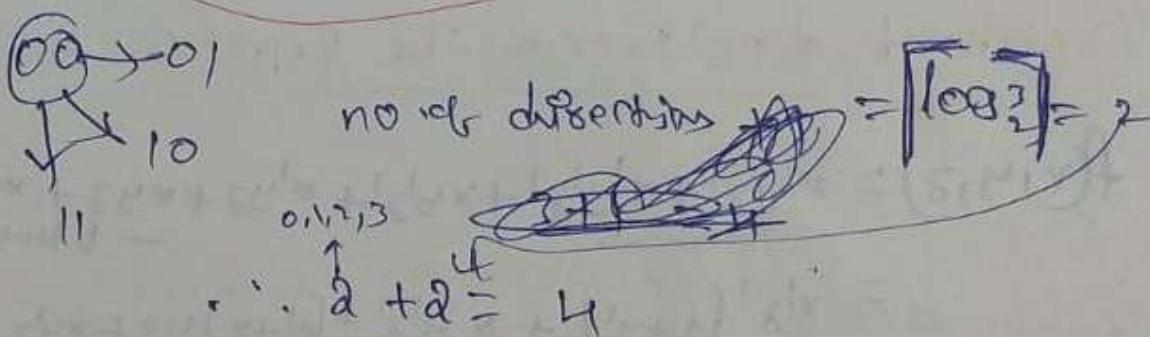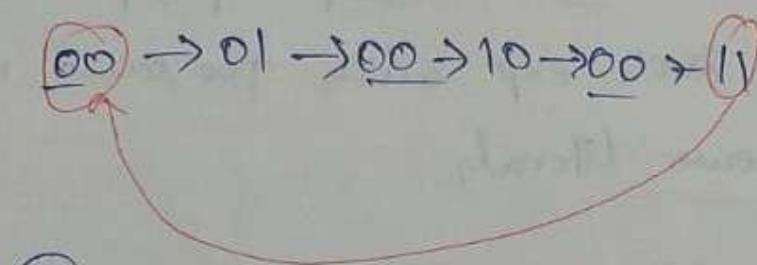

## ② Minimization

### ① Introduction to Minimization of Boolean Expressions

→ A switching function can usually be represented by writing a no. of expression.

$$\text{Ex: } f(x_1, y_1, z) = xy + yz + zx$$

$$= x'y'z + x'y'z' + x'yz + xyz$$

→ While simplifying a switching function  $f(x_1, x_2, \dots, x_n)$ , our aim is to find an